

313126

UNIT-IV.

TIMER AND PLL :


1) IC 555 timer.

2) Voltage controlled oscillator (VCO)

3) Phase locked loop (PLL)


IC 555 Timer:

Pin DIAGRAM.

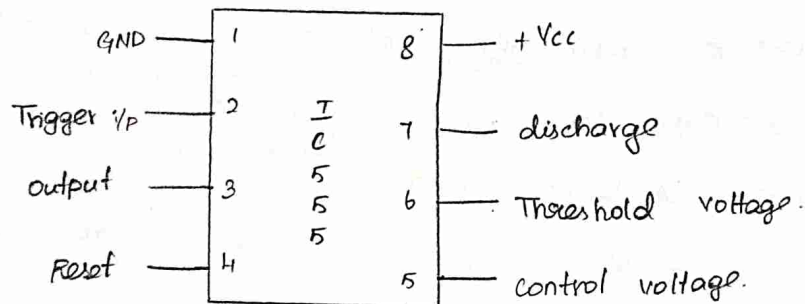

Supply voltage is 4.8 to 18 V.

INTERNAL CIRCUIT:

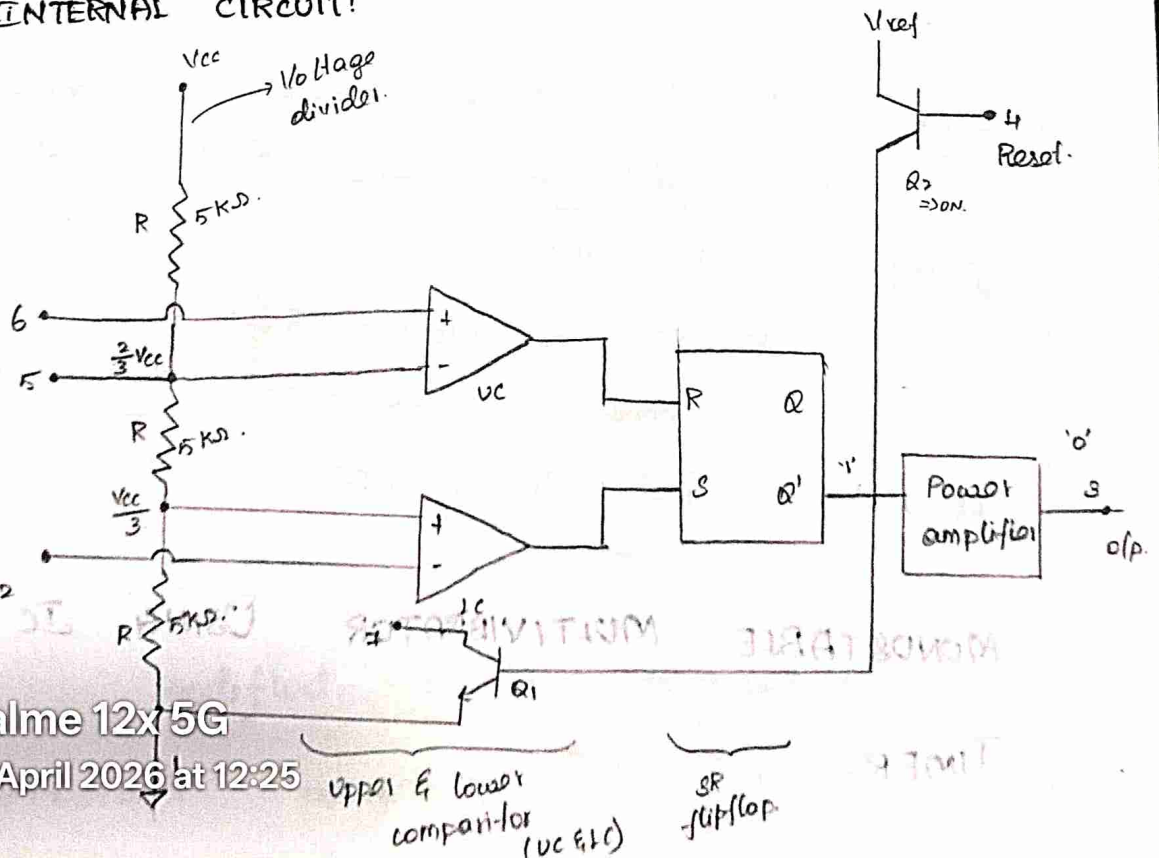


realme 12x 5G

20 April 2026 at 12:25



⇒ to improve the stability we add one capacitor in feedback.

Practical differentiator:

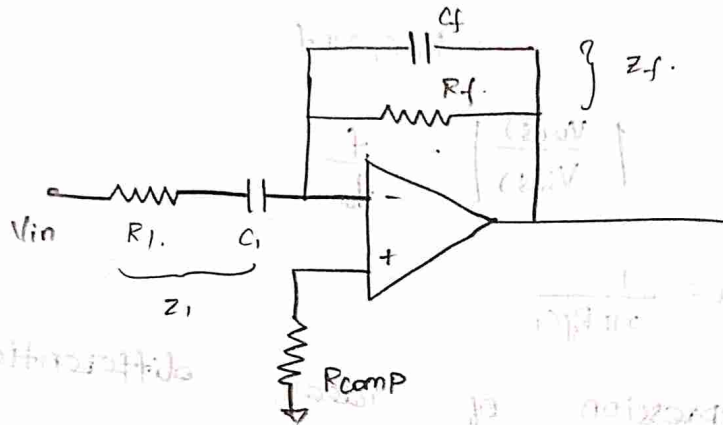

$$Z_f = R_f \parallel \frac{1}{sC_f}, \quad Z_i = R_1 + \frac{1}{sC_1}$$

$$\frac{V_o}{V_{in}} = - \frac{Z_f}{Z_i}$$

$$Z_i = \frac{sR_1C_1 + 1}{sC_1}$$

$$\frac{1}{Z_f} = \frac{1}{R_f} + \frac{1}{1/sC_f}$$

$$= \frac{1}{R_f} + sC_f$$

$$= \frac{1 + sR_fC_f}{R_f}$$

$$Z_f = \frac{R_f}{1 + sR_fC_f}$$

$$\frac{V_o}{V_{in}} = - \frac{R_f}{1 + sR_fC_f} \cdot \frac{1}{\frac{sR_1C_1 + 1}{sC_1}}$$

realme 12x 5G =
20 April 2026 at 12:23



Gain, $\frac{V_o(s)}{V_i(s)} = -R_f C_1 (j\omega)$.

$$\left| \frac{V_o(s)}{V_i(s)} \right| = R_f C_1 \omega$$

$$= R_f C_1 2\pi f.$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \frac{f}{f_a}$$

where, $f_a = \frac{1}{2\pi R_f C_1}$

* Gain expression of ideal differentiation.

Limitation of ideal differentiator:

$\Rightarrow$ when (i/p) signal frequency $\uparrow$ so what (about)

(i) the $\rightarrow$ i/p impedance.
 $\rightarrow$ gain.

* i/p frequency $\uparrow$ so - gain is more, it leads unstable.

* for high i/p frequency - i/p impedance is very low becoz of this the circuit will be affected by high frequency noise.

$\Rightarrow$ To overcome this we add

realme 12x 5G

20 April 2026 at 12:23

impedance

It is not

is

affected

'R'


when

high frequency.


High freq noise.



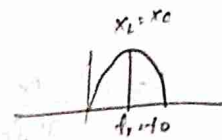Resonance - at which the gain is max.
($x_L = x_C$)



Differentiator:

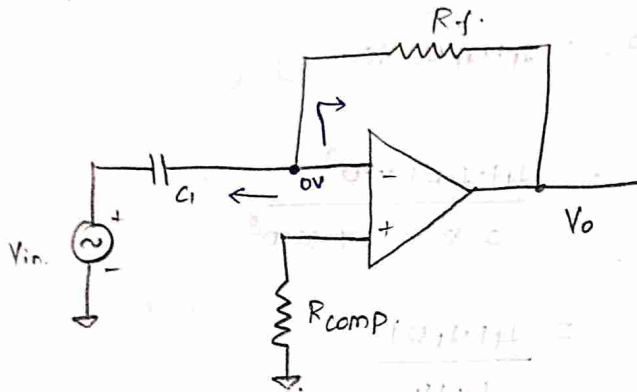

$\Rightarrow$ It differentiates the applied i/p.

Apply Nodal equation,

$$\frac{0 - V_{in}}{\left(\frac{1}{sC_1}\right)} + \frac{0 - V_o}{R_f} = 0$$

$$\frac{V_o(s)}{R_f} = -sC_1 V_{in}(s)$$

$$V_o(s) = -sR_f C_1 V_{in}(s)$$

$$\frac{V_o(s)}{V_i(s)} = -R_f C_1 s$$

Inverse Laplace of V_o :

$$\mathcal{L}^{-1}[V_o(s)] \Rightarrow$$

$$V_o(t) = -R_f C_1 \frac{dV_{in}(t)}{dt}$$

$$R_3 = 63.111 \Omega$$


$$4). R_3 = \frac{Q}{\pi f_{oc}} = \frac{13}{3.14 \times 1 \times 10^3 \times 10^{-7}} \\ = 4.1401 \times 10^4$$

$$R_3 = 41.401 \text{ K}\Omega$$

$$5). A_F = \frac{R_3}{R_1} = \frac{41.401 \times 10^3}{2 \times 2.07 \times 10^3} \\ = \frac{41.401}{4.14}$$

$$= 10.000$$

$$A_F = 10$$

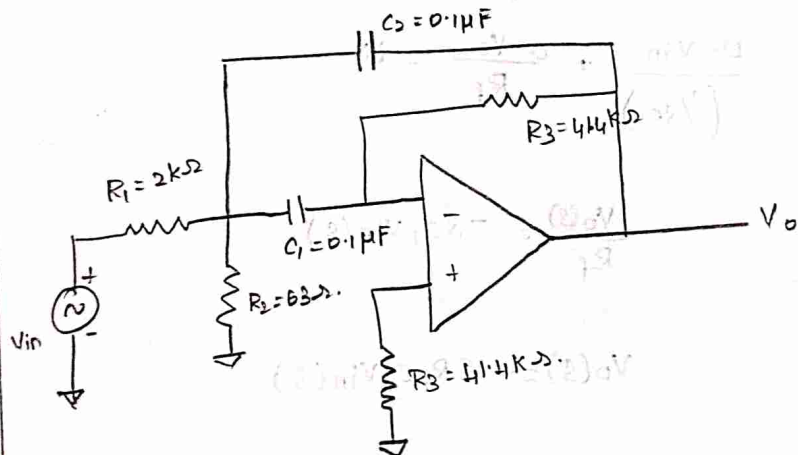

Find R_3' from $f_0 = 1 \text{ kHz}$ to 10 kHz .

$$R_3' = R_3 \left(\frac{f_0}{f_0'} \right)$$

$$= 63.111 \times \frac{1 \times 10^3}{10 \times 10^3}$$

$$R_3' = 6.311 \Omega$$



$$3). R_2 = \frac{Q}{2\pi f_0 C [2Q^2 - A_F]}$$

$$4). R_3 = \frac{Q+1}{\pi f_0 C}$$

$$5). A_F = \frac{R_3}{2R_1}$$

$$6). R_3' = R_3 \left[\frac{f_0}{f_0'} \right]$$

$$\text{also } A_F < 2Q^2.$$

$f_0 \rightarrow$ initial value of centre frequency
change to

$f_0' \rightarrow$ final value.
change $R_2 \rightarrow R_2'$

(ii). Design a NBPF with centre frequency of 1 kHz, $Q = 13$ and $A_F = 10$ also assume $C = 0.1 \mu F$.

Sol: Given, $f_0 = 1 \text{ kHz}$, $Q = 13$, $A_F = 10$.

$$1). C_1 = C_2 = 0.1 \mu F.$$

$$2). R_1 = \frac{Q}{2\pi f_0 C A_F} = \frac{13}{2 \times 3.14 \times 1 \times 10^3 \times 10^{-7} \times 10} = \frac{13}{6.28}$$

$$R_1 = 2.07 \text{ k}\Omega$$

$$3). R_2 = \frac{Q}{2\pi f_0 C [2Q^2 - A_F]} = \frac{13}{6.28 \times 10^3 \times 10^{-7} [2 \times 169 - 10]} = \frac{13}{6.28 \cdot (328) \times 10^{-4}} = \frac{13}{2059.84 \times 10^{-4}} = 6.3111 \times 10^{-4} \times 10^3$$




Consider

$$f_{in} > f_H$$

$x_{c1} \& x_{c2} = 0$ [it act as closed switch/ circuit]


$$V_0 = 0$$

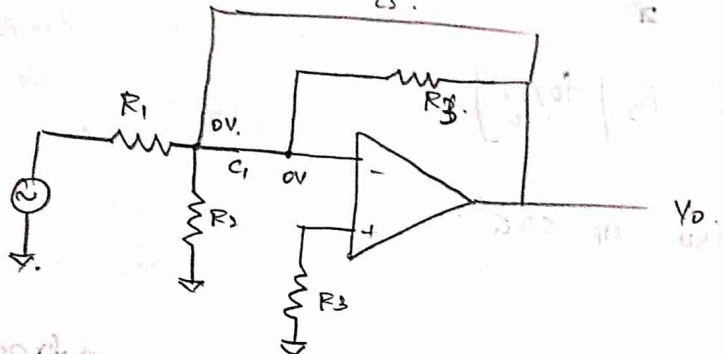$\Rightarrow$ It exhibits the behaviours of LPF.



Case (iii):

consider, $f_L < f < f_H$.

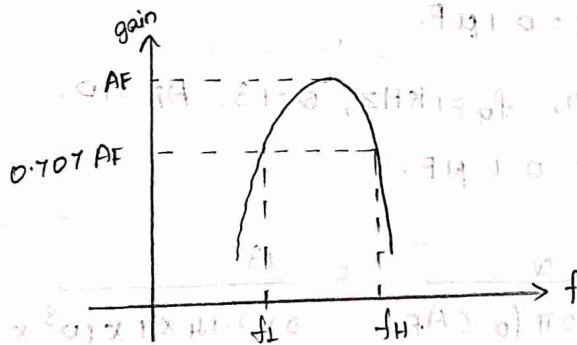

Advantage:

* By changing R_2 we can transient the center frequency of NBPF from one value to another value.

Steps: Design parameters for NBPF:

1). Assume $C_1 = C_2 = C$.


realme 12x5G

20 April 2026 at 12:23

$$= \frac{Q}{2\pi f_c \cdot C \cdot AF}$$



frequency above

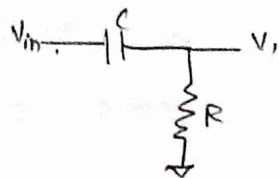

$$V_i = \frac{V_{in}}{R + 1/sC} \cdot R$$

$$V_i = V_{in} \cdot \left(\frac{R s C}{1 + s R C} \right) \rightarrow (1)$$

$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_i$$

$$= A_F \cdot \frac{V_{in} (s R C)}{1 + s R C}$$

$$\frac{V_o}{V_{in}} = A_F \cdot \frac{s R C}{1 + s R C}$$

$$\therefore s = j\omega$$

$$\omega = 2\pi f$$

$$\frac{V_o}{V_{in}} = A_F \cdot \left(\frac{j 2\pi f R C}{1 + j 2\pi f R C} \right)$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{A_F \cdot j (f/f_L)}{1 + j (f/f_L)}}$$

$$\text{here, } f_L = \frac{1}{2\pi R C}$$

$f_L \rightarrow$ cut-off frequency of HPF.

case (i): $f \ll f_L$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \frac{A_c (f/f_L)}{\sqrt{1 + (f/f_L)^2}}$$

[$\therefore$ It's gain is very less]

$$\left| \frac{V_o(s)}{V_i(s)} \right| < A_F \rightarrow \text{reduced.}$$


attenuates all the signal

frequency, $f \ll f_L$



realme 12x 5G

20 April 2026 at 12:22

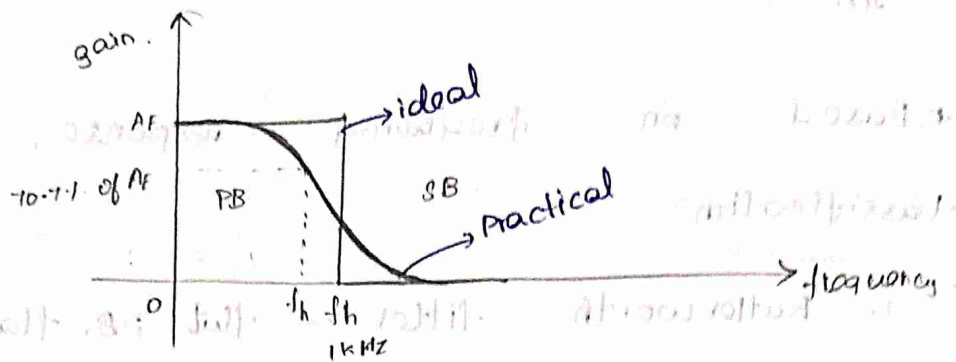

For ideal characteristics of LPF,

PB = 100% gain. [we get 'exact transition']

SB = No gain.

For Practical,

* We can't get exact transition from high to low.

* It is monotonically decreasing (gain) as frequency $\uparrow$ so.

$f_h \rightarrow$ frequency at which the separation (of) transition from PB to SB; [ideal].
[cutoff / corner freq].

$f_h \rightarrow$ It is frequency at which the gain reduced by 3 dB.

The gain which is reduced to 10.7% of its maximum gain, that


frequency cut-off frequency. [Practical].



realme 12x 5G

20 April 2026 at 12:21

First order butlerworth active LPF:

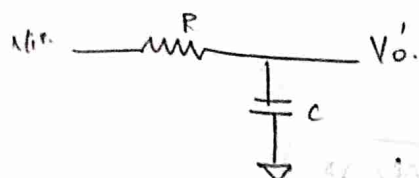

Passive LPF

⇒ max gain is, $A = 1$.


when $(\omega = 0)$

⇒ when $\omega = \infty$, $A = 0$.

$$V_o' = \frac{V_{in}}{R + 1/sC} \cdot \frac{1}{sC}$$

$$V_o' = \frac{V_{in}}{1 + j\omega RC}$$
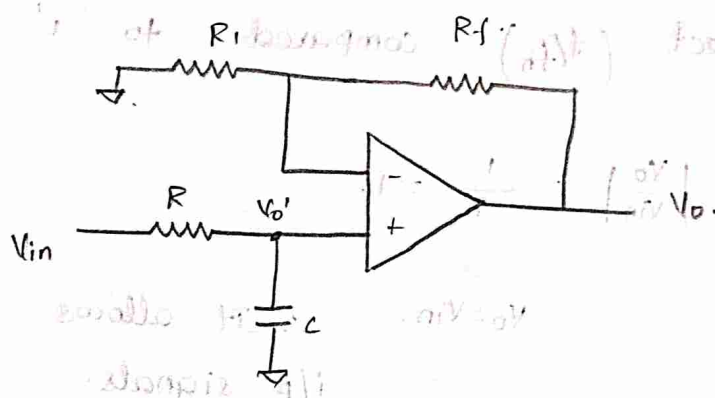
$$A = \frac{V_o'}{V_{in}} = \frac{1}{1 + j\omega RC}$$



$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_o' \rightarrow \textcircled{1}$$

Advantage:

⇒ In order to improve the gain of

passive LPF we added active component. that advantage of active component is applied to active filter.

⇒ By choosing proper R_f & R_i

we can improve the gain.

$$V_o = A_F \cdot \frac{V_{in}}{1 + j\omega RC}$$

Advantage: 2m

1. No loading-effect

in active filter.

2. Small size compare to passive filter.

3. Low cost becoz [inductance is not involved].

$$= \frac{A_F}{1 + j\omega RC} \cdot V_{in}$$

$$= \frac{A_F}{1 + j2\pi fRC} \cdot V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{A_F}{1 + j(f/f_h)} \rightarrow \textcircled{5}$$



where, $f_h = \frac{1}{2\pi RC}$.

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{1 + (f/f_h)^2}}$$

case (i): $f \ll f_h$.

Neglect (f/f_h) compared to '1'

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{1} = 1.$$

$V_o = V_{in}$. $\therefore$ It allows all the i/p signals.

case (ii): $f \gg f_h$.

neglect 1, $1 + (f/f_h)^2 \approx (f/f_h)^2$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{(f/f_h)^2}} = \frac{1}{f/f_h}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{f_h}{f}$$

$\therefore$ signal is get attenuated (deselected).

It suppress the all i/p signal.



realme 12x 5G

20 April 2026 at 12:21


case (iii):

$$f = f_h.$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{1 + (1)^2}} = \frac{1}{\sqrt{2}}.$$

$$\left| \frac{V_o}{V_{in}} \right| = 0.707$$

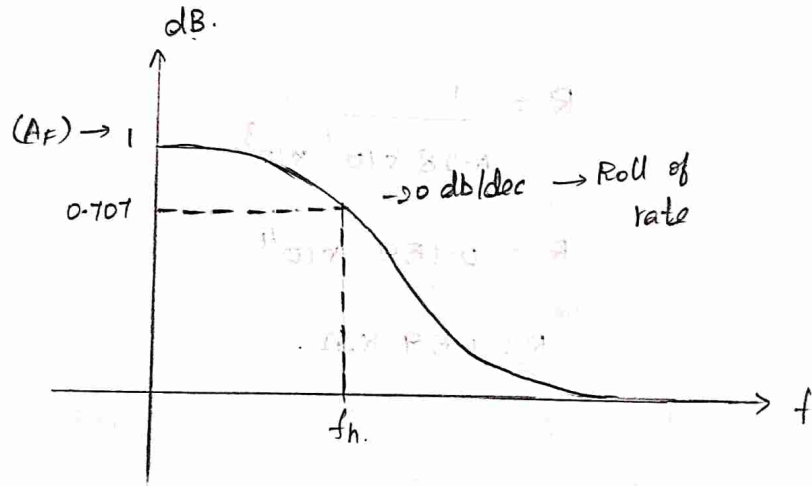The gain of circuit is reduced to 0.707 times of maximum gain.



In General,

Roll-of rate of n^{th} order filter is.

-n 20 db/dec.



7. Design a Butterworth 1st order LFP with a cutoff frequency of 1 kHz.

Sol:-

$$f_h = \frac{1}{2\pi RC} = 1 \times 10^3 \text{ Hz.}$$


Let us take, $C = 0.1 \mu\text{F}$.

$$10^3 = \frac{1}{2 \times 3.14 \times R \times 0.1 \times 10^{-6}}$$

$$R = \frac{1}{6.28 \times 10^{-7} \times 10^3}$$

$$R = 0.159 \times 10^4$$

$$R = 1.59 \text{ k}\Omega$$

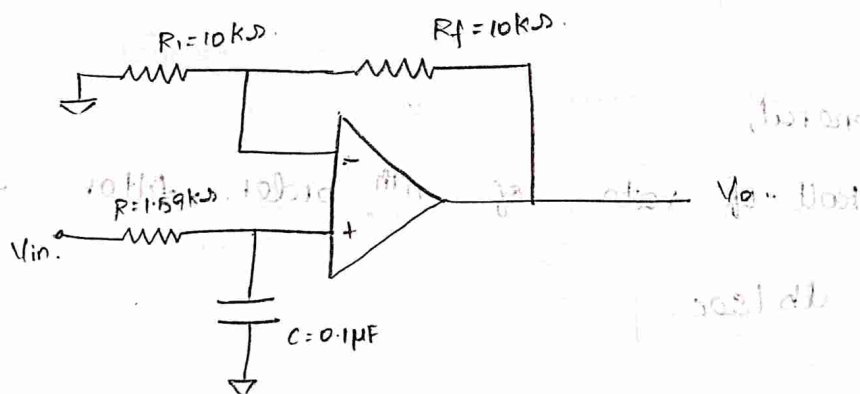

here, $1 + \frac{R_f}{R_i} = A_f = 1$

assume $R_i = R_f = 10 \text{ k}\Omega$.

$$\therefore 1 + \frac{R_f}{R_f} = A_f$$

$$1 + 1 = A_f$$

$$\text{gain, } A_f = 2$$




realme 12x 5G

20 April 2026 at 12:22


LPF
kHz.

2nd order Butterworth LPF:

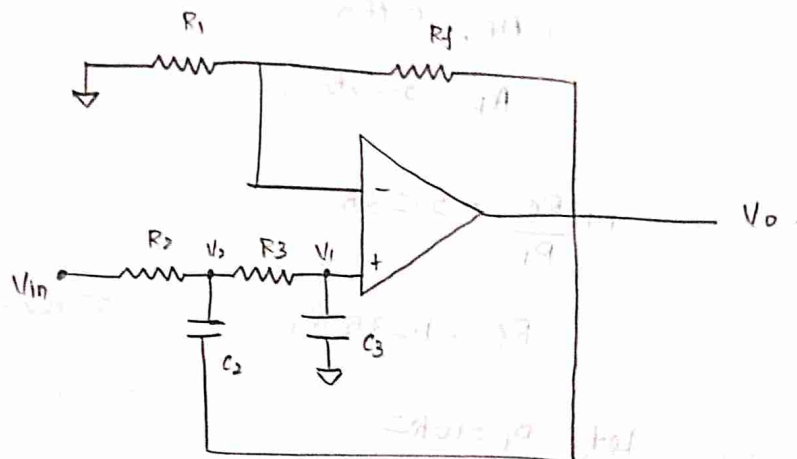The order of Butterworth LPF which strongly no. of RC section connected in the circuit.



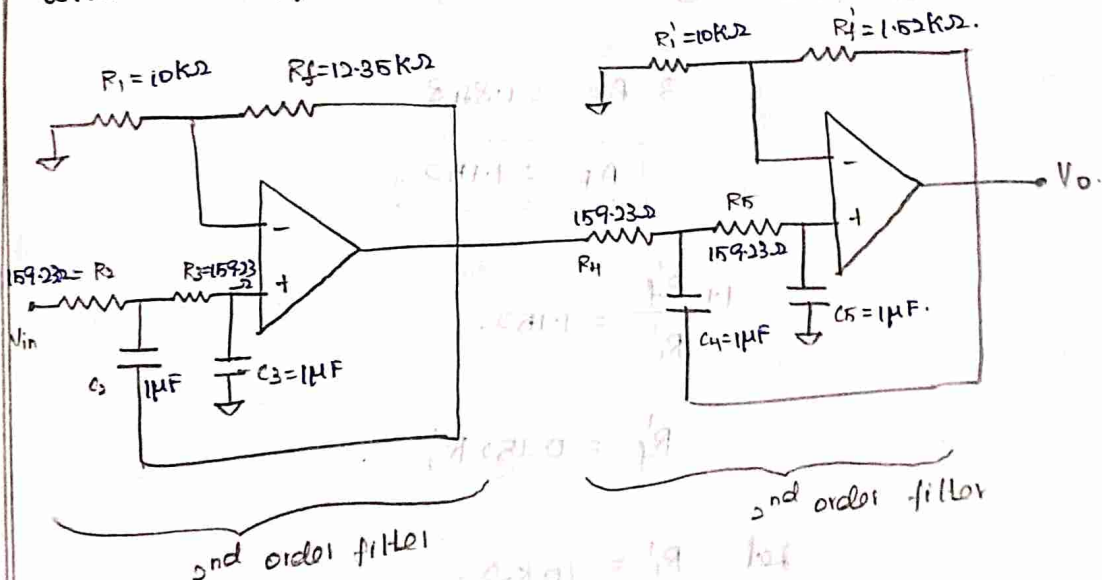8. Design a Butterworth n^{th} order LPF with cutoff frequency of 1 kHz.



Sol:

Given, $f_h = 1 \text{ kHz}$.

$$W.K.T, (s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$$

→ ①.



From 2nd order Butterworth LPF,

$$s^2 + \frac{(3-A_F)}{R_C} s + \frac{1}{R_C^2} \rightarrow \textcircled{2}$$

compare $\textcircled{1}$ & $\textcircled{2}$, for 1st & 2nd order.

$$3 - A_F = 0.765$$

$$A_F = 2.235$$

$$1 + \frac{R_f}{R_i} = 2.235$$

$$R_f = 1.235 R_i$$

$$\text{Let } R_i = 10 \text{ k}\Omega$$

$$R_f = 12.35 \text{ k}\Omega$$

compare $\textcircled{1}$ & $\textcircled{2}$, for 2nd (2nd order)

$$3 - A_F = 1.848$$

$$A_F = 1.152$$

$$1 + \frac{R'_f}{R'_i} = 1.152$$

$$R'_f = 0.152 R'_i$$

$$\text{Let } R'_i = 10 \text{ k}\Omega$$

$$R'_f = 1.52 \text{ k}\Omega$$

Let us assume, $R_2 = R_3 = R_4 = R_5 = R$

$$C_2 = C_3 = C_4 = C_5 = C$$



realme 12x 5G

20 April 2026 at 12:22

$$f_h = \frac{1}{2\pi RC} = 10^3 \text{ Hz}$$

Let, $C = 1 \mu F$

$$R = \frac{1}{6.28 \times 10^3 \times 10^{-6}}$$

$$R = 0.159 \text{ k}\Omega$$

$$R = 159.23 \Omega$$

Difference btw 1st & 2nd order LPF:

1st RC sections.

For 1st order - 1 RC section

For 2nd order - 2 RC sections.

∴ Roll-off rate.

1st order = -20 dB/dec.

2nd order = -40 dB/dec.

For nth order LPF:

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_h} \right)^{2n}}} ; f_h = \frac{1}{2\pi RC}$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = |H(j\omega)|$$

allows low freq & it eliminates high

realme 12x 5G

20 April 2026 at 12:02


Noise

[it is used in band-limited signal]



HPF $\rightarrow$ It allows all the frequency above the cut-off frequency.


High pass filter:

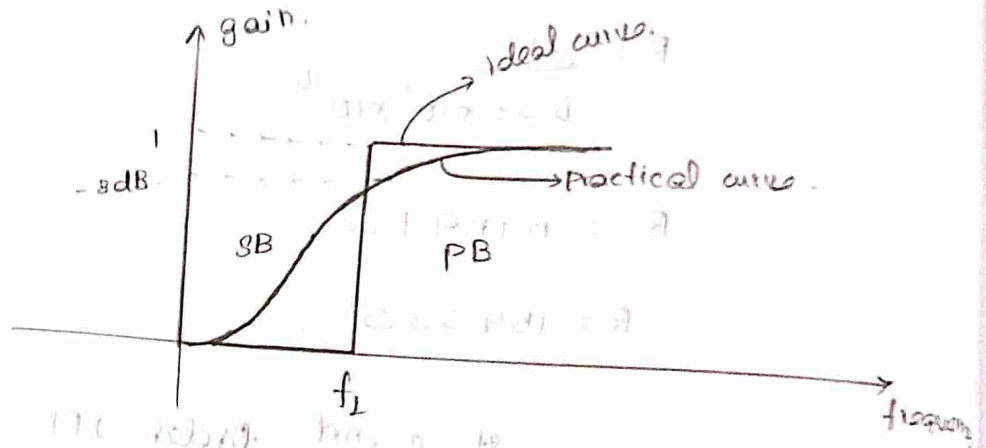

Exchange capacitor & Resistor in LPF

we get HPF.

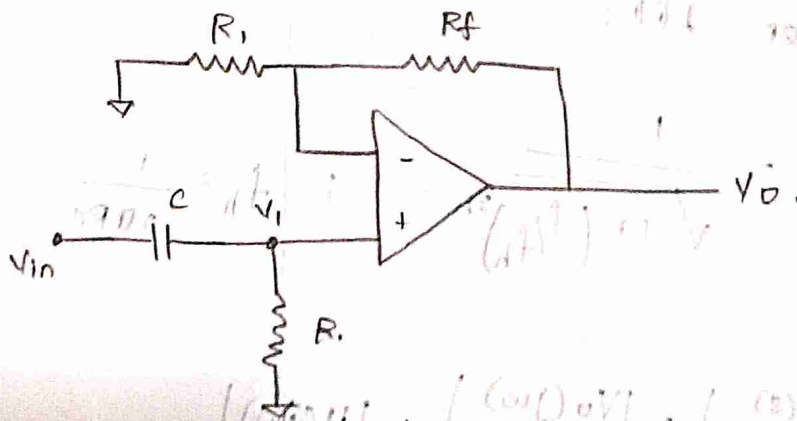
The filter which can allow all signal above the cutoff frequency and attenuate all the frequency signal below the cutoff frequency, 1st order active High pass filter.



realme 12x 5G

20 April 2026 at 12:25
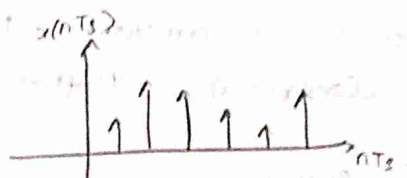
$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$



discrete - amplitude is continuous
digital - it has only 0's & 1's

Quantizer - It assigns the binary value to each & every amplitude of signal.

By smoothing the stair signal of i/p (analog signal), we get the approximate transmitted signal.

Sampling & Reconstruction :

⇒ To sample we have 2 condition.

1. Nyquist condition / criterion - $f_m = 2f_m = f_c$


* It says how to select the sample frequency.

$T_s \geq 2f_m$ [in order to reconstruct the original transmitter signal]

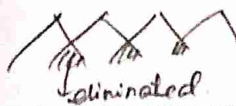2. To sample the analog signal should be band-limited signal.
+ for that we use anti-aliasing filter.

aliasing effect - overlapping of adjacent spectrum because of that improper in

condition, o/p is we get some elimination




Types:

1. weighted
2. R-2R
3. 3 input


DAC:

1 o/p.

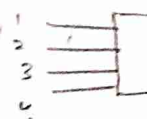

For DAC
summing

1. weighted

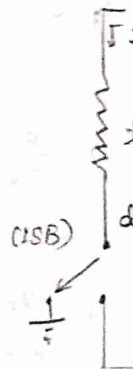

realme 12x 5G

20 April 2026 at 12:27