



20/01/2026

Unit - 2.


Applications of OP-AMP :-

2 types:

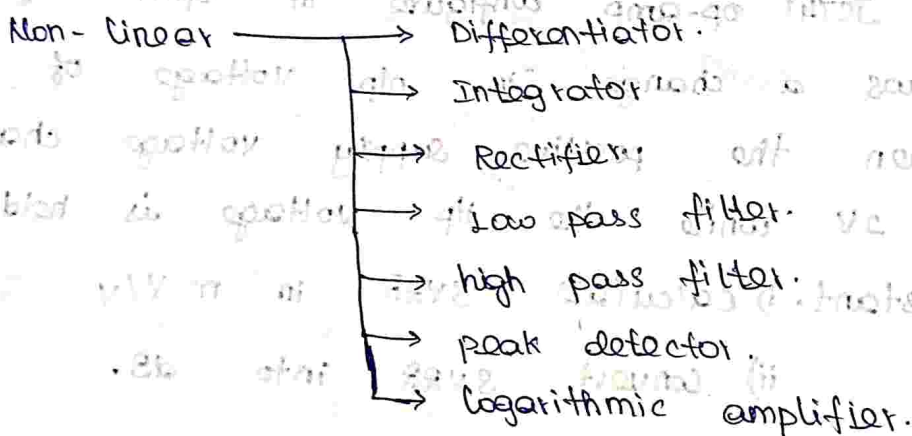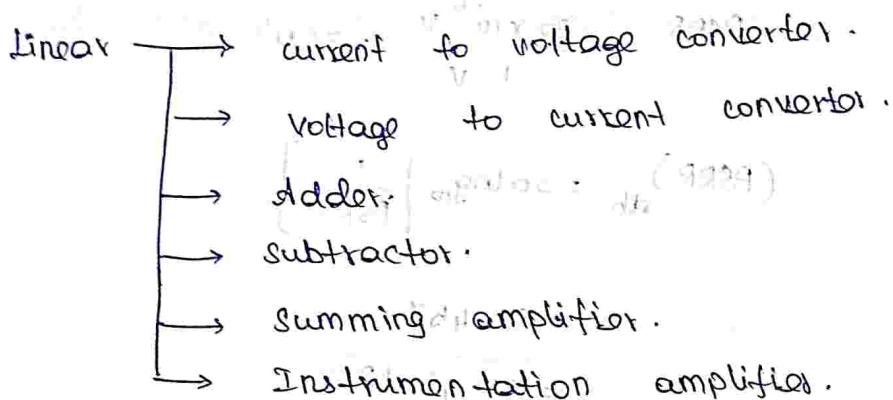1. Linear application. (linear relationship b/w i/p & o/p)
2. Non-linear application.



①. Inverting amplifier.

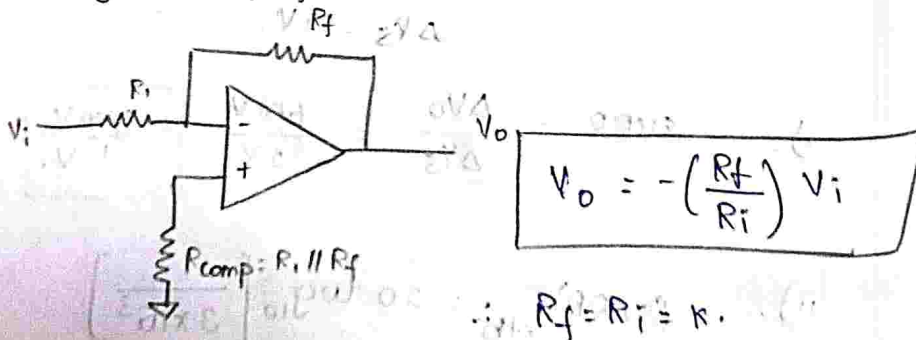

then - $V_o = -V_i$




realme 12x 5G

20 April 2026 at 12:15

$V_o = -V_i \rightarrow$ act as scale changer / inverter.

②. Non-inverting amplifier.

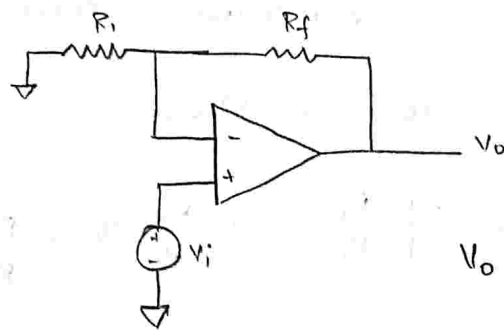


$$V_o = \left[1 + \frac{R_f}{R_1} \right] V_i.$$

Inverting Summing amplifier.

$\Rightarrow$ to get this, we modify the inverting amplifier.

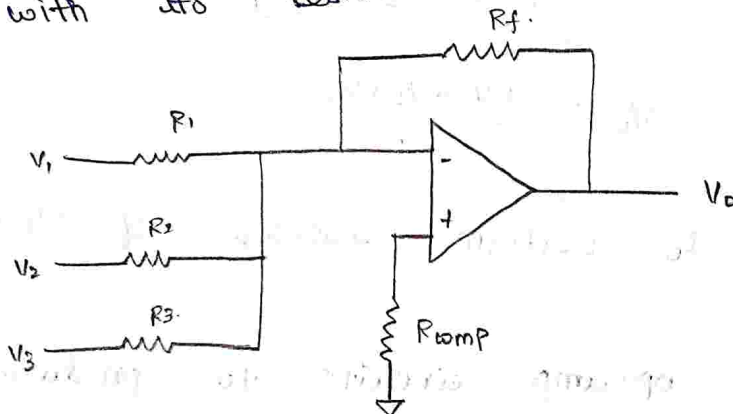* By applying multiple inputs along with its resistance.



* It performs addition and amplification.

$$V_{o1} \Rightarrow V_o \text{ due to } 'V_1' \text{ alone} = -\frac{R_f}{R_1} V_1$$

$$V_{o2} \Rightarrow \text{o/p } (V_o) \text{ due to } 'V_2' \text{ alone} = -\frac{R_f}{R_2} V_2$$

$$V_{o3} \Rightarrow V_o \text{ due to } 'V_3' \text{ alone} = -\frac{R_f}{R_3} V_3$$



realme 12x 5G

20 April 2026 at 12:15

by superposition theorem,

Total output is equal to output of each individual source.

$$V_o = V_{o1} + V_{o2} + V_{o3}.$$

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

if $R_1 = R_2 = R_3 = R_f$

then, $V_o = - (V_1 + V_2 + V_3)$ it performs addition of i/p's.

It has 180° phase shift]
 btw i/p & o/p.

if $R_1 = R_2 = R_3 = 3R_f$.

$$V_o = - \left[\frac{V_1}{3} + \frac{V_2}{3} + \frac{V_3}{3} \right]$$

$$V_o = - \frac{(V_1 + V_2 + V_3)}{3}$$

It can able to perform average of i/p's.

①. design an op-amp circuits to produce the output expression of $V_o = - (0.2 V_1 + V_2 + V_3)$


Sol: Inverting summing amplifier.

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$



realme 12x 5G

20 April 2026 at 12:15

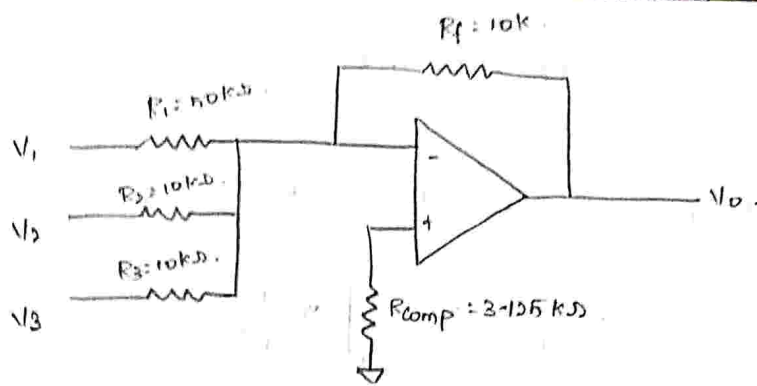

compare equation,

$$\frac{R_f}{R_1} V_1 = 0.2 V_1$$

$$\frac{R_f}{R_1} = 0.2$$

$$R_1 = \frac{R_f}{0.2}$$

let choose $R_f = 10k$.

$$R_1 = \frac{10k}{0.2} = 50k\Omega$$

Similarly,

$$\frac{R_f}{R_2} V_2 = V_2$$

$$R_f = R_2$$

$$\therefore R_2 = 10k\Omega$$

$$\frac{R_f}{R_3} V_3 = V_3$$

$$R_3 = R_f$$

$$\therefore R_3 = 10k\Omega$$



realme 12x 5G

20 April 2026 at 12:15

$$R_{comp} = R_1 \parallel R_2 \parallel R_3 \parallel R_f.$$

$$\frac{1}{R_{comp}} = \frac{1}{50k} + \frac{1}{10k} + \frac{1}{10k} + \frac{1}{10k}.$$


$$= \left[\frac{1}{50} + \frac{3 \times 1}{10} \right] \times \frac{1}{10^3}.$$

$$\frac{1}{R_{comp}} = \frac{16}{50} \times \frac{1}{10^3}.$$

$$R_{comp} = \frac{50}{16} \times 10^3.$$

$$R_{comp} = 3.125 \times 10^3 \Omega$$

Non Inverting - Summing Amplifier.

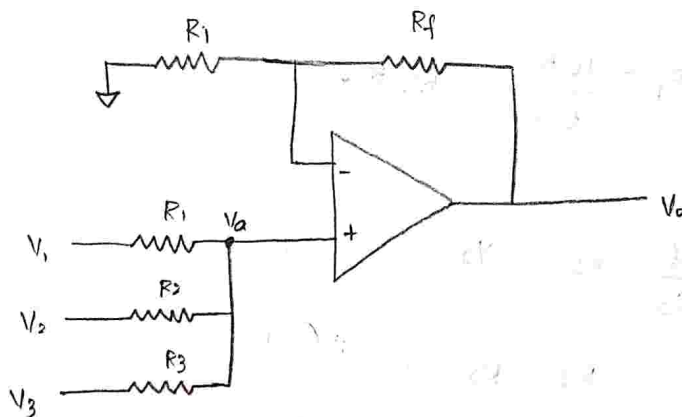

$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_a \rightarrow \text{①.}$$

Apply nodal analysis at V_a .

$$\frac{V_a - V_1}{R_1} + \frac{V_a - V_2}{R_2} + \frac{V_a - V_3}{R_3} = 0.$$

$$V_a \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}.$$

$$\therefore V_a = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \rightarrow \textcircled{2}$$

Substitute $\textcircled{2}$ in equ $\textcircled{1}$.

$$V_o = \left[1 + \frac{R_f}{R_i} \right] \frac{\left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]}{\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]}$$

Let us assume that

$$R_1 = R_2 = R_3 = R$$

$$V_o = \left[1 + \frac{R_f}{R_i} \right] \frac{\frac{V_1 + V_2 + V_3}{R}}{\frac{3}{R}}$$

$$V_o = \left(1 + \frac{R_f}{R_i} \right) \left(\frac{V_1 + V_2 + V_3}{3} \right)$$

choose , $R_i = \frac{R_f}{2}$.

$$V_o = \left[1 + \frac{2R_f}{R_f} \right] \left[\frac{V_1 + V_2 + V_3}{3} \right]$$

$$V_o = (3) \frac{V_1 + V_2 + V_3}{3}$$

$$\therefore V_o = V_1 + V_2 + V_3$$

$\therefore$ input and output of circuit

is same phase.

$\frac{V_3}{R_3}$




realme 12x 5G

20 April 2026 at 12:15

Subtractor:

* Difference Amplifier is used here.

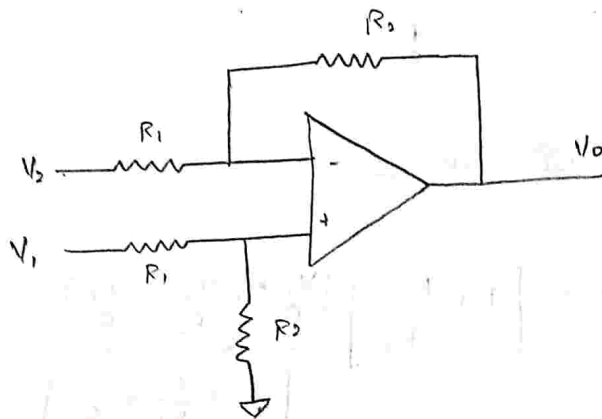


$$V_o = \frac{R_2}{R_1} (V_1 - V_2)$$

if $R_2 = R_1$,

$$\text{then } V_o = (V_1 - V_2)$$

⇒ it performs subtractor.

Adder - subtractor Circuit:

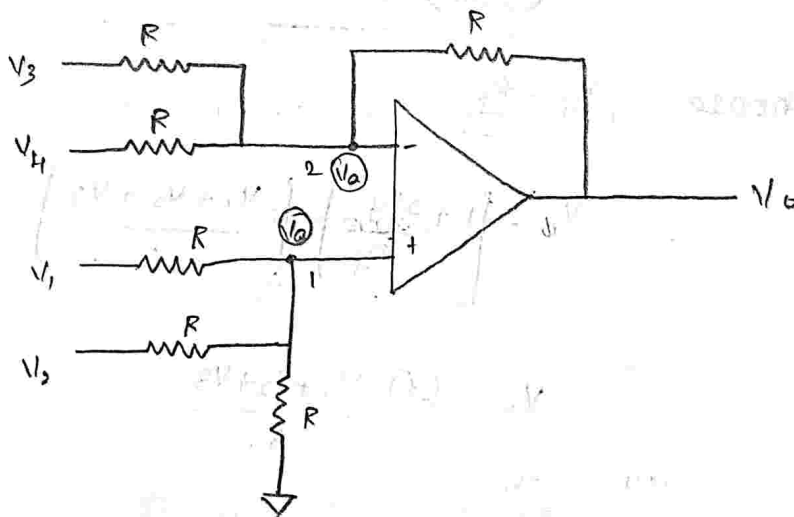

apply nodal analysis at node 1

$$\frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - 0}{R} = 0.$$

realme 12x 5G

20 April 2026 at 12:15

$$\therefore V_a \left[\frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right] = \frac{V_1}{R} + \frac{V_2}{R}$$



$$V_a = \frac{V_1 + V_2}{\frac{R}{\frac{3}{R}}}$$

$$V_a \left[\frac{3}{R} \right] = \frac{V_1 + V_2}{R} \rightarrow \textcircled{1}$$

apply nodal analysis at node a.

$$\frac{V_a - V_3}{R} + \frac{V_a - V_4}{R} + \frac{V_a - V_o}{R} = 0.$$

$$V_a \left[\frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right] = \frac{V_3}{R} + \frac{V_4}{R} + \frac{V_o}{R}.$$

$$V_a \left[\frac{3}{R} \right] = \frac{V_3 + V_4 + V_o}{R} \rightarrow \textcircled{2}$$

equate $\textcircled{1}$ & $\textcircled{2}$.

$$\frac{V_1 + V_2}{R} = \frac{V_3 + V_4 + V_o}{R}$$

$$\therefore V_o = (V_1 + V_2) - (V_3 + V_4)$$

Instrumentation Amplifier: [transducer bridge Based Instrumentation Amplifier]

transducer - convert non-electrical signal to electrical signal.

It is able to measure any physical quantity.


eg: temp, humidity, water flow, pressure

The o/p of transducer is very weak
it is connected to amplifier in that
we can see the o/p.



realme 12x 5G


20 April 2026 at 12:15

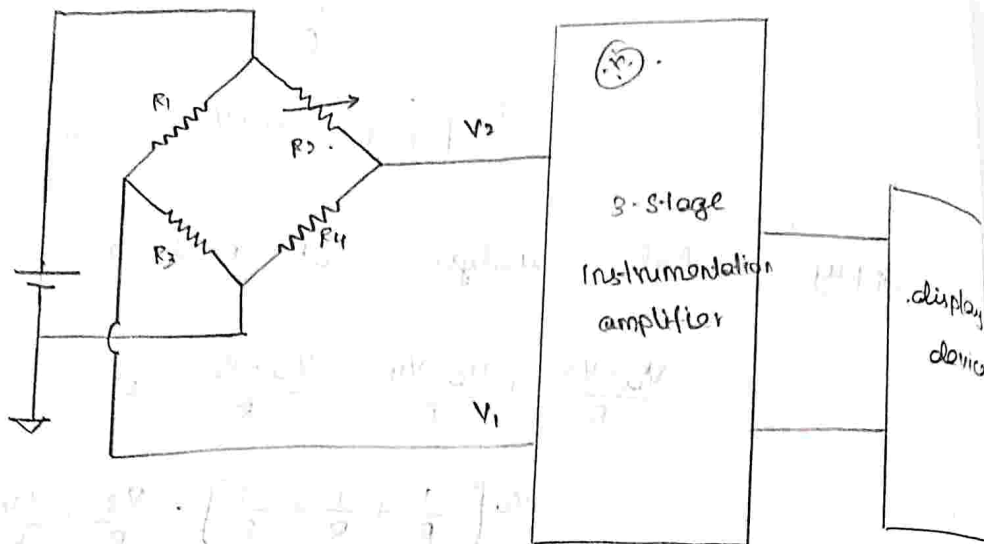

V_2 & V_1 is weak so it connected to Instrumentation amplifier.

* In difference amplifier loading effect is created becoz the input impedance are low to amplify.

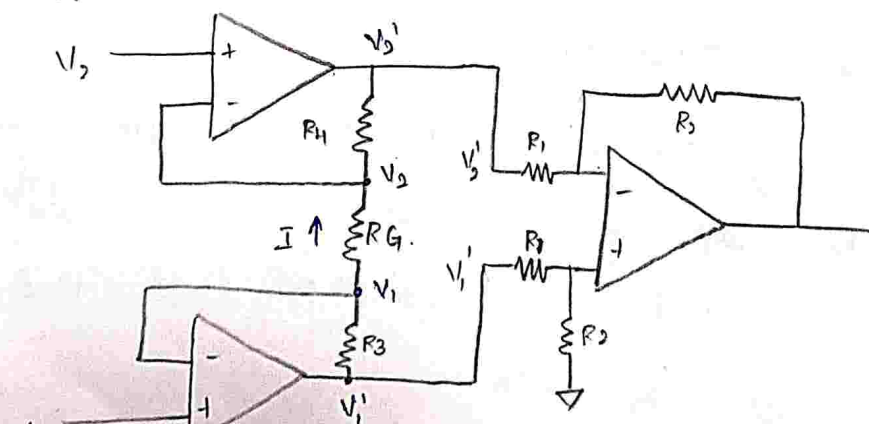* For instrumentation amplitude, the input sources given through the voltage ^{(or) buffer} follower circuit to the difference amplifier, by this loading effect is overcome.



realme 12x 5G

20 April 2026 at 12:16

2 Voltage follower circuits

+ 1 Difference amplifier

= 3 stage instrumentation amplifier

Advantage:

1. It offers high gain accuracy.
2. It offers high CMRR.
3. offers high stability.
4. low offset voltages.
5. low output impedance.


$$V_o = \frac{R_2}{R_1} (V_1' - V_2') \rightarrow \textcircled{1}$$

here $I = \frac{V_1 - V_2}{R_G} \Rightarrow V_1 - V_2 = I R_G \rightarrow \textcircled{2}$

no current flows through input terminal.

so, R_3, R_4, R_G are connected in series
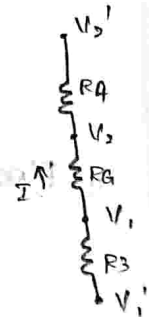
$$I = \frac{V_1' - V_2'}{R_3 + R_4 + R_G}$$



Let, $R_3 = R_4$

$$I = \frac{V_1' - V_2'}{2R_3 + R_G} \rightarrow \textcircled{3}$$

equate $\textcircled{2}$ & $\textcircled{3}$.

$$\frac{V_1 - V_2}{R_G} = \frac{V_1' - V_2'}{2R_3 + R_G}$$

$$\therefore V_1' - V_2' = \frac{2R_3 + R_G}{R_G} (V_1 - V_2)$$

$$V_1' - V_2' = \left[1 + \frac{2R_3}{R_G} \right] (V_1 - V_2) \rightarrow \textcircled{4}$$

substitute $\textcircled{4}$ in eqn $\textcircled{1}$.

$$V_o = \left(\frac{R_1}{R_1} \right) \left(1 + \frac{R_3}{R_4} \right) (V_1 - V_2)$$

$\frac{R_3}{R_1} \rightarrow$ gain of difference amplifier.

$1 + \frac{R_3}{R_4} \rightarrow$ gain of voltage follower amplifier.

Voltage to Current Converter:

$\downarrow$ [Transconductance amplifier]

1. Floating load type


V-I converter

2. Grounded load type

V-I converter.

$$\Rightarrow \text{gain} = \frac{I}{V} = \frac{1}{R} = g_m$$

1. Floating load type V-I converter.

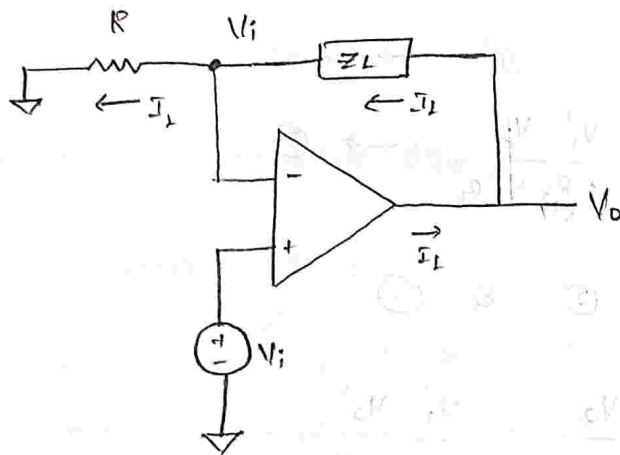

Load impedance is not grounded, it is floating, we connected to o/p.

The applied voltage should decide

realme 12x 5G


20 April 2026 at 12:16

$$I_1 = \frac{V_i}{R} \Rightarrow V_i = I_1 R.$$

Precision resistor:

At any cost, value of impedance won't change.

2. Grounded load type v-I converter.

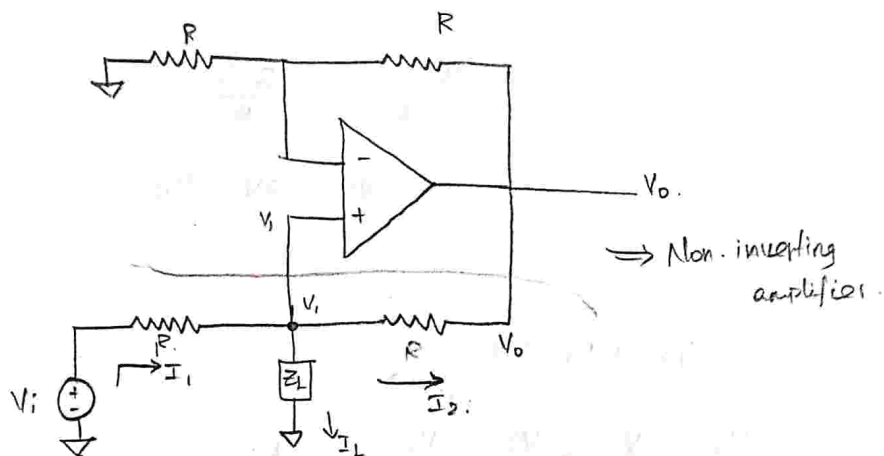

Here the load impedance is connected to ground.

Two steps is followed.

1. Apply KCL w.r.t V_i node.
2. Non-inverting amplifier.

∴ o/p of Non-inverting amplifier when V_i is known.

$$V_o = \left[1 + \frac{R}{R}\right] V_i$$

$$V_o = 2V_i \rightarrow \textcircled{1}$$

KCL eqn w.r.to Node ' V_i '



Let us assume $Z_L = R$.

$$\frac{V_o}{R} - \frac{V_i}{R} + \frac{V_i}{R} - \frac{V_i}{R} = \frac{V_i}{R}$$

$$\frac{V_o + V_i}{R} = \frac{2V_i}{R}$$

$$V_i = 2V_i - V_o$$

$$I_2 + I_1 = I_L$$

$$\frac{V_o}{R} - \frac{V_i}{R} + \frac{V_i}{R} - \frac{V_i}{R} = I_L$$

$$\frac{V_o + V_i}{R} - \frac{2V_i}{R} = I_L$$

$$V_o = I_L R + 2V_i - V_i \rightarrow \textcircled{2}$$

Sub $\textcircled{1}$ in $\textcircled{2}$.

$$V_o = I_L R + 2 \frac{V_o}{2} - V_i$$

$$V_i = I_L R$$

Precision
resistor

$$I_L = \frac{V_i}{R}$$

Y-I:

* current produced w.r to voltage.

circuit, which produce constant current

through load impedance.




realme 12x 5G

20 April 2026 at 12:16

Current to Voltage Converter:

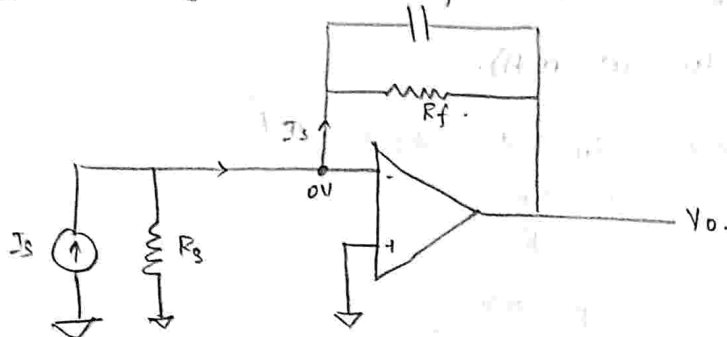Applied input current we get
o/p voltage.



Assume, there is no feedback capacitance.
 $\therefore C_f \rightarrow$ eliminate high frequency noise signals.

Apply KCL at in node.

$$I_s = \frac{0 - V_o}{R_f}$$

$$V_o = -I_s R_f$$

$$\text{gain} \Rightarrow \frac{V_o}{I_s} = -R_f = R_f$$

Gain of circuit expressed in resistance.

$\therefore I_f$ is also known as trans resistance

Amplifier.

C_f is not needed when we use

low frequency signals.

- ②. Design a $V-I$ converter with grounded load using an ideal op-amp such that i/p voltage range (0 to 5) V, output current range (0 to 10 mA).


sol: Given, $V_{in} = 5V$, $I_f = 10mA$.

$$I_f = \frac{V_{in}}{R}$$

$$R = \frac{5V}{10 \times 10^{-3}}$$

$$R = 0.5 \text{ K}\Omega$$

$$R = 500 \Omega$$

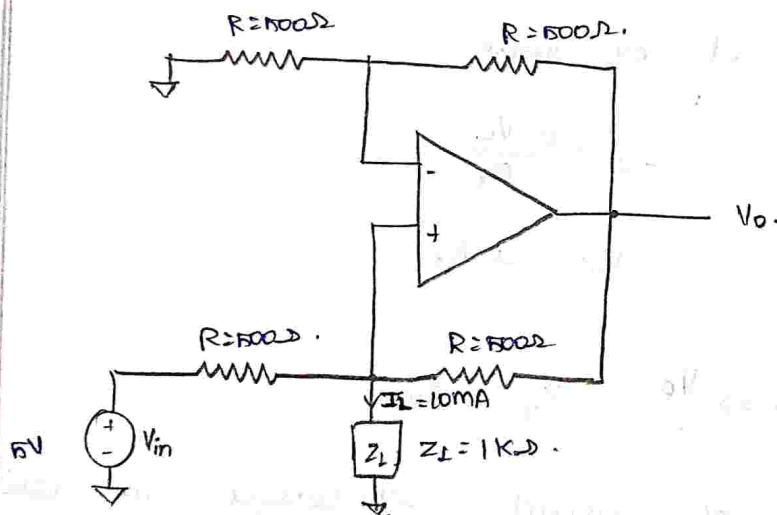

choose $Z_L = 1K\Omega$.

- ③. Design a grounded load $V-I$ converter that produces o/p current is $2mA/V$ of input signal, and maximum o/p voltage is 4 V.

sol: $I_f = \frac{V_{in}}{R}$




$$\frac{2 \text{ mA}}{1 \text{ V}} = \frac{I_L}{V_{in}} = \frac{1}{R_1}$$

$$R = \frac{1}{2 \times 10^{-3}}$$

$$R = 0.5 \text{ K}\Omega$$

$$R = 500 \Omega$$

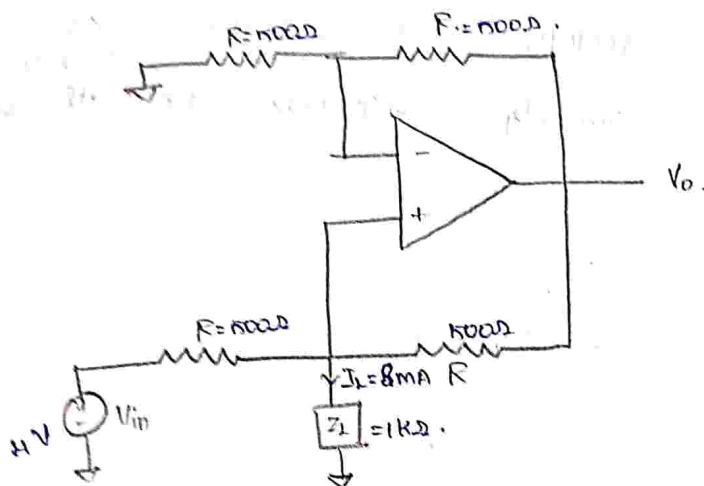

when $V_{in} = 1 \text{ V} \rightarrow I_L = 2 \text{ mA}$

$V_{in} = 4 \text{ V} \rightarrow I_L = 4 \times 2 \times 10^{-3}$

$$I_L = 8 \text{ mA}$$

Resistance remains same. (that's why

it is precision resistor),

$\Rightarrow$ when we use the input less than cut-off voltage of diode ($< 0.7 \text{ V}$), the rectifier can't rectify. then we can go for op-amp based rectifier circuit

which performs rectification.




realme 12x 5G
20 April 2026 at 12:16

Super-diode:

whenever the combination of two diodes and op-amp.

Precision Rectifier:

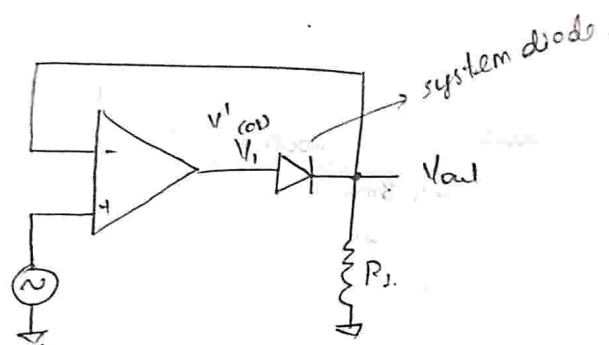Due to its open loop gain, the diode rectify the signal ($< 0.7V$) ($< \mu V$)
 V_{out} strongly depends on the diode



$$V_1 = A(V_{in} - V_{out}) \quad (\text{or}) \quad V_1 = A(V_+ - V_-)$$


$$V_1 = 0.7 + V_{out}$$

$$0.7 + V_{out} = A(V_{in} - V_{out})$$

$$\frac{0.7 + V_{out}}{A} = V_{in} - V_{out}$$




For ideal diode $\rightarrow$ No knee voltage & built-in voltage.
 $V_{in} = V_{out}$, if $A_{OL} = \infty$.

1) Normal diode

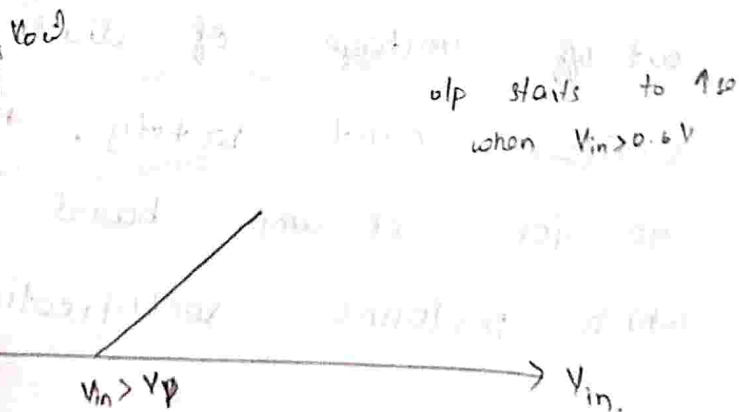

two

2). Super diode:

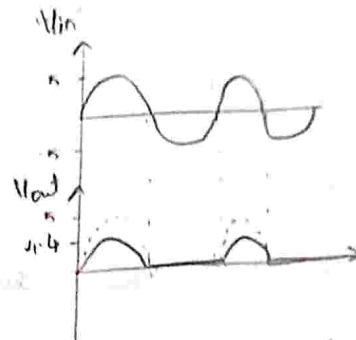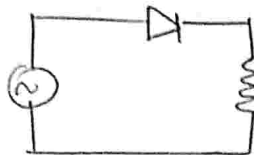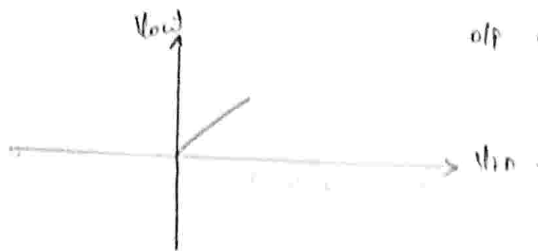

for non-ideal diode
*. Usually, diode has internal built-in voltage of $0.6V$ - Silicon, $0.3V$ - Germanium. This diode is non-ideal diode.

*. It gives the o/p by reducing $0.6V$. It doesn't rectify when i/p is less than $0.6V$.


*. In graph, it reduces the amplitude, whereas in ideal there is no change in amplitude.

*. If we want o/p for $(i/p < 0.6V)$ then we use op-amp with diode.

$$\text{So, } V_{out} = \frac{0.6}{A_{OL}} = \frac{0.6}{10^4} = 60\mu V.$$

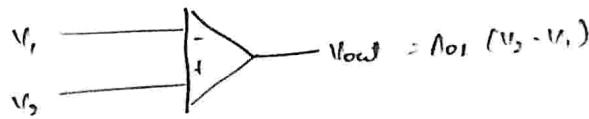*. Now at $60 \times 10^{-6} V$ the diode can





$$V_2 > V_1 = +V_{out}$$

$$V_2 < V_1 = -V_{out}$$


when, $V_i < 0$.

$$V_1 = -V_{sat}$$

The diode is off & reverse bias

$$V_o = 0$$

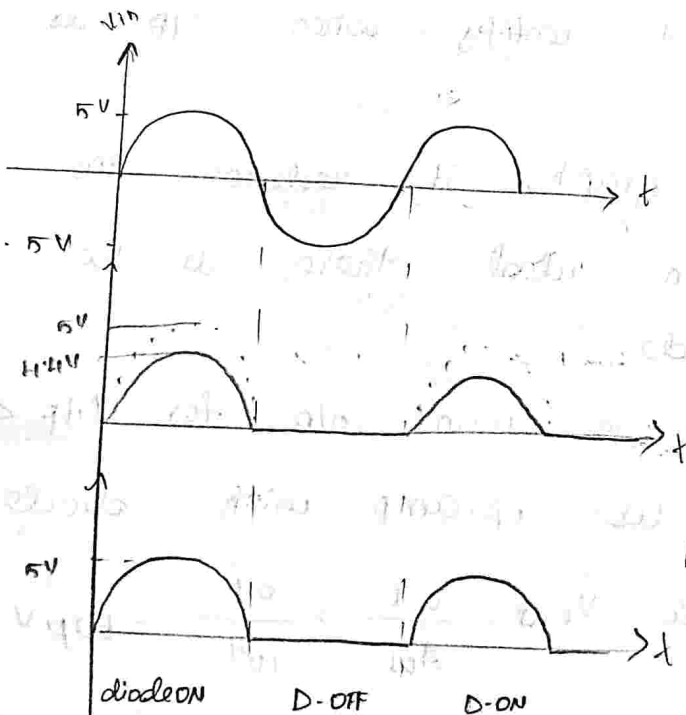in precision rectifier, it performs rectification with no drop voltage, in output.



Normal diode.

Precision rectifier.

Limitation:

It is only suitable to perform

realme 12x 5G

for low frequency

signal. [due to its slow rate it may not get o/p]



20 April 2026 at 12:16


$V_{in} \rightarrow$ during +ve half cycle.

$$V_o' = +V_{sat}.$$

$V_{in} \rightarrow$ during -ve half cycle.


$$V_o' = -V_{sat}.$$

Modified precision half wave rectifier.

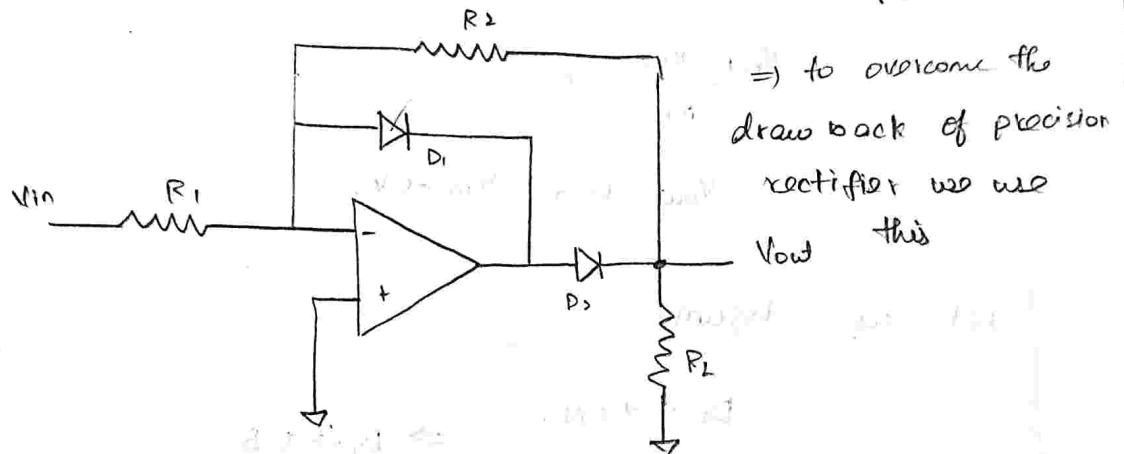

Let us assume, $D_1 \rightarrow$ ON, when $V_{in} > 0V$.

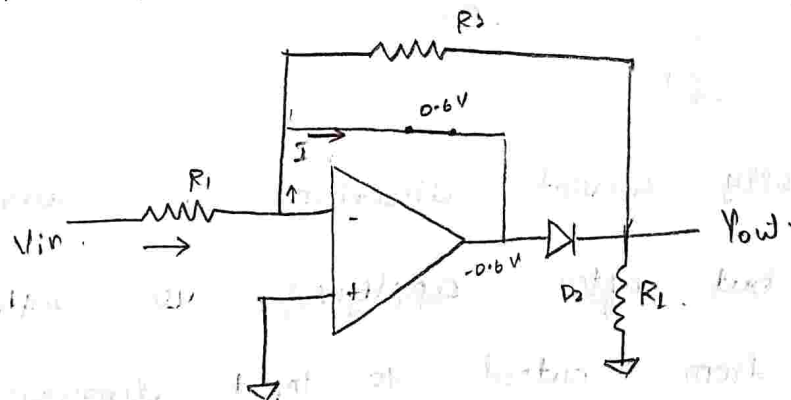D_1 & D_2 is not directly connected to o/p of op-amp.



$D_2 \rightarrow$ OFF [beoz -0.6V to the terminal connected


so Reverse bias occurs].

Due to virtual ground concept -ve terminal

The circuit, $V_{out} = 0$.



realme 12x 5G
20 April 2026 at 12:16

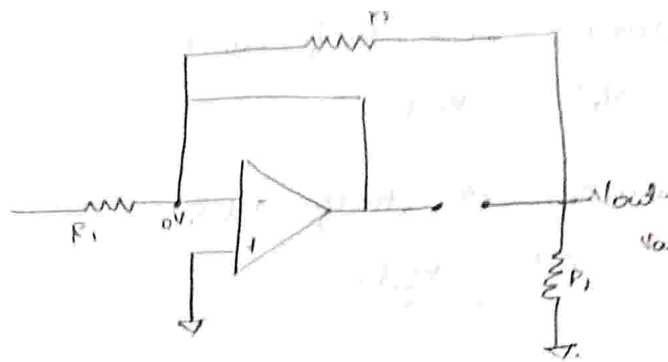


$$\frac{V_{out} - V_{in}}{R_2} = 0$$

$$V_{out} = 0, \quad V_{in} > 0V$$

Let us assume,

$$D_1 \rightarrow ON, \Rightarrow D_1 \rightarrow R.B$$

$$V_{in} = -10V$$

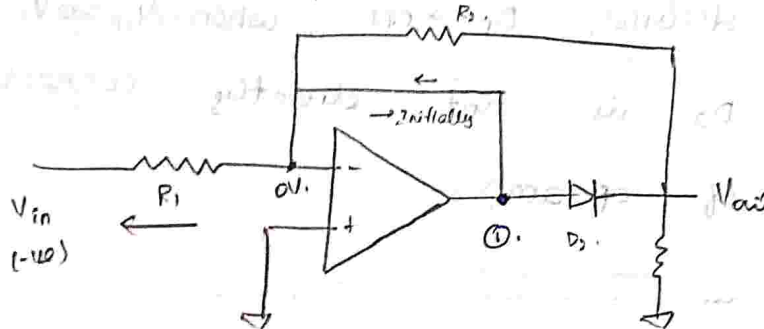

Initially current direction is towards V_{out}

D.F.B but after applying $-10V$ voltage

I flows from output to input direction,


direction changes, so D_1 is R.B, finally

$D_1 \rightarrow OFF$.

$\therefore$ Voltage at 1 is greater than $0V$ (th

so $+10V$ is connected to $+ve$ of D_2
 realme 12x 5G
 20 April 2026 at 12:16 $\rightarrow ON$.

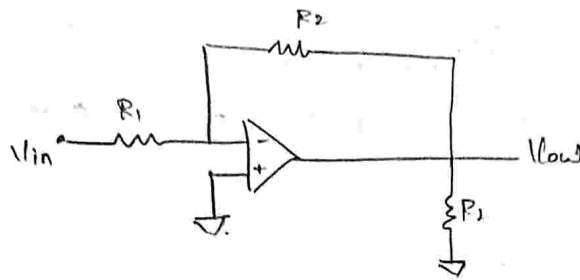
If $V_{in} = -10$, it is an inverting amplifier.



$$V_{out} = \left(-\frac{R_2}{R_1} \right) (-V_{in})$$


$$V_{out} = \frac{R_2}{R_1} V_{in}$$

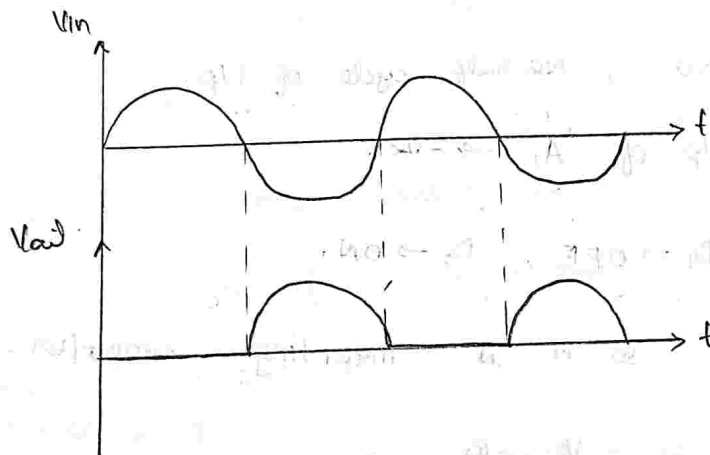Output of modified precision rectifier circuit.





* only +ve half cycle of circuit is rectified.

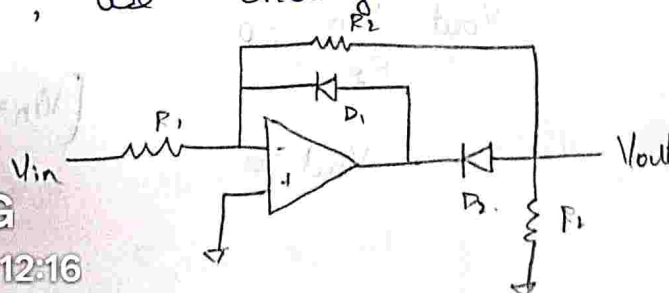* If we want to rectify -ve half cycle, we change the bias of D_1, D_2



(at rectifying $\odot$ -ve half cycle)

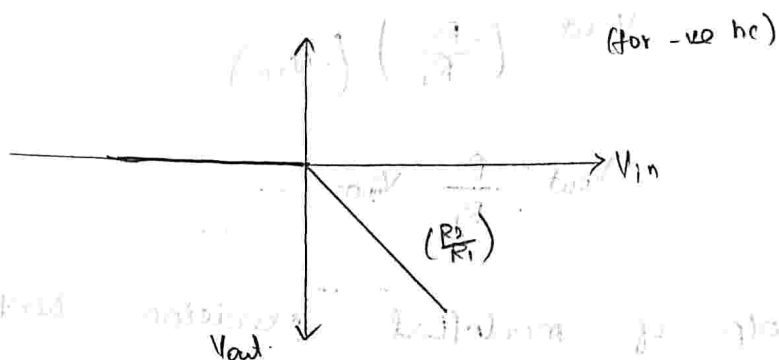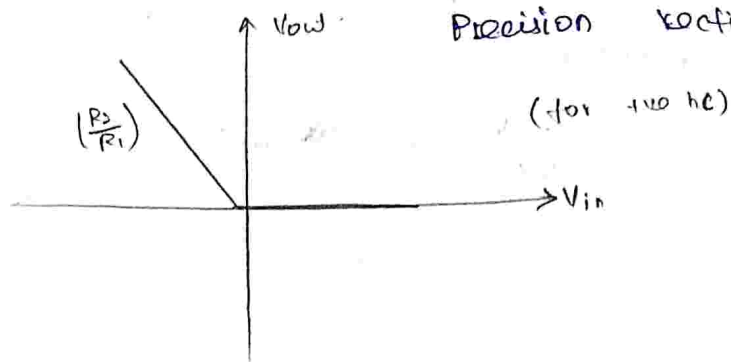Input & Output characteristics of Modified Precision Rectifier.



$V_{in} > 0$, +ve half cycle of i/p.

o/p of 'A' $\rightarrow$ -ve.

$D_1 \rightarrow$ OFF , $D_2 \rightarrow$ ON.

so it is inverting amplifier.

$$V_o = -\frac{R_2}{R_1} V_{in} .$$

It is rectified with amplitude $\frac{R_2}{R_1}$

$V_{in} < 0$, -ve half cycle of i/p.

o/p of 'A' $\rightarrow$ +ve.

$D_1 \rightarrow$ ON , $D_2 \rightarrow$ OFF.

$$\frac{V_{out} - V_{in}}{R_2} = 0 .$$

$$[V_{in} = 0]$$

$$V_{out} = 0 .$$



realme 12x 5G

20 April 2026 at 12:17

Modified
Precision Rectifier.

(for +ve half)

V_{in}


(for -ve half)

V_{in}


for.

Modified
amplitude $\frac{R_2}{R_1}$

$n=0$

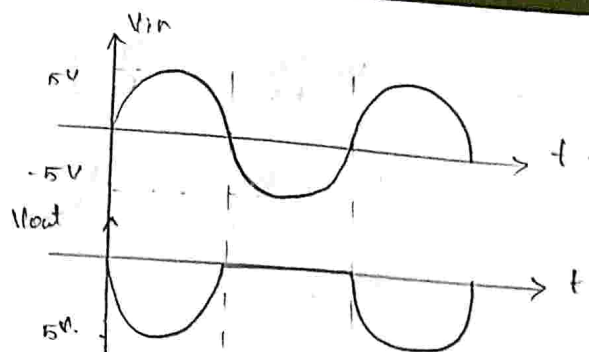

Full-wave Precision Rectifier.

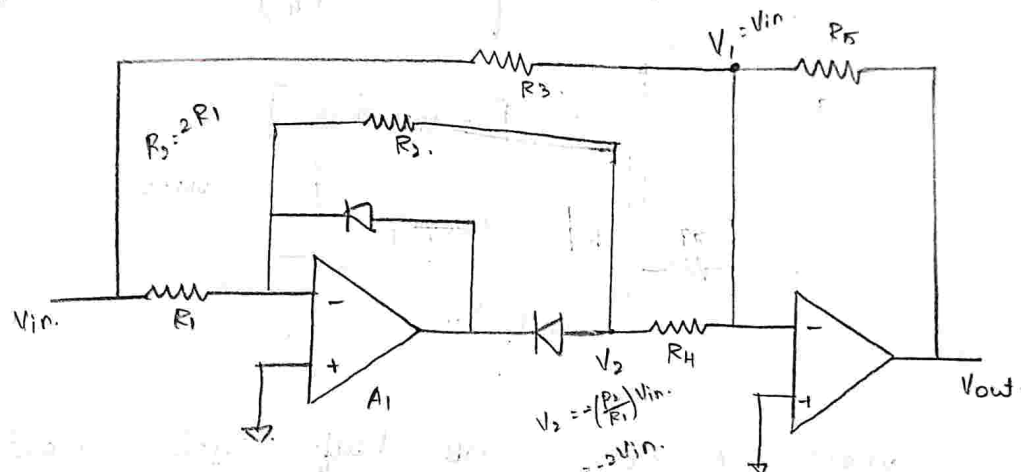

It is the combination modified
half-wave rectifier followed by inverting
summing amplifier.

when $V_{in} > 0$, [+ve half cycle i/p]

O/P of 'A1' $\rightarrow -V_O$.

$D_1 \rightarrow \text{OFF (R.B)}$

$D_2 \rightarrow \text{ON (F.B)}$.

$$V_O = V_2 = -\frac{R_2}{R_1} V_{in} \quad (-ve).$$

$$V_1 = V_{in} = +ve.$$

when, $V_1 = V_2$ with opp polarity.

$$R_3 = R_5 = R_4 = R.$$



realme 12x 5G

20 April 2026 at 12:17

$$V_{out} = - \left(V_1 \frac{R_5}{R_4} + V_2 \frac{R_5}{R_3} \right)$$

$$= - \left(-V_{in} \frac{R_5}{R_4} + V_{in} \frac{R_5}{R_3} \right)$$

$$= - (-V_{in} + V_{in})$$

$$(R_5 = R_4 = R_3 = R)$$

$$= 0$$

$$V_{out} = - \left[-2V_{in} \left(\frac{R_5}{R_4} \right) + V_{in} \left(\frac{R_5}{R_3} \right) \right]$$

$$= - [-2V_{in} + V_{in}]$$

$$= - (-V_{in})$$

$$\boxed{V_{out} = V_{in}}$$

when $V_{in} < 0$, -ve half cycle input.

o/p of 'A₁' → +ve.

D₁ → ON, D₂ → OFF


$$V_{out} = 0$$

$$\therefore V_2 = 0, V_1 = -V_{in}$$

$$V_o = - \left[V_2 \left(\frac{R_5}{R_4} \right) + V_1 \left(\frac{R_5}{R_3} \right) \right]$$

$$= - [0 - V_{in}]$$

$$V_o = +V_{in}$$

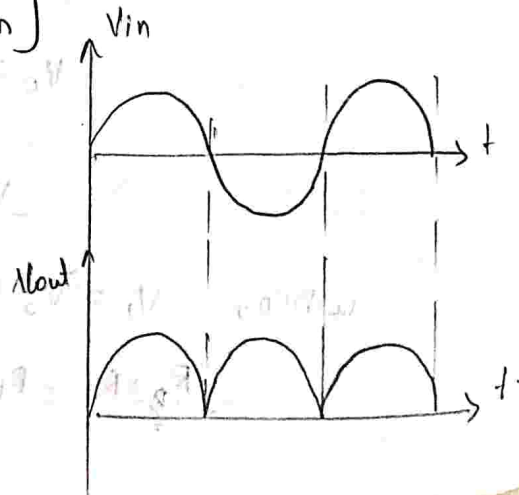


full wave
rectifier

realme 12x 5G

20 April 2026 at 12:17




Full-wave Precision Rectifier

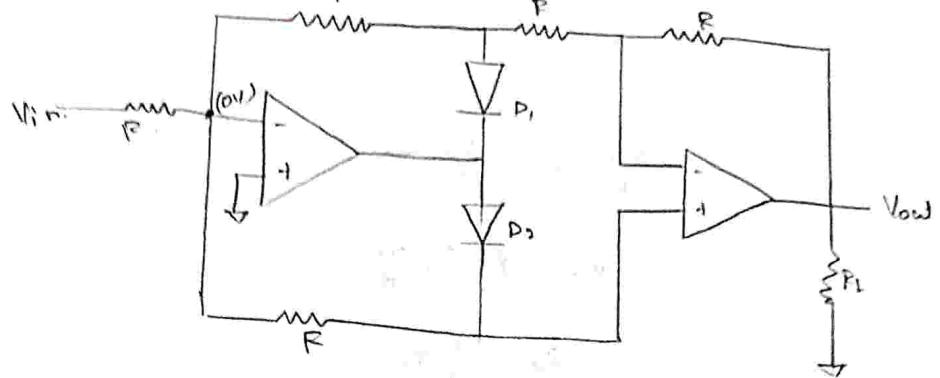

$V_{in} > 0$, +ve half cycle of i/p.

$D_1 \rightarrow \text{ON}$ (short circuit)

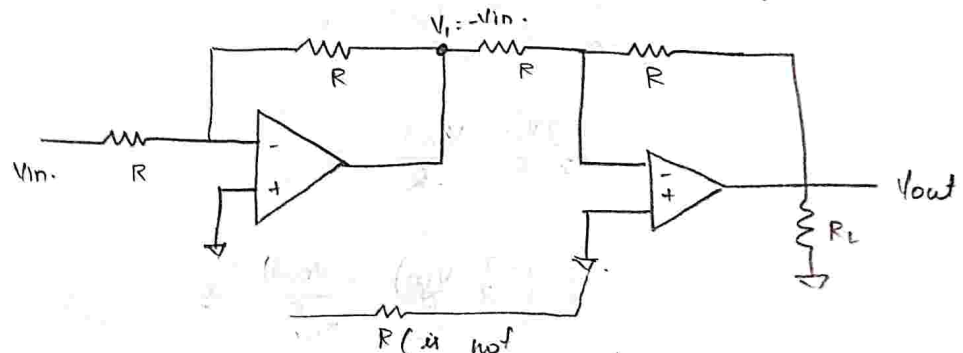$D_2 \rightarrow \text{OFF}$ (open circuit).



R is not considered due to o/p.


$$V_1 = V_{o1} = -V_{in}$$

$$V_{out} = -(-V_{in}) = V_{in}$$

$V_{in} < 0$, -ve half cycle of i/p.

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$.

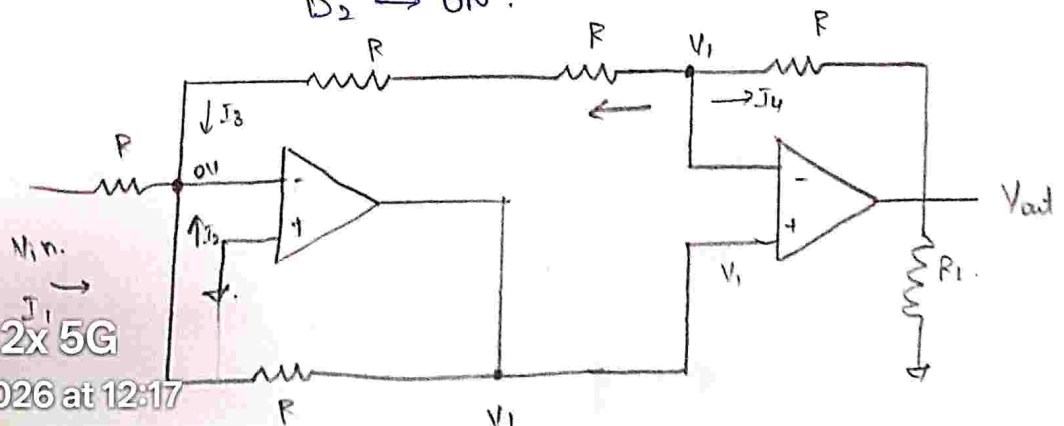

realme 12x 5G

20 April 2026 at 12:17

$$\frac{V_{in}-0}{R} + \frac{V_1-0}{R} + \frac{V_1}{2R} = 0.$$

$$\frac{V_{in}}{R} + \frac{3}{2} \frac{V_1}{R} = 0.$$

$$V_{in} = -\left(\frac{3}{2}\right) \frac{V_1}{R}.$$

$$V_{in} = -\frac{3}{2} V_1$$

$$V_1 = -\frac{2}{3} V_{in}.$$

$$I_3 + I_4 = 0.$$

$$\frac{V_1-0}{2R} + \frac{V_1-V_{out}}{R} = 0.$$

$$\frac{3V_1}{2R} - \frac{V_{out}}{R} = 0.$$

$$\frac{3}{2} \left(-\frac{2}{3} \frac{V_{in}}{R}\right) - \frac{V_{out}}{R} = 0.$$

$$-\frac{V_{in}}{R} = \frac{V_{out}}{R}$$


$$V_{out} = +V_{in}.$$



realme 12x 5G

20 April 2026 at 12:17

Logarithmic Amplifier

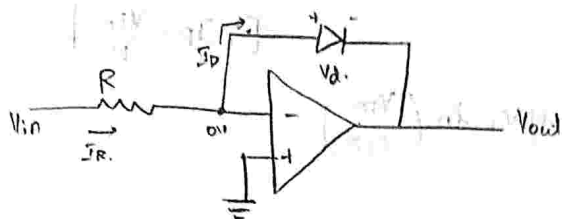

$I_s \rightarrow$ reverse saturation current

$I_D \rightarrow$ diode current

$V_D \rightarrow$ diode voltage

$V_T \rightarrow$ Volt equivalent temperature

diode current equation $I_D = I_s \left[e^{V_D / \eta V_T} - 1 \right]$

where,

$$V_T = \frac{kT}{q}$$

$k \rightarrow$ boltzman's constant $= 1.38 \times 10^{-23} \text{ J/K}$

$q \rightarrow 1.602 \times 10^{-19} \text{ C}$ [coulomb]

$T \rightarrow$ temperature.

$$V_T = \frac{kT}{q} \approx 26 \text{ mV at room temp } (25^\circ\text{C})$$

from the given circuit.

$$0 + V_D + V_{out} = 0$$

$$V_{out} = -V_D \rightarrow \textcircled{1}$$

From equ $\textcircled{1}$, $\frac{I_D}{I_s} = \left[e^{V_D / \eta V_T} - 1 \right]$

$$\frac{I_D}{I_s} + 1 = e^{V_D / \eta V_T}$$

$$\therefore \frac{I_D}{I_s} \gg 1, \text{ neglect } 1$$

$$\frac{I_D}{I_s} = e^{V_D / \eta V_T}$$

apply $\ln$ on b.s.

$$\frac{V_D}{\eta V_T} = \ln \left(\frac{I_D}{I_s} \right)$$



realme 12x 5G

20 April 2026 at 12:17

$$V_D = \eta V_T \ln \left(\frac{I_R}{I_S} \right)$$

$$[\because I_R = \frac{V_{in}}{R}]$$

$$V_D = \eta V_T \ln \left(\frac{V_{in}}{I_S R} \right)$$

from equ ②,

$$V_{out} = -V_D$$

$$V_{out} = -\eta V_T \ln \left(\frac{V_{in}}{I_S R} \right)$$


$\therefore$ output $\propto$ logarithm of V_{in}

V_{out} depends on η , we don't need this so we consider transistor base logarithm

op-amp.

drawback: presence of η , dependence of temperature parameter

Transistor Base Log - Amplifier:

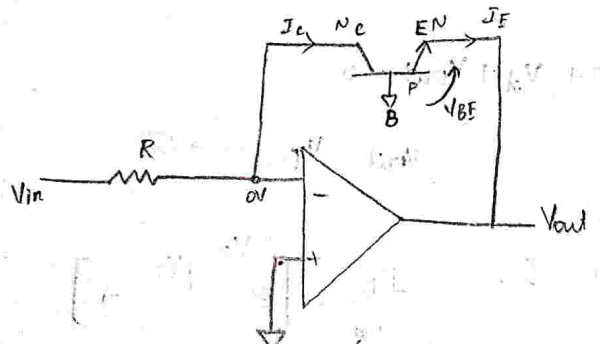

$$I_E = I_C + I_B \quad [\because \text{Base is grounded } I_B = 0]$$

$$I_E \approx I_C$$

collector current,

$$I_C = I_S \left[e^{V_E/V_T} - 1 \right] \rightarrow \textcircled{1}$$

from the circuit.

$$0 + V_E + V_{out} = 0$$

$$V_{out} = -V_E \rightarrow (1)$$

from eqn (1)

$$\frac{I_C}{I_S} = \left[e^{V_E/V_T} - 1 \right]$$


$$\frac{I_C}{I_S} + 1 = e^{V_E/V_T}$$

$\therefore \frac{I_C}{I_S} \gg 1$, 1 is neglected.

$$\frac{I_C}{I_S} = e^{V_E/V_T}$$

apply natural log on b.s.
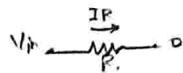
$$\frac{V_E}{V_T} = \ln \left(\frac{I_C}{I_S} \right)$$



$$\frac{V_E}{V_T} = \ln \left(\frac{I_R}{I_S} \right)$$

$$\left[\because I_R = \frac{V_{in}}{R} \right]$$

$$V_E = V_T \ln \left(\frac{V_{in}}{I_S R} \right) \rightarrow (2)$$

sub (2) in (1)

$$V_{out} = -V_T \ln \left(\frac{V_{in}}{I_S R} \right)$$

$$V_{out} = -\frac{kT}{q} \ln \left(\frac{V_{in}}{I_S R} \right)$$

Drawback:

Here, still V_{out} is dependent of

temperature.


realme 12x 5G

20 April 2026 at 12:17



Temperature compensated transistor

Based logarithmic Amplifier.

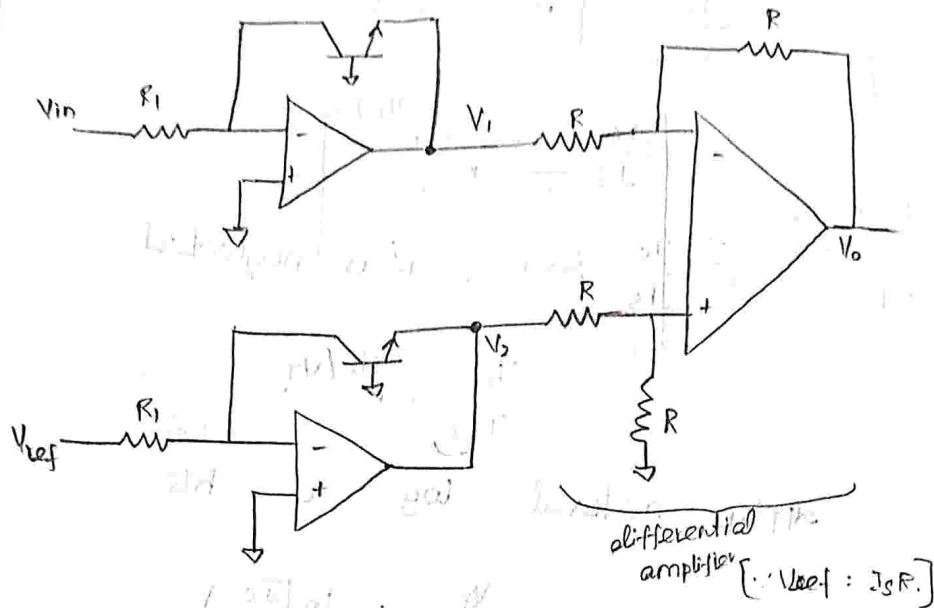

$$V_1 = -\frac{KT}{q} \ln \left[\frac{V_{in}}{I_S R_1} \right]$$

$$V_2 = -\frac{KT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right]$$

By differential amplifier we know,

$$V_0 = +\frac{R_2}{R_1} (V_2 - V_1)$$

$$\therefore V_{out} = \frac{R}{R} (V_2 - V_1)$$

$$V_{out} = -\frac{KT}{q} \ln \left(\frac{V_{ref}}{I_S R_1} \right) + \frac{KT}{q} \ln \left(\frac{V_{in}}{I_S R_1} \right)$$


$$V_{out} = \frac{KT}{q} \ln \left[\frac{V_{in}}{V_{ref}} \right]$$

In order to compensate the T

one more circuit, is non-inverting



amplifier.

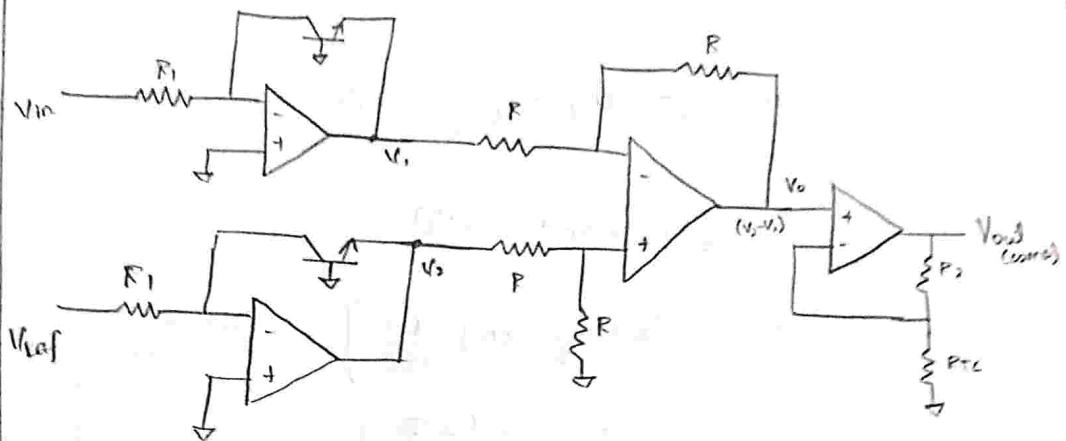


$R_{TC} \rightarrow$ temperature dependent resistor

$$V_{out (comp)} = \left(1 + \frac{R_2}{R_{TC}} \right) \frac{KT}{q} \ln \left[\frac{V_{in}}{V_{ref}} \right]$$

when $T \uparrow$ so R_{TC} also $\uparrow$ so both cancel each other, so temperature effect is cancelled.

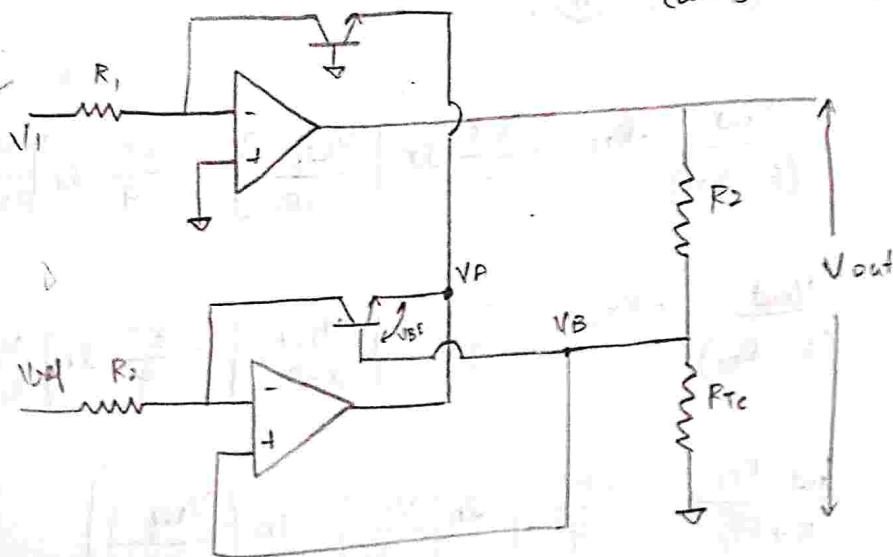Temperature compensated log-amplifier:
(using 2 log-amp).



V_A - collector terminal of Transistor 1 &
collector terminal of Transistor 2.

$$V_A = -\frac{kT}{q} \ln \left[\frac{V_1}{I_S R_1} \right] \rightarrow (1)$$

$$\therefore V_B - V_E = V_A \rightarrow (3)$$

$$\text{here, } V_E = \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] \Rightarrow \text{derived from transistor base log and it} \rightarrow (2)$$

sub (2) in (3).

$$V_B - \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] = -\frac{kT}{q} \ln \left[\frac{V_1}{I_S R_1} \right] \rightarrow (4)$$

here V_B = voltage across R_{TC}

By voltage divider theorem, $V_B = \frac{V_{out} R_{TC}}{(R_2 + R_{TC})}$

sub (4) in (5),

$$\frac{V_{out}}{(R_2 + R_{TC})} \cdot R_{TC} - \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] = -\frac{kT}{q} \ln \left[\frac{V_1}{I_S R_1} \right]$$

$$\frac{V_{out}}{(R_2 + R_{TC})} \cdot R_{TC} = \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] - \frac{kT}{q} \ln \left[\frac{V_1}{I_S R_1} \right]$$

$$\frac{V_{out} \cdot R_{TC}}{R_2 + R_{TC}} = \frac{-kT}{q} \left[\ln \left(\frac{V_1}{I_S R_1} \right) - \ln \left(\frac{V_{ref}}{I_S R_1} \right) \right]$$

V_B depends upon V_{out} .


$$V_{out} = \left(\frac{R_2 + R_{Te}}{R_{Te}} \right) \left(-\frac{kT}{q} \right) \ln \left[\frac{\frac{V_1}{I_S R_1}}{\frac{V_{ref}}{I_S R_1}} \right]$$

$$\therefore V_{out} = \left[1 + \frac{R_2}{R_{Te}} \right] \left(-\frac{kT}{q} \right) \ln \left(\frac{V_1}{V_{ref}} \right)$$

This is how we can design a temperature compensated log-amplifier using only two logarithmic op-amp.

eg: $\log(1000) = 3$
 $\text{antilog}(10^3) = 1000$

Anti-log amplifier:

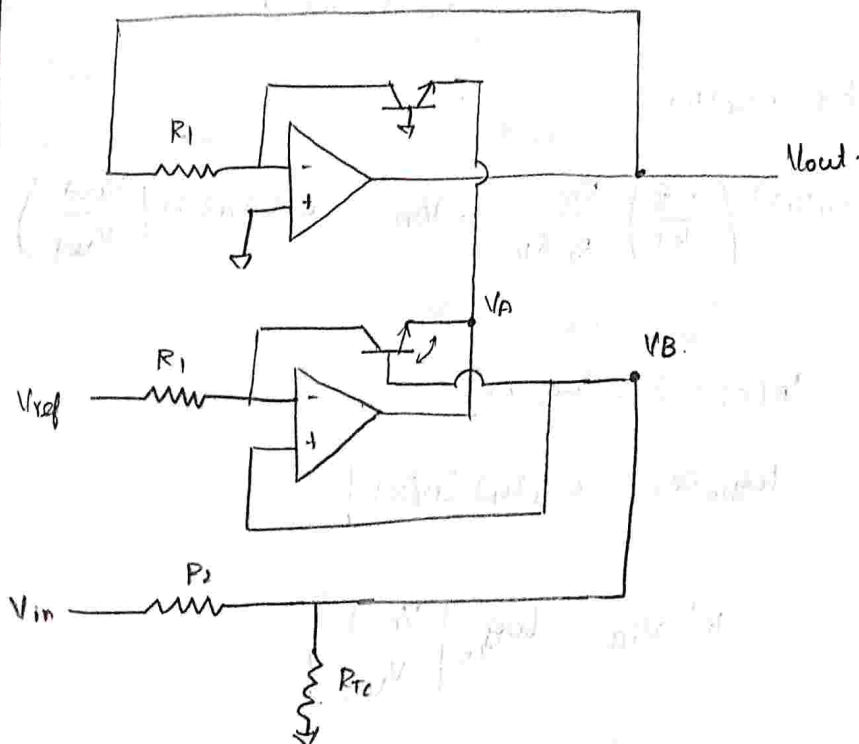

$$V_A = -\frac{kT}{q} \ln \left[\frac{V_{out}}{I_S R_1} \right] \rightarrow \text{①}$$

$$V_B - V_E = V_A$$

$$V_B - \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] = -\frac{kT}{q} \ln \left[\frac{V_{out}}{I_S R_1} \right]$$

$$\frac{V_{in} \cdot R_{Te}}{R_2 + R_{Te}} - \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] = -\frac{kT}{q} \ln \left[\frac{V_{out}}{I_S R_1} \right]$$

$$\frac{V_{in} \cdot R_{Te}}{R_2 + R_{Te}} = \frac{kT}{q} \ln \left[\frac{V_{ref}}{I_S R_1} \right] - \frac{kT}{q} \ln \left[\frac{V_{out}}{I_S R_1} \right]$$

$$\frac{V_{in} R_{Te}}{R_2 + R_{Te}} = -\frac{kT}{q} \left[\ln \left(\frac{V_{out}}{I_S R_1} \right) - \ln \left(\frac{V_{ref}}{I_S R_1} \right) \right]$$

$$\left(\frac{-q}{kT} \right) \left(\frac{R_{Te}}{R_2 + R_{Te}} \right) V_{in} = \ln \left(\frac{V_{out}}{V_{ref}} \right)$$

Wly by 0.4343,

$$(0.4343) \left(\frac{-q}{kT} \right) \frac{R_{Te}}{R_2 + R_{Te}} \cdot V_{in} = 0.4343 \ln \left(\frac{V_{out}}{V_{ref}} \right)$$

constants Replace by k'

$$\therefore \ln(x) = 2.3 \log_{10}(x)$$

$$\log_{10}(x) = 0.4343 \ln(x)$$

$$-k' V_{in} = \log_{10} \left[\frac{V_{out}}{V_{ref}} \right]$$

$$\therefore \frac{V_{out}}{V_{ref}} = 10^{-k' V_{in}}$$

$$\therefore V_{out} = V_{ref} 10^{-k' V_{in}}$$

$$\therefore V_{out} = V_{ref} 10^{-k' V_{in}}$$



realme 12x 5G


20 April 2026 at 12:17

eg: If $k' = V_{in} = 1$, then.

$$V_{out} = \frac{V_{ref}}{10}$$

V_{ref} ↓ by 10 times.

COMPARATOR:

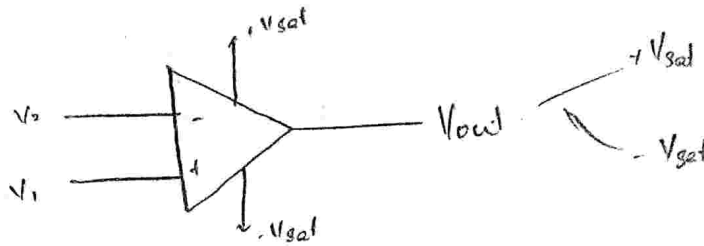

$$V_{out} = A_{OL} (V_1 - V_2) \quad [\because \text{If } (V_1 - V_2) \text{ is small}]$$


$$= +V_{sat} \text{ (or)} -V_{sat} \quad \text{due } A_{OL} (10^6) \text{ we get this}$$

It compares two terminal voltage, higher voltage terminal, the o/p goes to corresponding V_{sat} .


when, $V_1 > V_2$, o/p: $+V_{sat}$

$V_2 > V_1$, o/p: $-V_{sat}$.

Inverting mode comparator:

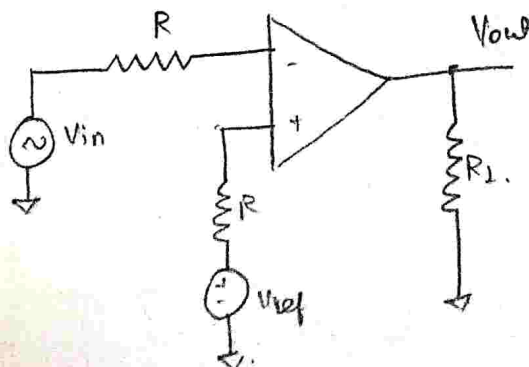

Assume, $V_{ref} = 2V$.

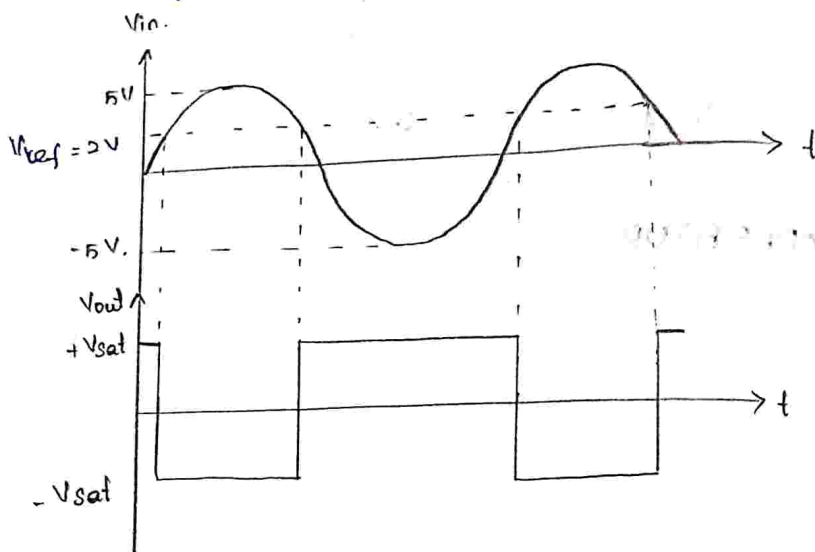

when, $V_{in} < 2V$, $V_{out} = +V_{sat}$;

$$(V_- < V_+)$$


when, $V_{in} > 2V$, $V_{out} = -V_{sat}$.

$$(V_- > V_+)$$


Assume, $V_{ref} = -2V$.

when, $V_{in} > -2V$, $V_o = -V_{sat}$.


$V_{in} < -2V$, $V_o = +V_{sat}$

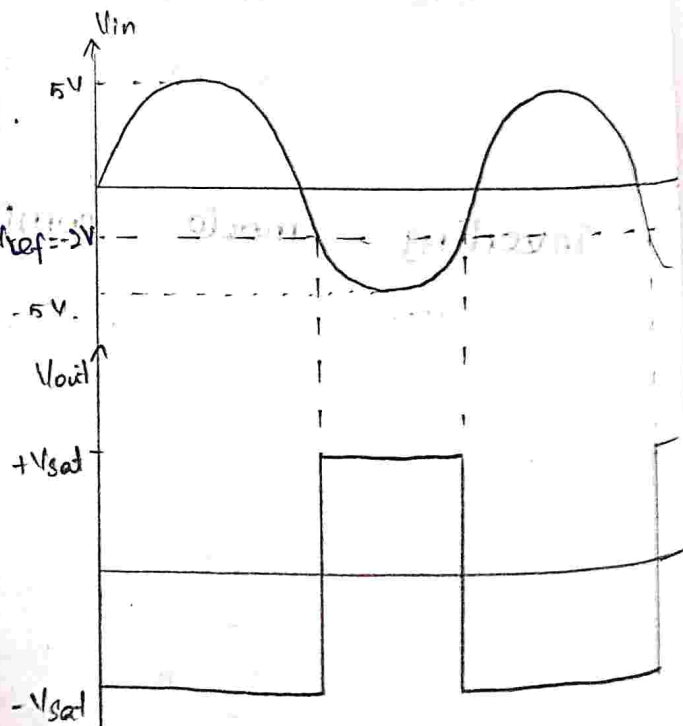

Non-Inver

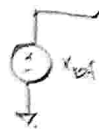

Assume,

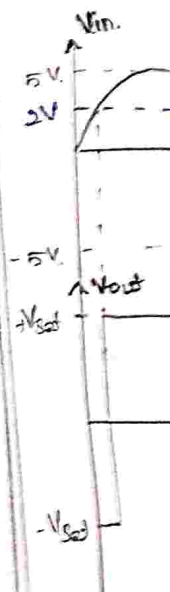

Assume

$V_{ref} = -2V$

$-5V$

$+V_{sat}$


$-V_{sat}$




realme 12x 5G

20 April 2026 at 12:17

Non-Inverting Mode comparator.

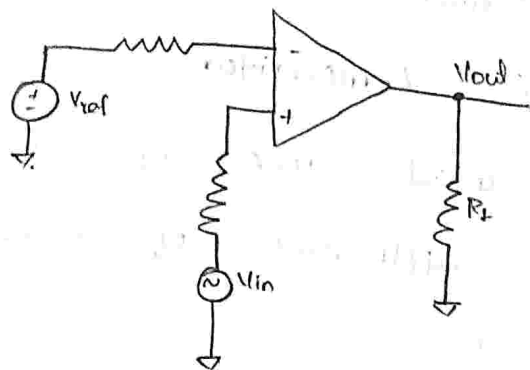

assume, $V_{ref} = 2V$.

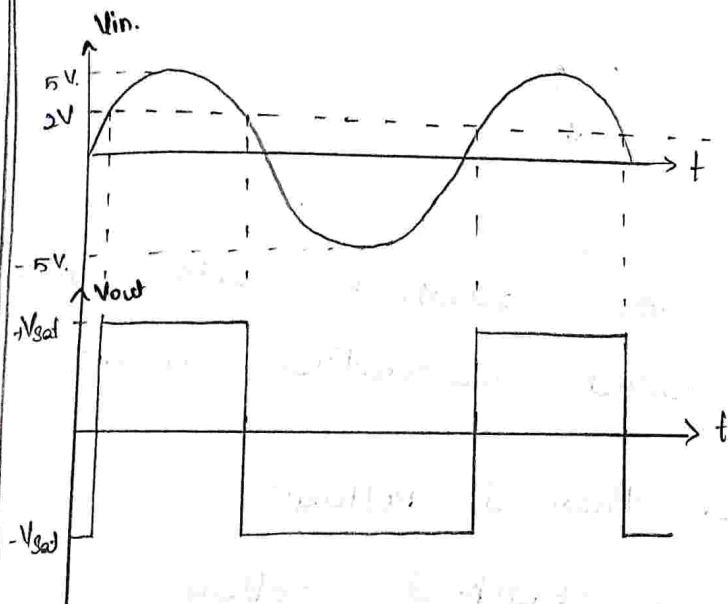


$$V_{in} < 2V \Rightarrow V_{out} = -V_{sat}$$

$$V_+ < V_-$$

$$V_{in} > 2V \Rightarrow V_{out} = +V_{sat}$$

$$V_+ > V_-$$

assume, $V_{ref} = -2V$.

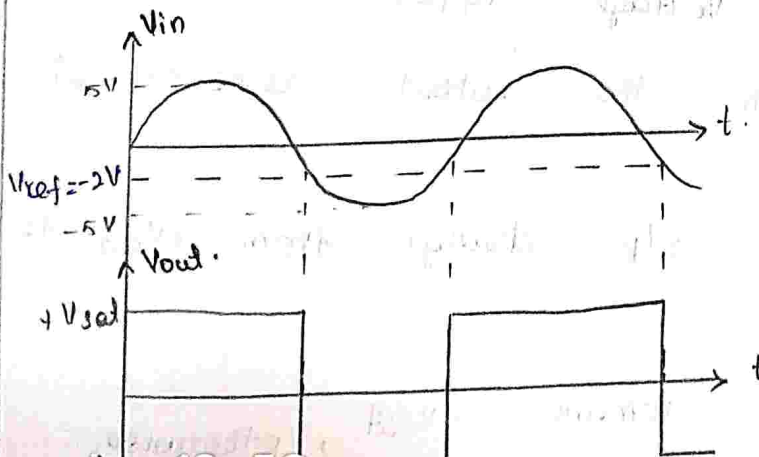

$$V_{in} > -2V \Rightarrow V_o = +V_{sat}$$

$$V_{in} < -2V \Rightarrow V_o = -V_{sat}$$

$$V_+ > V_-$$


If we keep $V_{ref} = 0V$ then it is zero-crossing integrator circuit.

Regenerative Comparator:

⇒ Using closed loop op-amp.

⇒ It is application of comparator.

[also called as schmitt trigger]

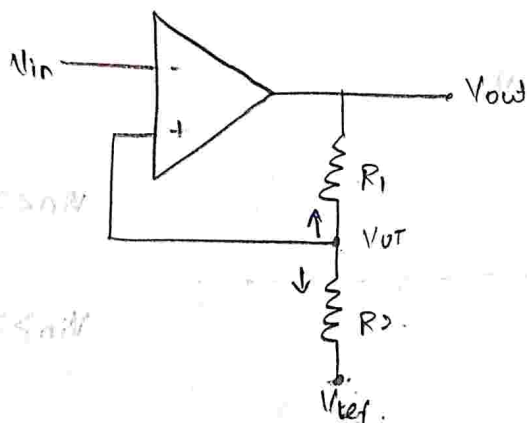

whenever the feedback exist in the circuit is called regenerative circuit.

$V_{UT} \rightarrow$ upper threshold voltage.

$V_{LT} \rightarrow$ lower threshold voltage.

$V_{UT} \Rightarrow$ Max Voltage appear at Non-inverting, (upto which the output remains at V_{sat})

(or)
[when the o/p change from $+V_{sat}$ to $-V_{sat}$]

$V_{LT} \Rightarrow$ output remains $-V_{sat}$, $V_{in} < V_{LT}$, otherwise



Minimum voltage, It remains $-V_{sat}$, otherwise the o/p transition from $-V_{sat}$ to $+V_{sat}$.

[Draw back of using open loop op-amp:

$\Rightarrow$ It has one threshold voltage]

$\Rightarrow$ o/p depends upon multiple threshold voltage [here we use 2].


when the i/p lies b/w V_{UT} & V_{LT} the o/p simply maintains go its previous

value. $\rightarrow$ hysteresis value.

$V_{UT} \rightarrow$ is a point max voltage at which the o/p change from $+V_{sat}$ to $-V_{sat}$.

$V_{LT} \rightarrow$ Max voltage at which o/p changes

from $-V_{sat}$ to $+V_{sat}$.

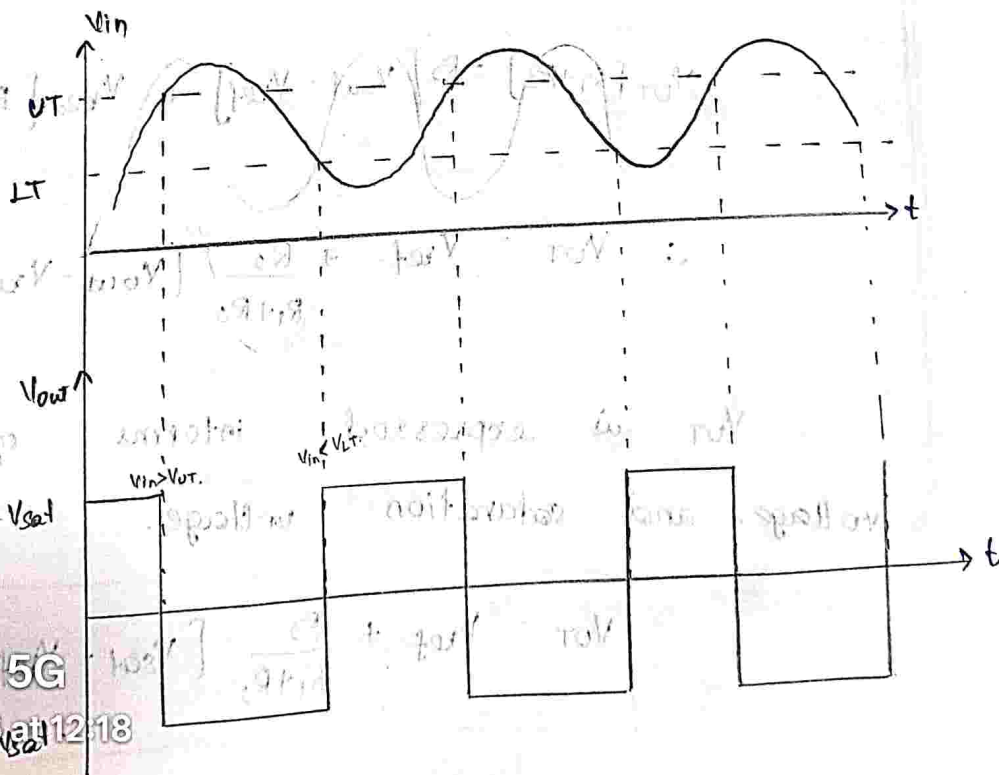

when, $V_{out} = +V_{sat}$, $V_{UT} = V_{UT}$

apply nodal analysis, w.r.t. " V_{UT} "

$$\frac{V_{UT} - V_{out}}{R_1} + \frac{V_{UT} - V_{ref}}{R_2} = 0$$

$$V_{UT} \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_{out}}{R_1} - \frac{V_{ref}}{R_2} = 0$$

$$V_{UT} \left[\frac{R_1 + R_2}{R_1 R_2} \right] = \frac{V_{out}}{R_1} + \frac{V_{ref}}{R_2}$$

$$V_{UT} [R_1 + R_2] = R_1 R_2 \left[\frac{V_{out}}{R_1} + \frac{V_{ref}}{R_2} \right]$$

$$V_{UT} [R_1 + R_2] = R_2 V_{out} + R_1 V_{ref}$$

add & sub by $R_2 V_{ref}$

$$V_{UT} [R_1 + R_2] = R_2 V_{out} + R_1 V_{ref} + R_2 V_{ref} - R_2 V_{ref}$$

$$V_{UT} [R_1 + R_2] = \frac{R_2 [V_{out} - V_{ref}]}{R_1 + R_2} + \frac{V_{ref} [R_1 + R_2]}{R_1 + R_2}$$

$$\therefore V_{UT} = V_{ref} + \frac{R_2}{R_1 + R_2} [V_{out} - V_{ref}]$$

V_{UT} is expressed in terms of reference voltage and saturation voltage.

realme 12x 5G

20 April 2026 at 12:18

$$V_{UT} = V_{ref} + \frac{R_2}{R_1 + R_2} [V_{sat} - V_{ref}]$$

when, $V_{out} = -V_{sat}$, $V_+ = V_{LT}$

$$\frac{V_{out} - V_{LT}}{R_1} + \frac{V_{ref} - V_{LT}}{R_2} = 0$$

apply nodal analysis w.r.to V_{LT} .

$$\frac{V_{LT} - V_{out}}{R_1} + \frac{V_{LT} - V_{ref}}{R_2} = 0$$

$$\frac{V_{LT} + V_{sat}}{R_1} + \frac{V_{LT} - V_{ref}}{R_2} = 0$$

$$V_{LT} \left[\frac{R_1 + R_2}{R_1 R_2} \right] = \frac{-V_{sat}}{R_1} + \frac{V_{ref}}{R_2}$$

xy by $R_1 R_2$:

$$V_{LT} [R_1 + R_2] = -R_2 V_{sat} + R_1 V_{ref} + R_2 V_{ref}$$

$$V_{LT} [R_1 + R_2] = -R_2 [V_{sat} + V_{ref}] + V_{ref} [R_1 + R_2]$$

$$V_{LT} = \frac{-R_2}{R_1 + R_2} [V_{sat} + V_{ref}] + \frac{V_{ref} [R_1 + R_2]}{R_1 + R_2}$$

$$\therefore V_{LT} = V_{ref} - \frac{R_2}{R_1 + R_2} [V_{sat} + V_{ref}]$$

Hysteresis Voltage:

$$V_H = V_{UT} - V_{LT}$$

$$= \cancel{V_{ref}} + \frac{R_2}{R_1 + R_2} [V_{sat} - V_{ref}] - \cancel{V_{ref}} + \frac{R_2}{R_1 + R_2} (V_{sat} + V_{ref})$$

$$= \frac{R_2}{R_1 + R_2} [V_{sat} - \cancel{V_{ref}} + V_{sat} + \cancel{V_{ref}}]$$

$$V_H = \frac{2 R_2}{R_1 + R_2} (V_{sat})$$





Advantage:


1. Noise immunity offered by regenerative comparator is high.
2. Switch speed is more.
3. Stability is more.

Application:

1. Time marker generative circuit.

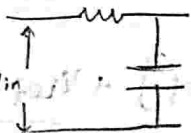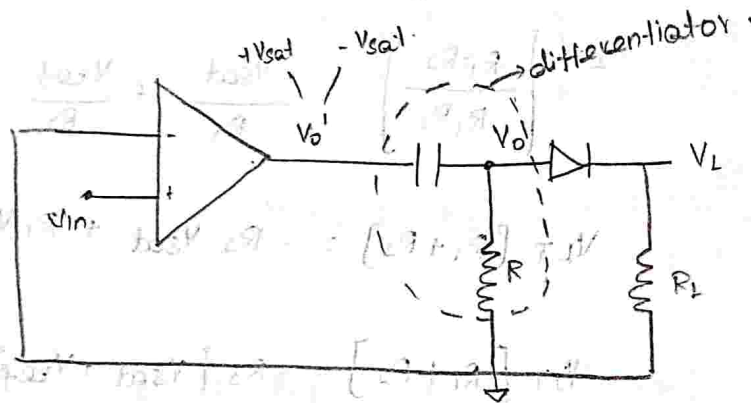

passive low pass filter
[integrator]

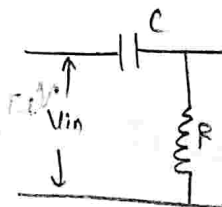

[differentiator]

$$V_o = +V_{sat} \quad D \rightarrow ON$$

$$V_o = -V_{sat} \quad D \rightarrow OFF$$

MULT-VIBRATORS:

Types of multivibrators.

1. Astable $\rightarrow$ No stable states / both are quasi stable states.
2. Monostable $\rightarrow$ 1 stable state & 1 quasi stable state.
3. Bistable $\rightarrow$ 2 stable states.

Astable $\Rightarrow$ no need to apply external inp pulse to change its o/p states.

eg: oscillator, Relaxation oscillator.

- also called Free-Running multivibrator.

Monostable $\Rightarrow$ it requires -ve trigger pulse to change o/p from stable to quasi-stable state.


- also called one-shot multivibrator.

Bistable $\Rightarrow$ It requires two trigger pulse


- also called binary circuit bcoz it has

2 stable state.

Astable Multivibrator!

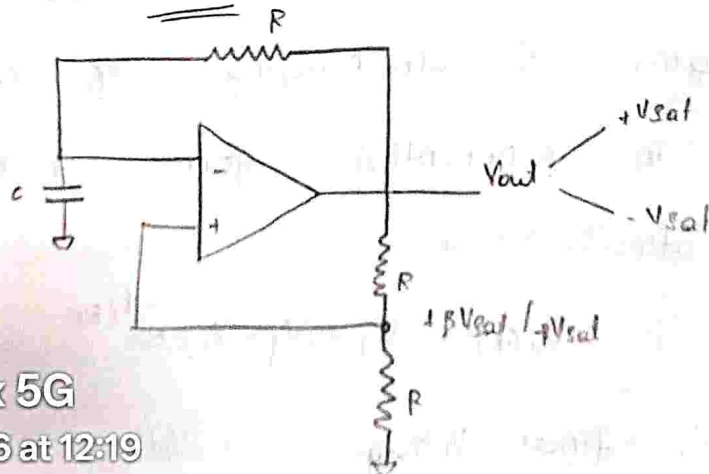

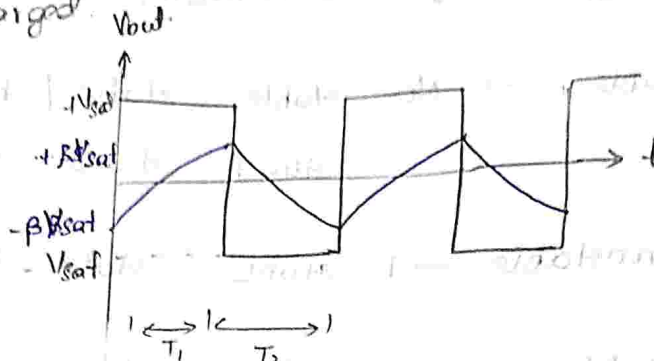→ Based on o/p the capacitor charged & discharged.



→ o/p voltage depends upon threshold

voltage & charging / discharging of capacitor.

→ Initially Assume, $V_o = +V_{sat}$, voltage at the terminal $+βV_{sat}$.

→ Capacitor → charged beyond $β$ voltage charge $V_o > V_1$ then output is $-V_{sat}$.

Assume, $V_o = -V_{sat}$.

$V_1 = -βV_{sat}$.

$C \rightarrow$ discharge upto $-βV_{sat}$ when it goes lower than $-βV_{sat}$.

$V_o < V_1$ then the o/p is $+V_{sat}$.

charging & discharging of capacitor occur in exponential form, which is mathematically as.

$$V_c(t) = V_f - (V_f - V_i) e^{-t/RC}.$$

realme 12x 5G

20 April 2026 at 13:19

$V_i \rightarrow$ initial voltage.



(Max voltage 'c' can be charged is V_{sat}).

T_1 — time period when capacitor charged exponentially

T_2 — time period when capacitor discharged exponentially.

By Mathematical,

$$V_c(t) = V_{sat} - (V_{sat} - (-\beta V_{sat})) e^{-t/RC}$$

$$V_c(t) = V_{sat} - (V_{sat} + \beta V_{sat}) e^{-t/RC}$$

$$\text{at } t = T_1, V_c(t) = +\beta V_{sat}.$$

$$+\beta V_{sat} = V_{sat} - (V_{sat} + \beta V_{sat}) e^{-T_1/RC}.$$

$$\beta V_{sat} - V_{sat} = -(V_{sat} + \beta V_{sat}) e^{-T_1/RC}.$$

$$+V_{sat} (1 - \beta) = +V_{sat} (1 + \beta) e^{-T_1/RC}.$$

$$\frac{1 - \beta}{1 + \beta} = e^{-T_1/RC}.$$

Apply $\ln$ on B.S,

$$-T_1/RC = \ln \left(\frac{1 - \beta}{1 + \beta} \right)$$

$$\frac{T_1}{RC} = -\ln \left(\frac{1 - \beta}{1 + \beta} \right)$$

$$\therefore T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

Capacitor required same time for

charging & discharging.



If o/p is symmetrical,

$$T = T_1 + T_2 = 2T_1$$

$$T = 2RC \ln \left(\frac{1+\beta}{1-\beta} \right)$$

$\therefore$ Time period depends on R, C & β .

If we don't want V_{sat} in o/p we can use clipping circuit by zener diode.

Connected (1 by 1 zener diode) in V_{out} , it limits the amplitude.

$$\beta = \frac{R_2}{R_1 + R_2}$$

If $R_1 = R_2$.

$$\beta = \frac{R_1}{2R_1} = \frac{1}{2} = 0.5$$

$$T = 2RC \ln \left[\frac{1+0.5}{1-0.5} \right] \Rightarrow T = 2RC \ln [3]$$

If $R_1 = 1.16R_2$.

$$\beta = \frac{R_2}{1.16R_2 + R_2} = \frac{1}{2.16} = 0.463$$

$$T = 2RC \ln \left[\frac{1+0.463}{1-0.463} \right] = 2RC \ln [2.724]$$

$$T = 2RC (1.000)$$



realme 12x 5G

20 April 2026 at 12:19

R, C & R.

o/p

zener

o) in

high

3]

4]

$$T_s = 2RC.$$


In this case time period is completely depends on external R, C.

$$\therefore f_o = \frac{1}{T} = \frac{1}{2RC}.$$

It is a symmetrical square wave generator circuit.

symmetric - on & off time is same.

For asymmetry square wave:

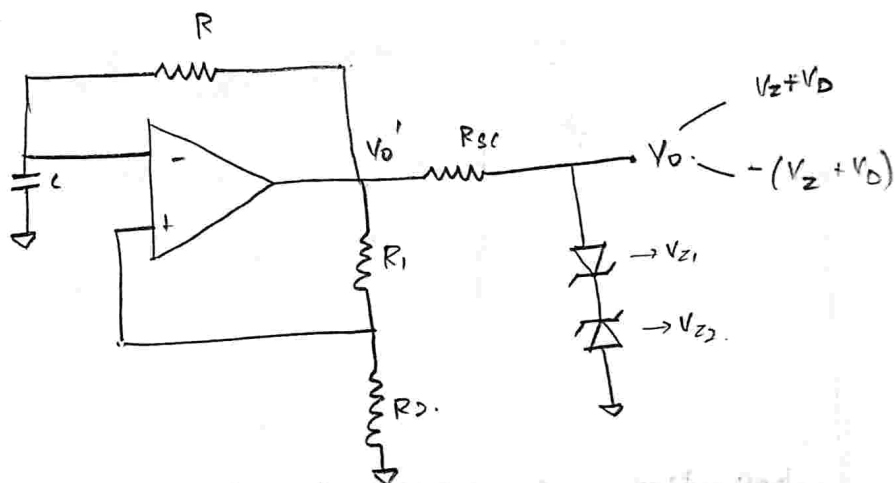

I am going to fix V_o value by taking zener diode back to back. standard voltage of zener diode $\approx 5.6V$.

$R_{sc} \rightarrow$ current limiting resistor in order to prevent the breakdown of zener by allowing excessive

current in R.B).




By connecting zener diode we can able to fix voltage $(V_z + V_D)$ or $-(V_z + V_D)$ rather than $+V_{sat}$, $-V_{sat}$.

$$I = \frac{V_{out} - V_z}{R_{sc}} \quad V_z \rightarrow \text{breakdown voltage}$$

$V_{z1} = V_{z2} \Rightarrow$ generate symmetric square wave.

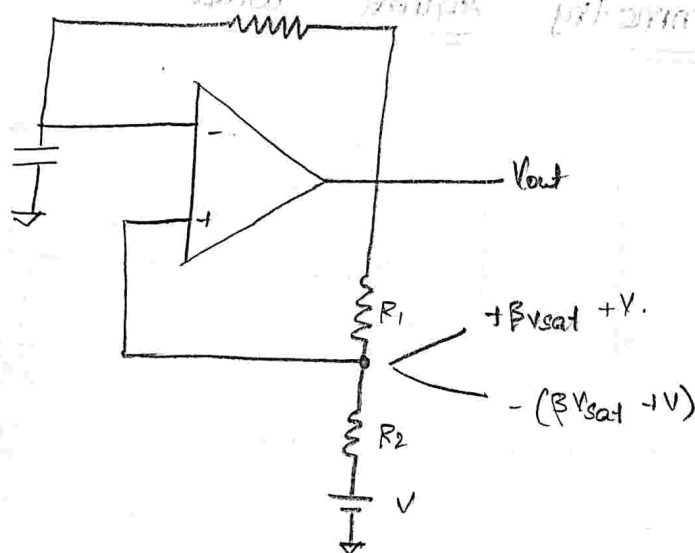$V_{z1} \neq V_{z2} \Rightarrow$ generate asymmetric "square" asymmetric square wave generator.



[Application of Astable:

*. Voltage to frequency converter.]

$\Rightarrow$ We can control the frequency

by changing the dc voltage.

realme 12x 5Gp of astable depends on

20 April 2026 at 12:19

external dc supply.



Design a square wave oscillator for $f_0 = 1 \text{ kHz}$ using an ICH1 op-amp and dc supply voltage of $\pm 12 \text{ V}$

Sol:

Given, $f_0 = 1 \text{ kHz}$.

Design a symmetric square wave.

$$f_0 = \frac{1}{2RC}$$

$$R_1 = 1.16 R_2$$

$$\text{Let } R_2 = 10 \text{ k}\Omega$$

$$\text{Therefore } R_1 = 11.6 \text{ k}\Omega$$

$$f_0 = \frac{1}{2RC} = 1 \text{ kHz} \quad (10)$$


let us choose, $C = 1 \mu\text{F}$.

$$\frac{1}{2 \times 10^{-6} \times 10^{-3}} = R$$

$$\frac{1}{2 \times 10^{-3}} = R$$

$$R = 0.5 \text{ k}\Omega$$

$$R = 500 \Omega$$

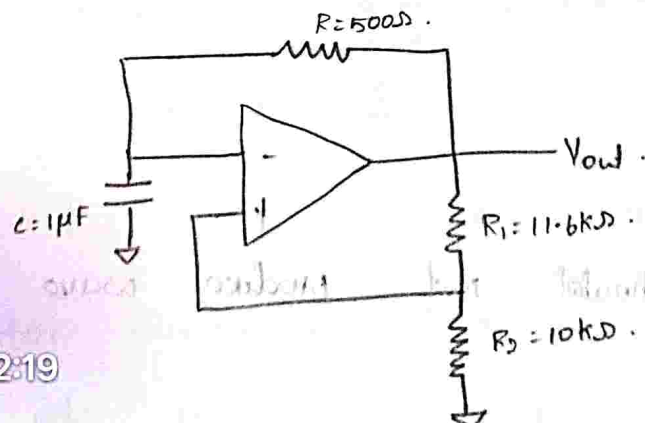

MONOSTABLE

MULTIVIBRATOR:

1. It has 1 stable state & 1 quasi stable state.


⇒ quasi stable state → Non-permanent state

2. It requires 1 triggering pulse extremely. (to change state of o/p)

3. It is called 1-shot multi-vibrator.

4. Gating circuits - It can generate a pulse (or) square wave in specified time period (fixed time period).

5. Time delay circuit.

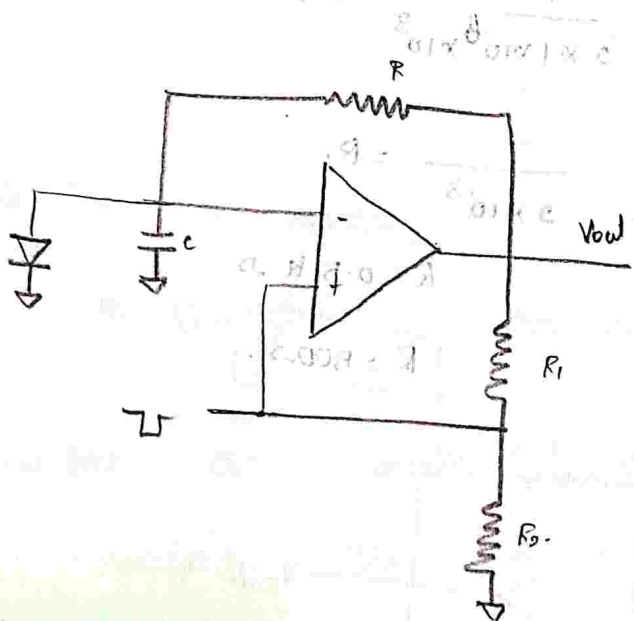

It should not produce wave form

continuously.



20 April 2026 at 12:19

By placing the diode in parallel to capacitor, when $0.7V$ the capacitor stop charging (so that it doesn't produce continuous).

→ $V_{out} = +V_{sat}$. (Before applying -ve trigger)

The voltage at capacitor fixed at ' V_0 '
 $\downarrow$
 $0.7V$.

Now, I need to apply with suitable amplitude. (giving -ve max voltage.)

eg: $-4.00V < 0.00$
 $\downarrow$
 -ve trigger pulse.
 $\downarrow$
 Inverting terminal voltage.

[trigger → short duration pulse]

∴ Inverting terminal > Non-Inverting

voltage, the $[o/p \rightarrow -V_{sat}]$

⇒ Now capacitor start discharge upto $-V_{sat}$.

⇒ when it goes below $-V_{sat}$,

$V_- < V_+$ (-ve trigger) like $(-5.00V < -4.00V)$,
 V_- V_+ (-ve trigger)


$o/p \rightarrow +V_{sat}$

⇒ due to parallel connection of diode,

capacitor discharge linearly.

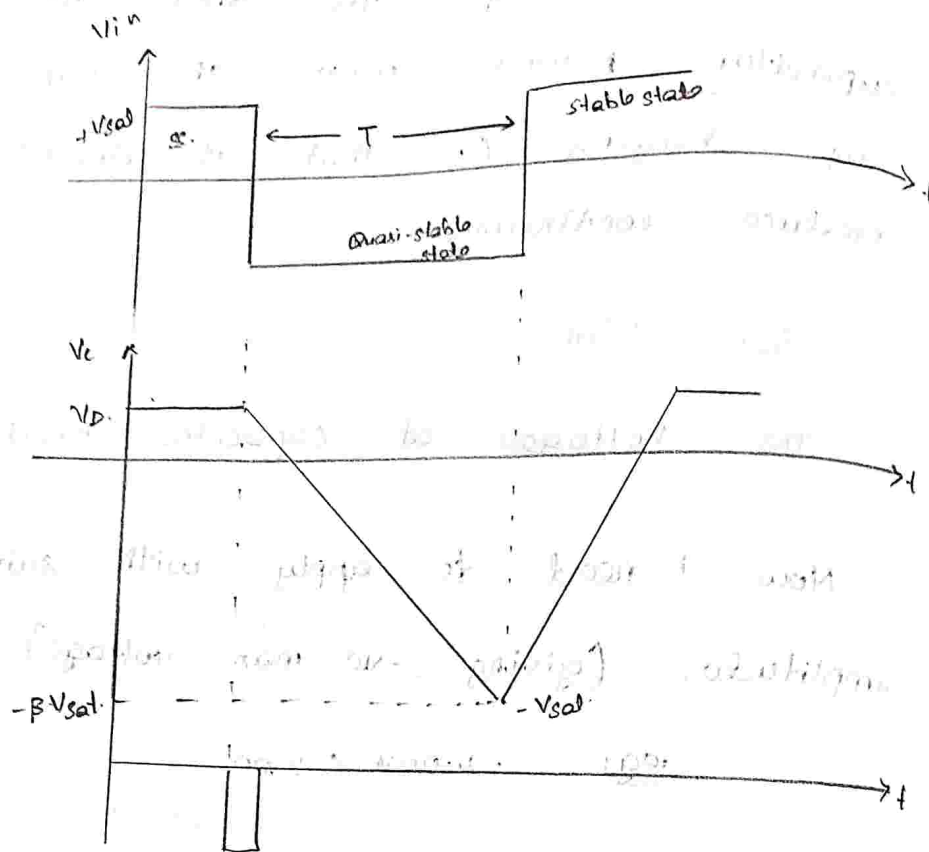after it charge upto $+V_{sat}$, but due to diode charge upto $0.7V$ after that remains V_0 .






$$V_o(t) = V_f - (V_f - V_i) e^{-t/RC}$$

$$V_o(t) = -V_{sat} - (-V_{sat} - V_D) e^{-t/RC}$$
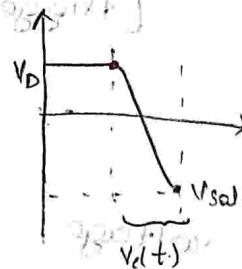
$$\Rightarrow [\because V_o(t) = -\beta V_{sat}, \text{ at } t=T.]$$



$$-\beta V_{sat} = -V_{sat} - [-V_{sat} - V_D] e^{-T/RC}$$

$$-\beta V_{sat} + V_{sat} = [V_{sat} + V_D] e^{-T/RC}$$

$$\frac{V_{sat} [1 - \beta]}{V_{sat} + V_D} = e^{-T/RC}$$

$$e^{-T/RC} = \left[\frac{1 - \beta}{1 + \frac{V_D}{V_{sat}}} \right]$$



$$\tau_{RC} = \frac{1 + \frac{V_D}{V_{sat}}}{1 - \beta}$$

take $\ln$ on b/s,

$$\frac{T}{RC} = \ln \left(\frac{1 + \frac{V_D}{V_{sat}}}{1 - \beta} \right)$$

$$T = RC \ln \left(\frac{1 + \frac{V_D}{V_{sat}}}{1 - \beta} \right)$$

$\therefore V_D \rightarrow$ diode drop. (less = 0.7V).

$V_{sat} \rightarrow$ very high

When $V_D < V_{sat}$, $\frac{V_D}{V_{sat}} \ll 1$, so it is neglected.

$$T = RC \ln \left[\frac{1}{1 - \beta} \right], \text{ here } \beta = \frac{R_2}{R_1 + R_2}$$

if $R_1 = R_2$.

$$\beta = \frac{R_2}{2R_2} = 0.5$$

$$T = RC \ln \left[\frac{1}{1 - 0.5} \right] = RC \ln \left[\frac{1}{0.5} \right]$$

$$T = RC \ln(2)$$

$$\textcircled{X} \quad \boxed{T = 0.693 RC}$$


By choosing RC we can determine

real time 5G a pulse of T .

20 April 2026 at 12:20



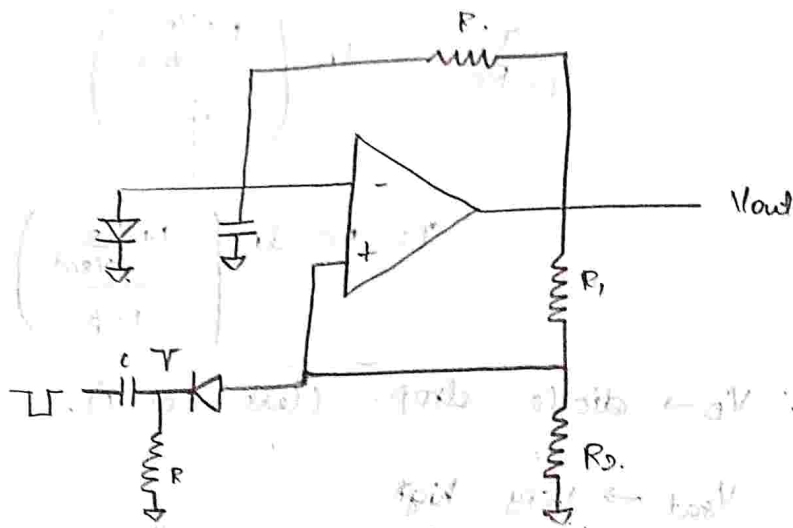diode is connected to ensure the
-ve trigger is applied, when the
trigger apply diode become OFF.



Q. Design a monostable multivibrator with
trigger pulse shaping which will drive a
LED ON for 0.5 sec, each time it is
pulsed.

Sol:-

Given, $T = 0.5 \text{ sec.}$

Formula, $T = 0.69 RC.$

Let us choose, $C = 1 \mu F$

$$R = \frac{0.5}{0.69 \times 1 \times 10^{-6}}$$

$$R = 0.7246 \times 10^6$$


$$R = 724.63 \text{ K}\Omega$$

realme 12x 5G


20 April 2026 at 12:20

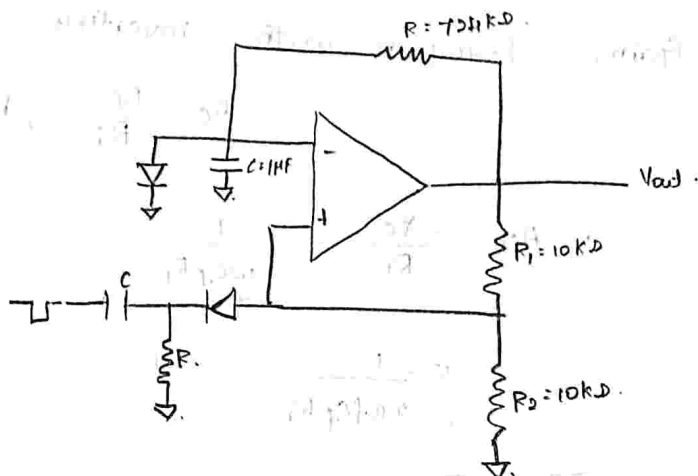assume, $R_1 = R_2 = 10 \text{ K}\Omega.$





Integrator:

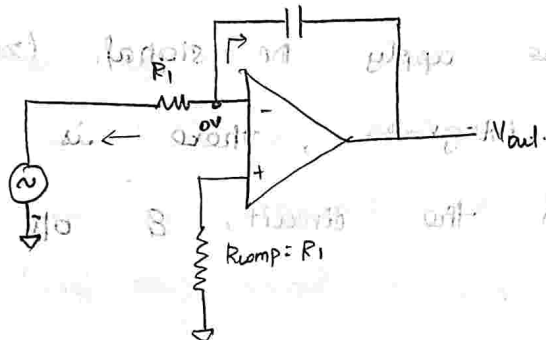

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

Apply nodal analysis at inverting terminal node.

$$\frac{0 - V_{in}}{R_1} + \frac{0 - C \frac{dV_{out}}{dt}}{1} = 0$$

$$-\frac{C \frac{dV_{out}}{dt}}{1} = \frac{V_{in}}{R_1}$$

$$\frac{dV_{out}}{dt} = -\frac{V_{in}}{R_1 C_f}$$

$$V_{out} = -\frac{1}{R_1 C_f} \int V_{in} \cdot dt + V_c(0)$$

$V_c(0) \rightarrow$ initial voltage at capacitor.

Gain, [compare with inverting amplifier,
 $A_c = -\frac{R_f}{R_i}$, here $R_f = X_c$]

$$\therefore A_{cl} = \frac{-X_c}{R_i} = -\frac{1}{\omega C_f R_i}$$

$$= -\frac{1}{2\pi f C_f R_i}$$

$$|A_{cl}| = \frac{1}{2\pi f R_i C_f}$$

If we apply DC signal (zero frequency) to the integrator, there is no feedback exist in the circuit, & o/p become saturated. (beoz it become open loop)

Due to the high gain it can't provide good stability.


open loop gain $\sim 10^6$

$$\text{gain in dB} = 20 \log_{10}(10^6)$$

$$= 20 \times 6 \\ = 120 \text{ dB}$$

$$|A_{cl}| = \frac{1}{2\pi f R_i C_f} = \frac{1}{(f/f_b) 120 \text{ dB}}$$


$$f_b = \frac{1}{2\pi R_i C_f}$$

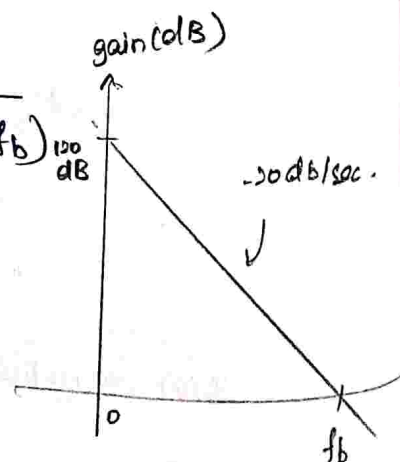

realme 12x 5G
 20 April 2026 at 12:20

gain of circuit touch '0' dB.

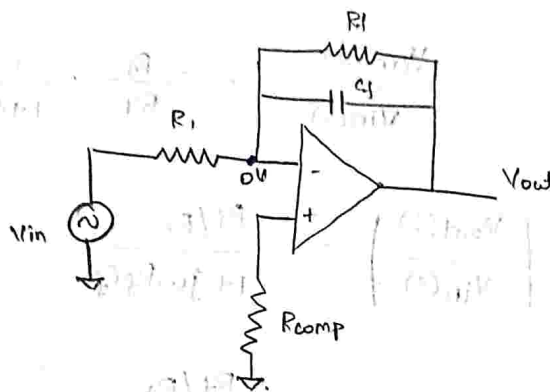practical Integrator : (lossy integrator).
To overcome the drawback we add one more resistor in feedback.



Now, if we give 0 Hz as frequency, the impedance of C_f is ∞ it becomes open circuit, now it is similar as inverting amplifier. so o/p doesn't saturate. Now the gain is $-\frac{R_f}{R_i}$.

Apply Nodal Analysis.

$$\frac{0 - V_{in}}{R_i} + \frac{0 - V_{out}}{R_f} - C \frac{dV_{out}}{dt} = 0.$$

$$-C \frac{dV_{out}}{dt} = \frac{V_{in}}{R_i} + \frac{V_{out}}{R_f}$$

take Laplace transform.

$$-s C_f V_{out}(s) = \frac{V_{in}(s)}{R_i} + \frac{V_{out}(s)}{R_f}$$

$$\frac{V_{out}(s)}{R_f} + s C_f V_{out}(s) = -\frac{V_{in}(s)}{R_i}$$

$$V_{out}(s) \left[\frac{1}{R_f} + s C_f \right] = -\frac{1}{R_i} V_{in}(s)$$

$$V_{out}(s) \left[\frac{1 + s R_f C_f}{R_f} \right] = -\frac{1}{R_1} V_{in}(s)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_f}{R_1} \cdot \frac{1}{1 + s R_f C_f}$$

$$\left| \frac{V_{out}(s)}{V_{in}(s)} \right| = \frac{R_f / R_1}{1 + j\omega R_f C_f}$$


$$= \frac{R_f / R_1}{1 + j2\pi f R_f C_f}$$

$$\left| \frac{V_{out}(s)}{V_{in}(s)} \right| = \frac{R_f / R_1}{1 + j \left[\frac{f}{f_a} \right]}$$

$$\therefore f_a = \frac{1}{2\pi R_f C_f}$$

If $f=0$, gain is $\frac{R_f}{R_1}$ (low freq)

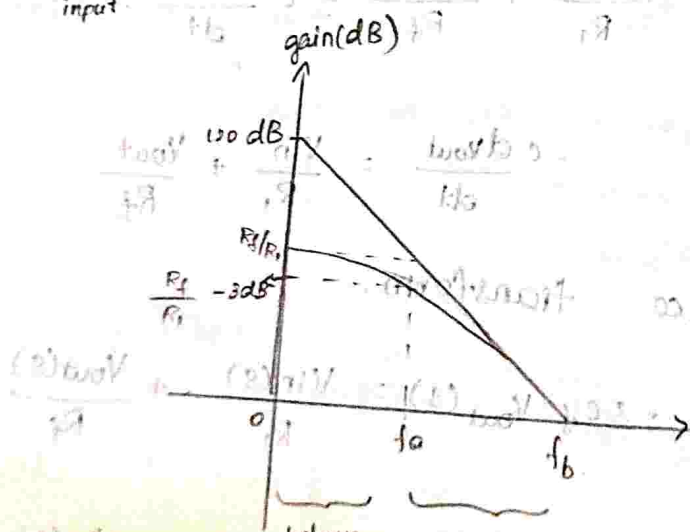when, $f=f_a$, the gain is reduce to -3 dB.



realme 12x 5G
20 April 2026 at 12:20

when we follow the

① R

②

③

⇒ without

⇒ with


is not

is not

so look

lossy (L)

Triangular

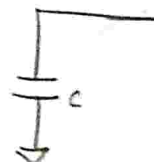

In order

square

In order

wave

when we design practical integrator we need to follow three rules:

① Relationship between R_f & $R_i \Rightarrow R_f = 10R_i$

② $f_{in} = 10f_o$


③ $f_o < f \leq f_2$

$\Rightarrow$ without R_f , C_f charge completely full)

$\Rightarrow$ with R_f , amount of charging by capacitor is reduce, no possible for full (or) complete charge.

$\therefore$ current divide & pass through R_f & C_f
so leakage of current occurs. so it is called lossy. (loss of power due to R_f).

Triangular Wave Generator:

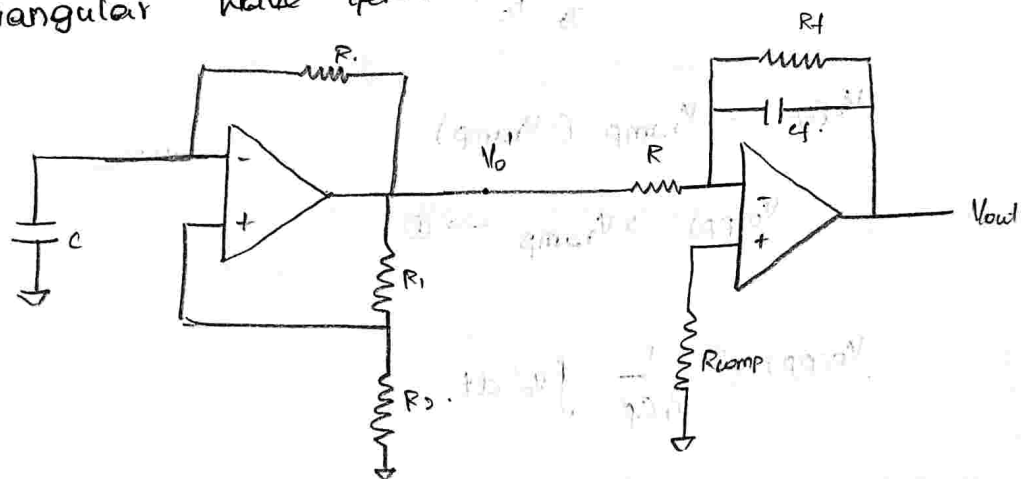



In order to determine the frequency of square wave generator. remove R & C .

In order to change voltage of square of wave generator. connect output with it.



realme 12x 5G

20 April 2026 at 12:20

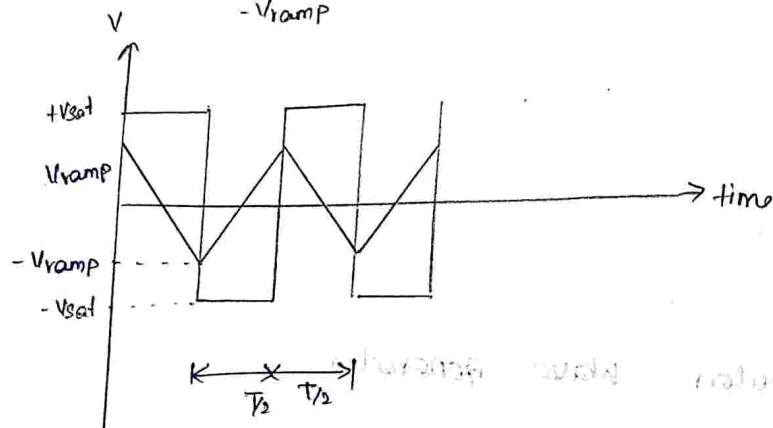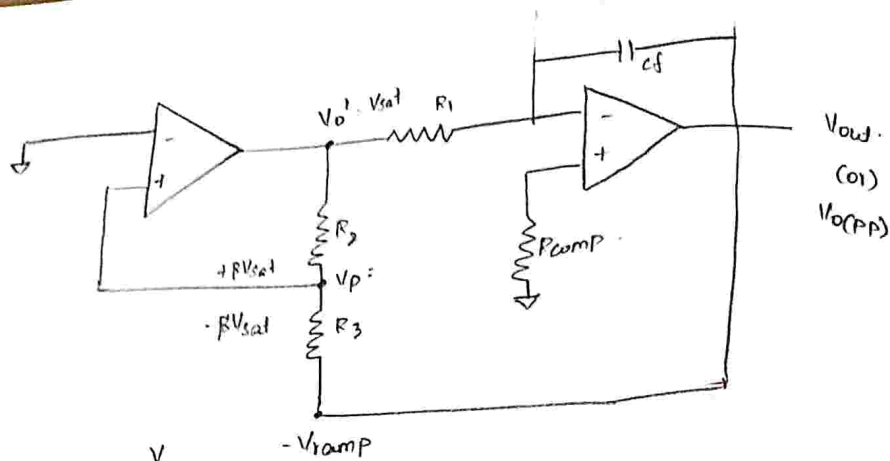

$$V_{o(pp)} = V_{ramp} - (-V_{ramp})$$

$$V_{o(pp)} = 2V_{ramp} \rightarrow \text{①}$$

$$V_{o(pp)} = \frac{-1}{R_1 C_f} \int V_0' dt$$

Initially we assume, $V_0' = +V_{sat}$

$$V_{out} = -V_{ramp}$$

apply nodal analysis with respect to V_p

$$\frac{V_p - V_{sat}}{R_3} + \frac{V_p - (-V_{ramp})}{R_3} = 0$$

$$V_p \left[\frac{1}{R_3} + \frac{1}{R_3} \right] = \frac{V_{sat}}{R_3} - \frac{V_{ramp}}{R_3}$$



realme 12x 5G

20 April 2026 at 12:20

$$V_p \left(\frac{R_2 + R_3}{R_2 R_3} \right) = \frac{V_{sat}}{R_2} - \frac{V_{ramp}}{R_3}$$

$$V_p (R_2 + R_3) = R_3 V_{sat} - R_2 V_{ramp}$$

$$V_p (R_2 + R_3) = R_3 V_{sat} - R_2 V_{ramp} + R_3 V_{ramp} - R_3 V_{ramp}$$

$$V_p (R_2 + R_3) = R_3 (V_{sat} + V_{ramp}) - V_{ramp} (R_2 + R_3)$$

$$V_p = \frac{R_3}{R_2 + R_3} (V_{sat} + V_{ramp}) - V_{ramp}$$

$V_p \rightarrow$ is point at which the transition from $+V_{sat}$ to $-V_{sat}$ make, $\therefore V_p = 0$.

$$\frac{R_3}{R_2 + R_3} [V_{sat}] + \frac{R_3}{R_2 + R_3} V_{ramp} - V_{ramp} = 0$$

$$\frac{R_3}{R_2 + R_3} \cdot V_{sat} + V_{ramp} \left[\frac{R_3}{R_2 + R_3} - 1 \right] = 0$$

$$V_{ramp} \left[\frac{R_3 - R_2 - R_3}{R_2 + R_3} \right] + \left(\frac{R_3}{R_2 + R_3} \right) V_{sat} = 0$$

$$R_3 V_{sat} = R_2 V_{ramp}$$

$$\therefore V_{ramp} = \frac{R_3}{R_2} V_{sat}$$

$$\therefore V_o(PP) = 2 V_{ramp} = \frac{2 R_3}{R_2} V_{sat}$$

$$V_{out}(PP) = \frac{1}{R_1 C_f} \int_0^{T/2} V_o' dt$$



realme 12x 5G

20 April 2026 at 12:20

$\frac{V_{ramp}}{R_3}$

$$= -\frac{1}{R_1 C_f} \int_0^{T/2} (-V_{sat}) dt$$

$$= \frac{1}{R_1 C_f} V_{sat} \cdot [t]_0^{T/2}$$

$$V_{out(PP)} = \frac{T \cdot V_{sat}}{2 R_1 C_f} \rightarrow (3)$$

equate (2) & (3)

$$\frac{2 R_3}{R_2} V_{sat} = \frac{T V_{sat}}{2 R_1 C_f}$$

$$T = \frac{4 R_1 R_3 C_f}{R_2}$$

This is time period of triangular wave generator.

$$\therefore f = \frac{1}{T} = \frac{R_2}{4 R_1 R_3 C_f}$$

OSCILLATOR:

It is an electronic device, to produce a sinusoidal (or) Non-sinusoidal signal periodically (continuously) without applying external input.




realme 12x 5G

20 April 2026 at 12:20

-ve F.B $\rightarrow \frac{V_o(s)}{V_i(s)} = \frac{G}{1+GH} \quad \text{or} \quad \frac{A}{1+A\beta}$

+ve F.B $\rightarrow \frac{V_o(s)}{V_i(s)} = \frac{G}{1-GH} \quad \text{or} \quad \frac{A}{1-A\beta}$

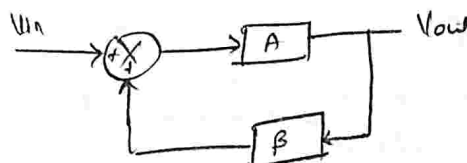* crystal oscillator provide high stability.



Barkhausen criterion: $|AB| = 1$

$\phi = 0^\circ / 360^\circ$

* if oscillator has -ve F.B, we won't get constant amplitude. (it can't generate continuously)

* To design a oscillator, the circuit should have +ve feedback. to get continuously $\rightarrow$ should be in-phase.

if $AB < 1$, $AB > 1$; we won't get continuous wave without apply external i/p.

RC oscillators:

The feedback network $\frac{V_o}{V_i}$ is designed only with the help (use) of resistor & capacitor.

Drawback:

* The o/p of signal the frequency is in Hz (or) $> 10^4$ Hz.

realme 12x5G stability is low


20 April 2026 at 12:20



①. R-C phase shift oscillator.

⑤. Wien-bridge oscillator.

①. RC phase shift oscillator.

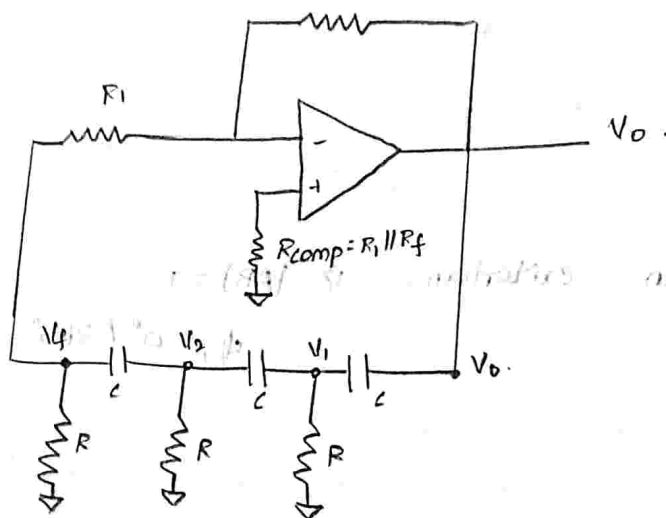

OP-amp provide -180° phase shift.


Feedback network - 180° phase shift provide

$$= 360^\circ$$

In F.B network, each RC network provide 60° to satisfy, $|A\beta| = 1$. Phase shift

by phase $\beta = \frac{V_f}{V_o}$ [feedback gain]

$$V_f = \beta V_o$$

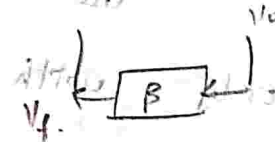

Sustained oscillation:

It generates waveform with

constant amplitude & frequency.

$$|A\beta| = 1$$



realme 12x 5G

20 April 2026 at 12:20

uator.

If $|AB| < 1$, the amplitude decreases.

If $|AB| > 1$, the output becomes saturated.

write down KCL with respect to node 1 V_1 .

$$\frac{V_1 - V_0}{X_c} + \frac{V_1 - 0}{R} + \frac{V_1 - V_2}{X_c} = 0.$$

$$X_c = \frac{1}{sC}$$

$$(V_1 - V_0) sC + \frac{V_1}{R} + (V_1 - V_2) sC = 0.$$

$$V_1 sC + \frac{V_1}{R} + V_1 sC - V_0(sC) - V_2(sC) = 0.$$

$$V_1 \left[2sC + \frac{1}{R} \right] - V_0(sC) - V_2(sC) = 0.$$

$$V_1 \left[\frac{1 + 2sCR}{R} \right] - V_0(sC) - V_2(sC) = 0.$$

$$V_1 (1 + 2sCR) - V_0(sCR) - V_2(sCR) = 0.$$

$$V_1 [1 + 2sCR] - V_2 [sCR] = V_0 [sCR]$$

$$V_0 = \frac{V_1 (1 + 2sCR)}{sCR} - V_2 \rightarrow \text{①}$$


write down KCL with respect to

node 2 V_2

$$\frac{V_2 - V_1}{X_c} + \frac{V_2 - 0}{R} + \frac{V_2 - V_3}{X_c} = 0.$$

$$(V_2 - V_1) (sC) + \frac{V_2}{R} + (V_2 - V_3) (sC) = 0.$$

provide 60°
phase shift.

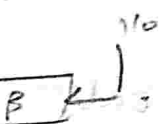

realme 12x 5G

20 April 2026 at 12:20

$$V_2 sC + \frac{V_2}{R} + V_2 sC - V_1(sC) - V_f(sC) = 0$$

$$V_2 \left[2sC + \frac{1}{R} \right] - V_1(sC) - V_f(sC) = 0$$

$$V_2 \left[\frac{1+2sCR}{R} \right] - V_1(sCR) - V_f(sCR) = 0$$

$$V_f(sCR) = V_2 (1+2sCR) - V_1(sCR)$$

$$V_f = \frac{V_2 (1+2sCR)}{sCR} - V_1 \rightarrow \textcircled{D}$$

write down KCL with respect to node 3

$$\frac{V_f - V_2}{R_C} + \frac{V_f - 0}{R} = 0$$

$$(V_f - V_2) sC + \frac{V_f}{R} = 0$$

$$V_f \left[sC + \frac{1}{R} \right] - V_2(sC) = 0$$

$$V_f \left[\frac{1+R sC}{R} \right] - V_2(sC) = 0$$

$$V_f (1+R sC) - V_2(sCR) = 0$$

$$V_2 = \frac{V_f (1+R sC)}{sCR} \rightarrow \textcircled{B}$$

sub $\textcircled{B}$ in $\textcircled{D}$

$$V_f = \frac{V_f (1+R sC)}{sCR} \cdot \frac{(1+2sCR)}{sCR} - V_1$$

$$V_f = \frac{V_f (1+R sC) (1+2sCR)}{s^2 C^2 R^2} - V_1$$



realme 12x 5G

20 April 2026 at 12:21

$$V_f = \frac{V_f (1 + 2sCR + sRC + 2s^2 R^2 C^2)}{s^2 R^2 C^2} = V_1$$

$$-V_f + \frac{V_f (1 + 3sCR + 2(sRC)^2)}{(sRC)^2} = V_1$$

$$\frac{-V_f (sRC)^2 + V_f (1 + 3sCR + 2(sRC)^2)}{(sRC)^2} = V_1$$

$$\frac{V_f [- (sRC)^2 + 1 + 3sCR + 2(sRC)^2]}{(sRC)^2} = V_1$$

$$V_1 = \frac{V_f [(sRC)^2 + 1 + 3sCR]}{(sRC)^2}$$

$$V_1 = \frac{V_f [1 + 3sCR + (sRC)^2]}{(sRC)^2}$$

sub $V_1 \rightarrow V_2$ in (1)

$$V_0 = \frac{V_f [1 + 3sCR + (sRC)^2]}{(sRC)^2} \cdot \frac{(1 + 2sCR)}{(sRC)} - \frac{V_f (1 + sRC)}{sRC}$$

$$= \frac{V_f (1 + 3sCR + (sRC)^2) (1 + 2sCR)}{(sRC)^3} - \frac{V_f (1 + sRC)}{sRC}$$

$$= \frac{V_f [1 + 3sCR + (sRC)^2] (1 + 2sCR) - V_f (1 + sRC)(sRC)^2}{(sRC)^3}$$

$$= \frac{V_f [1 + 2sCR + 3sCR + 6(sRC)^2 + (sRC)^2 + 2(sRC)^3] - V_f [(sRC)^2 + (sRC)^3]}{(sRC)^3}$$

$$V_o = \frac{V_f [1 + 5sRC + 7(sRC)^2 + 2(sRC)^3] - V_f [(sRC)^2 + (sRC)^3]}{(sRC)^3}$$

$$V_o = \frac{V_f [1 + 5sRC + 7(sRC)^2 + 2(sRC)^3 - (sRC)^2 - (sRC)^3]}{(sRC)^3}$$

$$V_o = \frac{V_f [1 + 5sRC + (sRC)^3 + 6(sRC)^2]}{(sRC)^3}$$

$$\frac{V_f}{V_o} = \frac{(sRC)^3}{[1 + 5sRC + 6(sRC)^2 + (sRC)^3]}$$

$$B = \frac{(sRC)^3}{(sRC)^3 \left[\frac{1}{(sRC)^3} + 5 \frac{1}{(sRC)^2} + \frac{6}{sRC} + 1 \right]}$$

$$B = \frac{V_f}{V_o} = \left[\frac{1}{1 + \frac{5}{(sRC)^2} + \frac{6}{sRC} + \frac{1}{(sRC)^3}} \right]$$

Replace s with $j\omega$ and ω with

$2\pi f$.

$$B = \frac{1}{1 + \frac{5}{j2\pi f RC} + \frac{6}{4\pi^2 f^2 R^2 C^2} + \frac{1}{j(2\pi f RC)^3}}$$

$$B = \frac{1}{1 - 5\left(\frac{f}{f_c}\right)^2 + \frac{1}{j} \left[6\left(\frac{f}{f_c}\right) - \left(\frac{f}{f_c}\right)^3 \right]}$$



realme 12x 5G
20 April 2026 at 12:21

$$[(SRC)^2 + (SRC)^3]$$

$$- (SRC)^3]$$

$$\therefore f_1 = \frac{1}{2\pi RC}$$

$$= \frac{1}{\left[1 - 5\left(\frac{f_1}{f}\right)^2\right] - j \left[6\left(\frac{f_1}{f}\right) - \left(\frac{f_1}{f}\right)^3\right]}$$

The imaginary term is zero.

$$\beta = \frac{1}{\left(1 - 5\left(\frac{f_1}{f}\right)^2\right)} \rightarrow (3)$$

$$\left[6\left(\frac{f_1}{f}\right) - \left(\frac{f_1}{f}\right)^3\right] = 0$$

$$6\left(\frac{f_1}{f}\right) = \left(\frac{f_1}{f}\right)^3$$

$$\frac{f_1}{f} = \sqrt{6} \rightarrow (11)$$

$$f_0 = \frac{1}{\sqrt{6} \cdot 2\pi RC}$$

sub (11) in (3),

$$\beta = \frac{1}{1 - 5(6)}$$

$$\beta = \frac{1}{1 - 30} = \frac{1}{-29}$$

$$A_V \cdot \beta = 1$$

$$A_V \cdot \left(-\frac{1}{29}\right) = 1$$

$$A_V \geq -29$$

To find R_i & R_f .

$$1 - \frac{R_f}{R_i} = -29$$

$$R_f = 29 R_i$$


$$R_i = 10 R$$



realme 12x 5G

20 April 2026 at 12:21

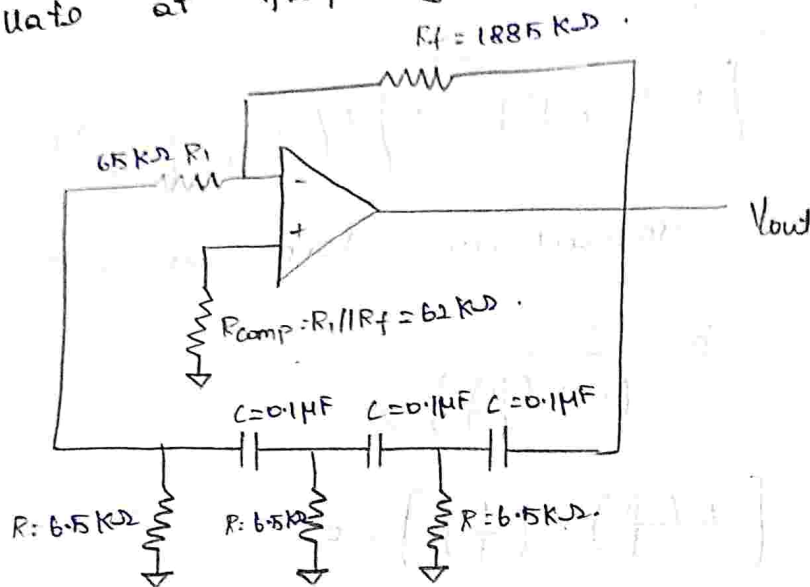6). Design an RC phase shift oscillator to oscillate at frequency $f_0 = 100 \text{ Hz}$.



$$f_0 = \frac{1}{\sqrt{6} \cdot 2\pi RC}$$

Let $C = 0.1 \mu\text{F}$.

$$100 = \frac{1}{\sqrt{6} \times 2 \times 3.14 \times R \times 0.1 \times 10^{-6}}$$

$$100 = \frac{1}{1.5382 \times 10^{-6} \times R}$$

$$\frac{1}{R} = 153.82 \times 10^{-6}$$

$$R = 6.501 \times 10^6 \times 10^{-3}$$

$R = 6.5 \text{ k}\Omega$.

$$R_1 = 10(R)$$

$$= 10 \times 6.5 \times 10^3$$

$R_1 = 65 \text{ k}\Omega$.

$$R_f = 29(65 \text{ k}\Omega)$$

$R_f = 1885 \text{ k}\Omega$.



realme 12x 5G

20 April 2026 at 12:21

$$\frac{1}{R_{comp}} = \frac{1}{R_1} + \frac{1}{R_f}$$

$$\frac{1}{R_{comp}} = \frac{1}{65000} + \frac{1}{1885000}$$

$$\frac{1}{R_{comp}} = \frac{1885000 + 65000}{(65000)(1885000)}$$

$$= \frac{1950000}{1.225 \times 10^{11}}$$

$$= 1950 \times 10^{-8}$$

$$1.225 \times 10^{11}$$

$$\frac{1}{R_{comp}} = 1591.83 \times 10^{-8}$$


$$R_{comp} = 6.283 \times 10^{-4} \times 10^8$$

$$= 6.283 \times 10^4$$

$$R_{comp} = 62 \text{ K}\Omega$$

WHEATSTONE - BRIDGE

OSCILLATOR:

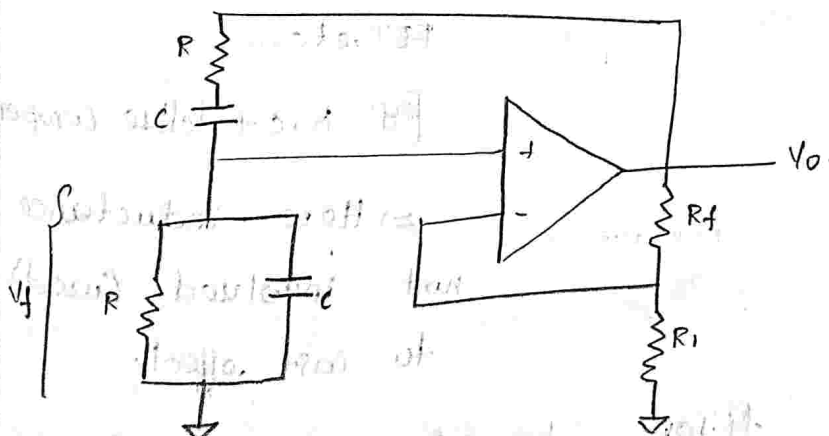

Active Filters:


Filter $\rightarrow$ Frequency selective Network.

* Based on nature of signals as i/p.

Filter is classified in.

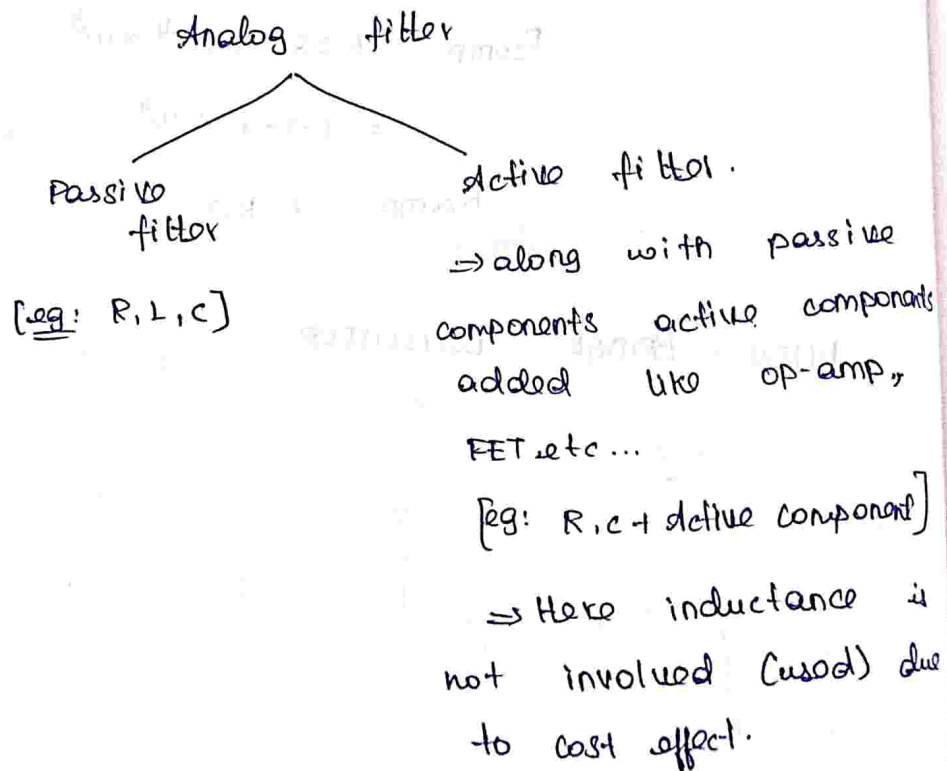1. Analog filter.
2. Digital filter.

* In analog filter is classified based on the components used.



* Active filter based on suppression of i/p signal is classified as,

1. Low pass filter - LPF

2. High pass filter - HPF

3. Band pass filter - BPF.



realme 12x5G
20 April 2026 at 12:21

4). BEF / BRF / BSF

*. Based on frequency response, the filter classification.

reduction in gain occurs in monotonically ↓ so.

PS → Pass band.

SB → Stop band.

1. Butterworth filter - flat PB, flat SB.

[You may not find the ripple

2. Chebyshev filter ↑

3. Bessel function.

⇒ We use Butterworth filters.

Parameters:

1). Pass Band.

2). Stop Band.

3). Cut-off frequency.

Let us consider low pass filter.

f_h → maximum range of freq. that is transmitted

by LPF filter.

stop band } Range of frequency of LP signal
band } that can be suppressed / eliminated /
attenuated by filter circuit.

case (ii): $f \gg f_L$

(a)

$$\left| \frac{V_o(s)}{V_i(s)} \right| > A_F$$

$$V_o(s) > A_F V_{in}(s)$$


It allows all the signal frequency greater than cut-off frequency.

case (iii): $f = f_L$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \frac{A_F \left(\frac{f}{f_L} \right)}{\sqrt{1 + \left(\frac{f}{f_L} \right)^2}}$$

$$= \frac{A_F \cdot (1)}{\sqrt{1+1}} = \frac{A_F}{\sqrt{2}}$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = 0.707 A_F$$

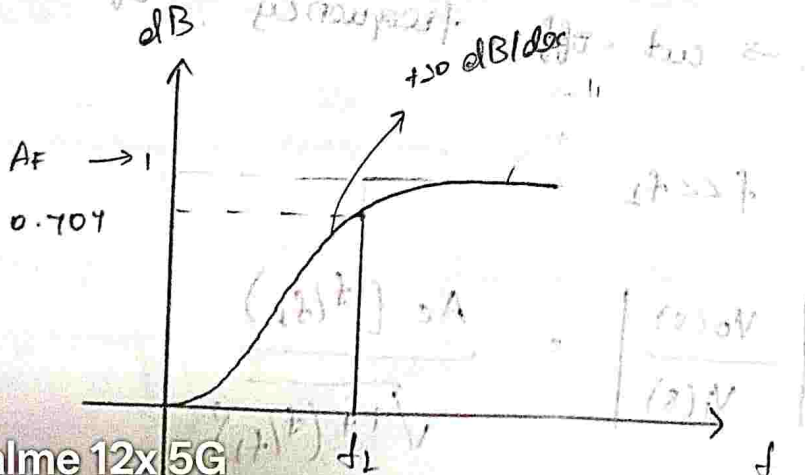

Design a 1st HPF the cut off frequency of 2 KHz.

$$f_1 = 2 \text{ KHz.}$$

$$f_1 = 2 \times 10^3 \text{ Hz.}$$

$$f_1 = \frac{1}{2\pi RC} = 2 \times 10^3$$


frequency.

Let $C = 1 \mu\text{F}$, $R = \frac{1}{4 \times \pi \times 1 \times 10^6 \times 10^3}$

$$= \frac{1}{12.5663}$$

$$R = 0.07957 \text{ K}\Omega$$

$$R = 79.57 \Omega$$

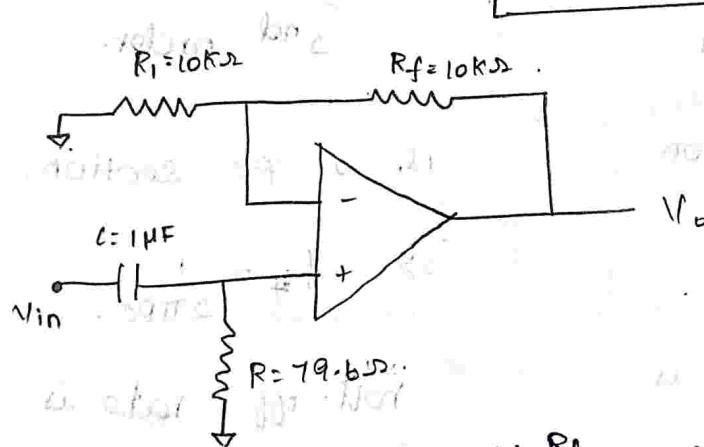

$$A_{F_1} = 1 + \frac{R_f}{R_1} = 2$$

$$\frac{R_f}{R_1} = 1$$

$$\therefore R_f = R_1$$

Let us assume

$$R_1 = R_f = 10 \text{ K}\Omega$$



realme 12x 5G

20 April 2026 at 12:22

Note:

*. For n^{th} order high pass filter, the generalized expression of gain is.

(1/4)

$$\left| \frac{V_o(s)}{V_i(s)} \right| = |H(s)| = \frac{A_F}{\sqrt{1 + (f_L/f)^{2n}}}$$

*. For n^{th} order of LPF.

$$\left| \frac{V_o(s)}{V_i(s)} \right| = |H(s)| = \frac{A_F}{\sqrt{1 + (f/f_H)^{2n}}}$$

Difference btwn 1st & 2nd order HPF.

1st order

1). 1 RC section

2). $f_L = \frac{1}{2\pi RC}$

roll-off rate is
+20 db/dec.

2nd order.

1). 2 - RC section.

2). $f_H = \frac{1}{2\pi RC}$

roll-off rate is
+40 db/dec.


*. For n^{th} order HPF, is +n20 db/dec.



realme 12x 5G


20 April 2026 at 12:22

2nd order high-pass filter

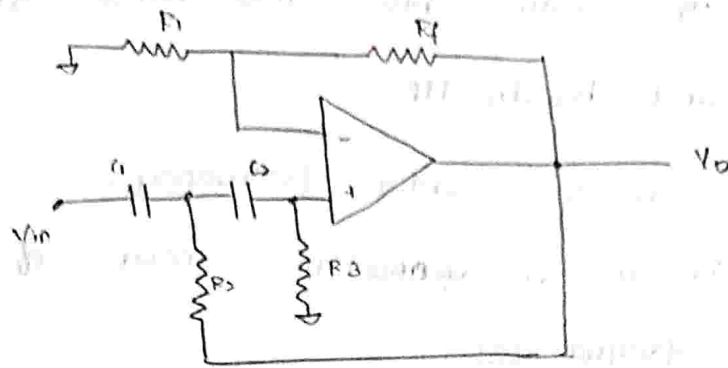

Band-pass filter (BPF).

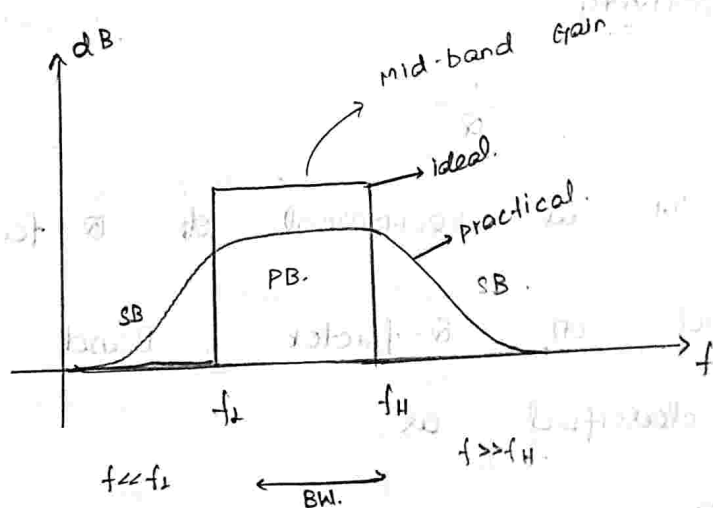It allows all the signal frequency which is lies between two cut-off frequency. (f_L & f_H)



$\Rightarrow$ The signal is attenuated when $f \ll f_L$, $f \gg f_H$.
 $\Rightarrow$ b/w f_L & f_H is called "mid band frequency".

Bandwidth:

* The range of frequency for which (the gain is maximum) or (the circuit maximum gain)

is used to analyse the performance of the active filters.



realme 12x 5G providing

20 April 2026 at 12:22

Quality-factor:
 * The ratio b/w mid-band frequency (f_0) and bandwidth.

$\therefore f_0 = f_c = \text{center frequency.}$

$\Rightarrow$ It is a geometric mean of two cut-off frequencies.

$$Q = \frac{f_0}{BW} = \frac{f_c}{BW}$$

$$f_0 = f_c = \sqrt{f_L \cdot f_H}$$

selectivity:


$$= \frac{1}{Q}$$

It is reciprocal of Q-factor.

• Based on Q-factor, Band pass filter is classified as,

①. If $Q > 10 \rightarrow$ NBPF - Narrow band pass filter.

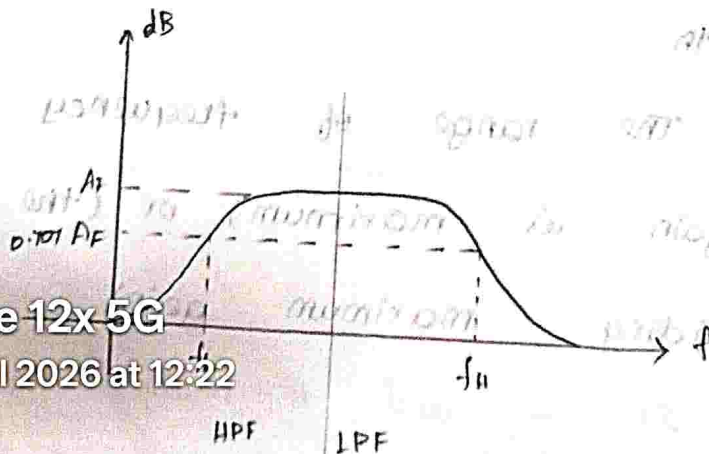
②. If $Q < 10 \rightarrow$ WBPF - wide band pass filter.



realme 12x 5G
 20 April 2026 at 12:22

1st order wide Band Pass filter (WBPF).

*. The HPF is cascaded with LPF.

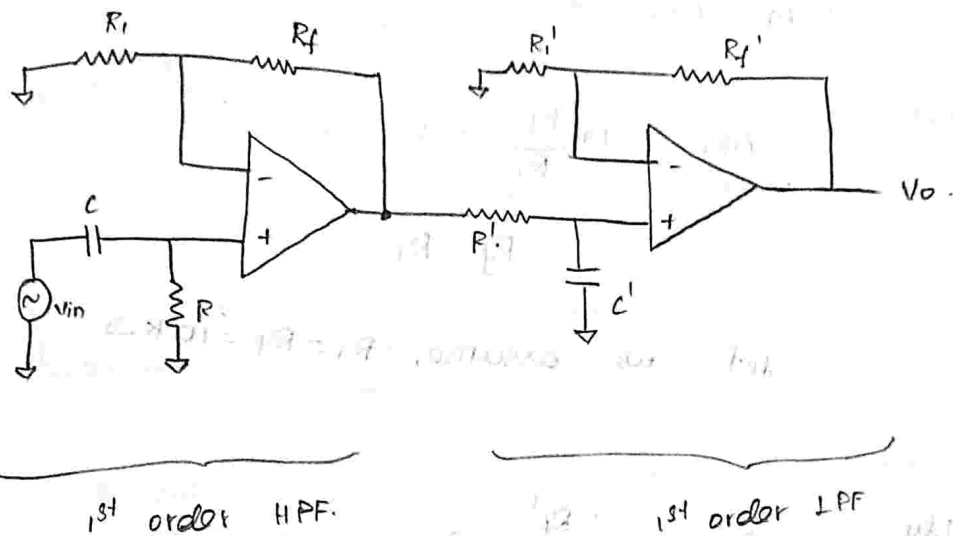

$$\left| \frac{V_o(s)}{V_{in}(s)} \right| = |H(s)| = \frac{A_{F1} \left(\frac{f}{f_L} \right)}{\sqrt{1 + \left(\frac{f}{f_L} \right)^2}} \cdot \frac{A_{F2}}{\sqrt{1 + \left(\frac{f}{f_H} \right)^2}}$$

[∴ gain of WBPF = Product of HPF & LPF.]

- Q. Design a wide BPF having $f_L = 400 \text{ Hz}$.
and $f_H = 2 \text{ kHz}$ and pass band gain of 4.
also find the quality factor of the filter circuit.

Sol.

$$f_L = 400 \text{ Hz}$$

$$f_H = 2 \text{ kHz}$$

WBPF gain of 4.

realme 12x 5G

20 April 2026 at 12:22

Q = ?



$$1 = A_{F1} \cdot A_{F2}$$

$$\therefore A_{F1} = A_{F2} = 2$$

here,

$$A_{F1} = 1 + \frac{R_f}{R_1} = 2$$

$$R_f = R_1$$

let us assume, $R_1 = R_f = 10 \text{ K}\Omega$.

also,

$$A_{F2} = 1 + \frac{R_f'}{R_1'} = 2$$

$$\therefore \frac{R_f'}{R_1'} = 1 \Rightarrow R_f' = R_1'$$

let us assume $R_1' = R_f' = 10 \text{ K}\Omega$.

for HPF,

$$f_c = 400 \text{ Hz}$$

$$f_c = \frac{1}{2\pi RC} = 400$$

let $C = 1 \text{ }\mu\text{F}$

$$R = \frac{1}{400 \times 2 \times \pi \times 10^{-6}}$$

$$= \frac{1}{2513.27 \times 10^{-6}}$$

$$= 397.88 \times 10^3$$

$R = 397.88 \text{ }\Omega$



realme 12x 5G

20 April 2026 at 12:23

for LPF, $f_H = 5 \text{ kHz}$


$$f_H = \frac{1}{2\pi R' C'} = 5 \times 10^3$$

Let $C = 1 \mu\text{F}$

$$R' = \frac{1}{4 \times \pi \times 10^3 \times 1 \times 10^{-6}}$$


$$= 0.07961 \times 10^3$$

$$R' = 79.61 \Omega$$

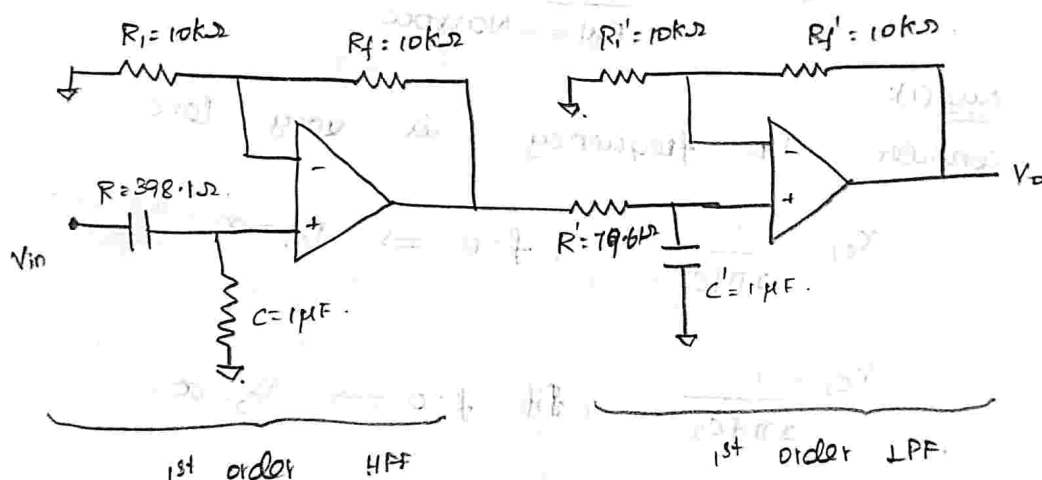

Narrow Band pass filter: (NBPF)

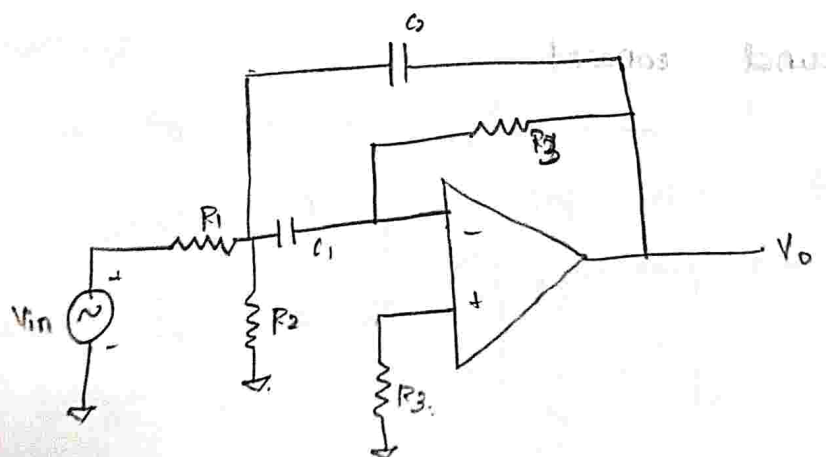⇒ The input signal is given in inverting terminal.



op-amp is configured in inverting mode.

②. It has two feedback.

because of this $\therefore$ feedback it is
known as multiple feedback filter.

③. C_1 is responsible for make this
circuit fn as LPF.

C_2 is responsible for make this
circuit fn as HPF.

$C_1 \rightarrow$ LPF

$C_2 \rightarrow$ HPF.

④. $Q > 10 = \frac{f_0}{\text{BWL} \leftarrow \text{Narrow}}$

case (i):

consider i/p frequency is very less.


$$X_{C_1} = \frac{1}{2\pi f C_1}, \text{ if } f=0 \Rightarrow X_{C_1} = \infty.$$

$$X_{C_2} = \frac{1}{2\pi f C_2}, \text{ if } f=0 \Rightarrow X_{C_2} = \infty.$$

$\therefore$ If $X_{C_1} = X_{C_2} = \infty$ it act as open circuit.

hence $V_D = 0$ due to virtual

ground concept.

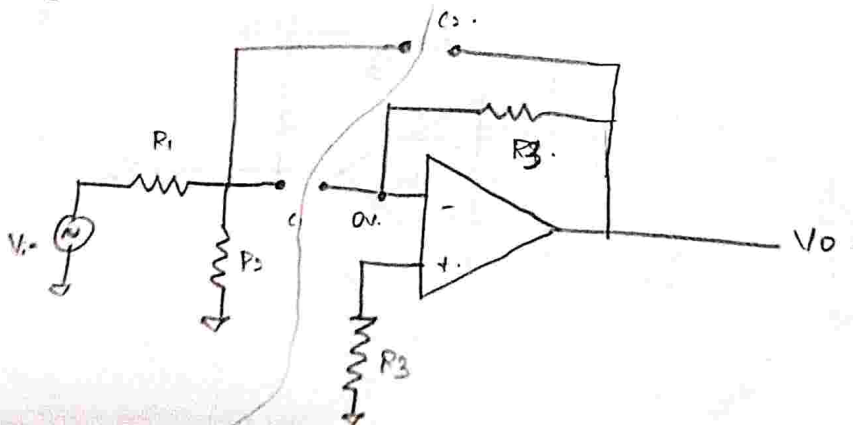

$\Rightarrow$ It exhibits the behaviour
of HPF.

$$\frac{V_o}{V_{in}} = \frac{-sR_f C_i}{(1+sR_f C_f)(1+sR_i C_i)}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{sR_f C_i}{(1+sR_f C_f)(1+sR_i C_i)}$$

assume, $R_f C_f = R_i C_i$.

$$\left| \frac{V_o}{V_{in}} \right| = \frac{sR_f C_i}{[1+sR_i C_i]^2}$$


$$s = j\omega$$

$$= j2\pi f$$

$$= \frac{sR_f C_i}{[1+j2\pi f R_i C_i]^2}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{sR_f C_i}{[1+j(f/f_b)]^2}$$
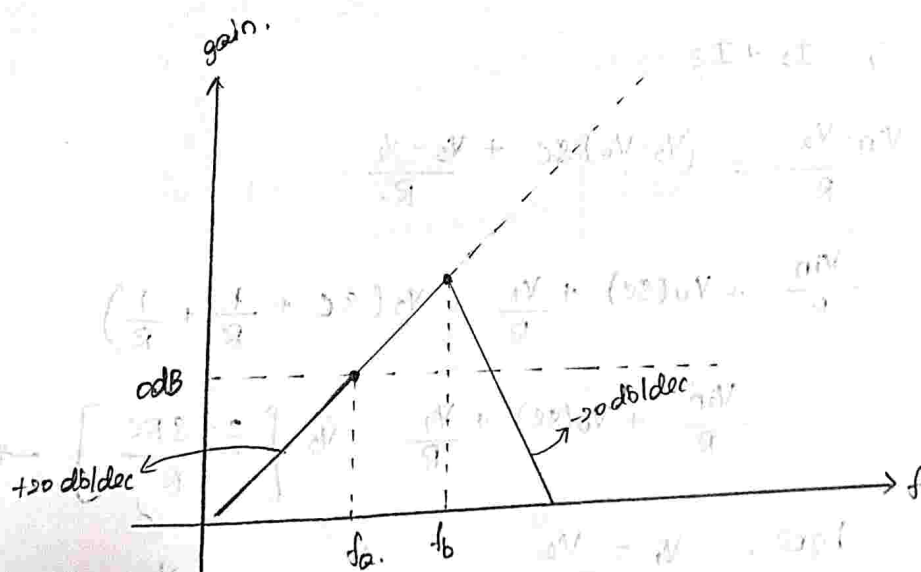
$$\text{here, } f_b = \frac{1}{2\pi R_i C_i} = \frac{1}{2\pi R_f C_f}$$



realme 12x 5G

20 April 2026 at 12:24

A = 0 dB.

conditions to design:

$$\rightarrow f_b = 10 f_a$$

→ signal frequency $f_s = \frac{f_a}{50}$

$$\rightarrow T \geq R_f C_1$$


$$\rightarrow R_1 C_1 = R_f C_f$$

→ use f_a find R_f

→ use $f_b = 10 f_a$ find f_b


→ use f_b find R_1

2nd order low pass filter:

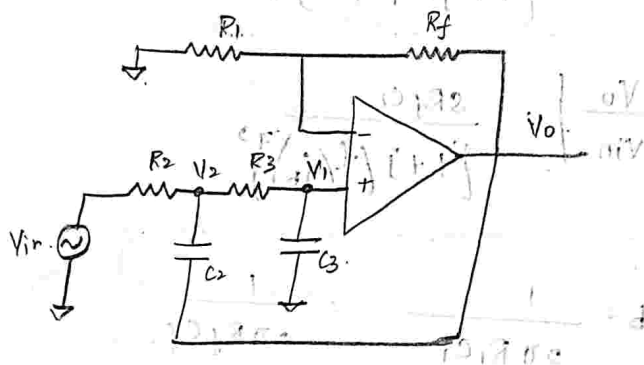

$$V_o = \left[1 + \frac{R_f}{R_1} \right] V_1 \rightarrow (1)$$

let $R_2 = R_3 = R$, $C_2 = C_3 = C$

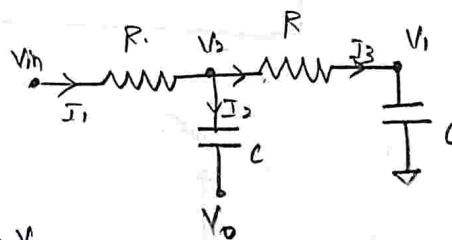

$$I_1 = I_2 + I_3$$

$$\frac{V_{in} - V_2}{R} = (V_2 - V_o) sC + \frac{V_2 - V_1}{R}$$

$$\frac{V_{in}}{R} + V_o(sC) + \frac{V_1}{R} = V_2 \left(sC + \frac{1}{R} + \frac{1}{R} \right)$$

$$\frac{V_{in}}{R} + V_o(sC) + \frac{V_1}{R} = V_2 \left[\frac{2 + sRC}{R} \right] \rightarrow (2)$$

here, $V_1 = \frac{V_2}{R + 1/sC} \cdot \frac{1}{sC} = \frac{V_2}{1 + sRC}$



realme 12x 5G

20 April 2026 at 12:24

$$\therefore V_3 = V_1 (1 + sRC)$$

apply this into equ (3).

$$\frac{V_{in}}{R} + V_o(sC) + \frac{V_1}{R} = \frac{V_1 (1 + sRC) (2 + sRC)}{R}$$

$$\frac{V_{in}}{R} + V_o(sC) = \frac{V_1 [2 + sRC + 2sRC - (sRC)^2] - V_1}{R}$$

$$\frac{V_{in}}{R} + V_o(sC) = \frac{V_1}{R} [2 + 3sRC + (sRC)^2 - 1]$$

$$\frac{V_{in}}{R} + V_o(sC) = \frac{V_1}{R} [1 + 3sRC + (sRC)^2]$$

$$V_{in} + V_o(sRC) = V_1 [1 + 3sRC + (sRC)^2]$$

$$\therefore V_1 = \frac{V_{in} + V_o(sRC)}{1 + 3sRC + (sRC)^2}$$

apply this into equ (1).

$$V_o = A_f \left[\frac{V_{in} + V_o(sRC)}{1 + 3sRC + (sRC)^2} \right]$$


$$V_o = A_f \left[\frac{V_{in}}{1 + 3sRC + (sRC)^2} \right] + A_f \left[\frac{V_o(sRC)}{1 + 3sRC + (sRC)^2} \right]$$

$$V_o \left[1 - \frac{A_f(sRC)}{1 + 3sRC + (sRC)^2} \right] = A_f \frac{V_{in}}{1 + 3sRC + (sRC)^2}$$

$$V_o \left[\frac{1 + 3sRC + (sRC)^2 - A_f(sRC)}{1 + 3sRC + (sRC)^2} \right] = A_f \frac{V_{in}}{1 + 3sRC + (sRC)^2}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{A_f}{1 + sRC [3 - A_f] + (sRC)^2}$$
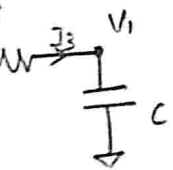
$$\left[\frac{1}{1 + sRC} \right] V_1 \rightarrow (1)$$



$$\rightarrow (2)$$



$$\frac{V_o}{V_{in}} = \frac{A_F}{1 + sRC[3 - A_F] + s^2 R^2 C^2}$$

$$= \frac{A_F}{R^2 C^2 \left[s^2 + \frac{s}{RC} (3 - A_F) + \frac{1}{R^2 C^2} \right]}$$

$$= \frac{A_F}{(RC)^2}$$

$$\frac{s^2 + \left[\frac{3 - A_F}{RC} \right] s + \frac{1}{R^2 C^2}}$$

$$= \frac{A_F \omega_h^2}{s^2 + \alpha \omega_h s + \omega_h^2}$$

$$\omega_h = \frac{1}{RC}$$

$$\alpha = 3 - A_F$$

(2)

design

filter

1 KHz.

sol:

$$\frac{V_o}{V_{in}} = A_F \cdot \frac{1/R^2 C^2}{s^2 + \left[\frac{3 - A_F}{RC} \right] s + \frac{1}{R^2 C^2}} \rightarrow (3)$$

we know that for 2nd order system.

$$\frac{V_o}{V_{in}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} = \frac{\omega_n^2}{s^2 + \sqrt{2}s + 1} \rightarrow (4)$$

compare (3) & (4).

$$\frac{3 - A_F}{RC} = \sqrt{2}$$

$$\text{let } RC = 1,$$

$$3 - A_F = \sqrt{2}$$

$$A_F = 3 - \sqrt{2}$$

$$A_F = 1.586$$

Realme 12x5G

LPH

20 April 2024 at 12:24

$$\left| \frac{H(j\omega)}{A_0} \right| = \frac{1}{\sqrt{1 + (\omega/\omega_h)^2}}$$

Vin.

Also,

$$\omega_h^2 = \omega_o^2 = \frac{1}{R^2 C^2}$$

$$\omega_o = \frac{1}{RC}$$

$$f_o = \frac{1}{2\pi RC}$$

$$H, R_1 = R_2 = R, C_1 = C_2 = C$$

$$f_o = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$\omega_h = \frac{1}{RC}$$

$$X = 3 - AF$$

② design a second order butterworth lowpass filter having upper cut-off frequency of 1 kHz.

Sol:-

$$AF = 1 + \frac{R_f}{R_1} = 1.586$$


$$R_f = 0.586 R_1$$

$$\text{Let } R_1 = 10 \text{ k}\Omega, R_f = 5.86 \text{ k}\Omega$$

$$f_o = \frac{1}{2\pi RC} = 1000$$

$$\text{Let } C = 0.1 \mu\text{F}, R = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 1000}$$


$$R = 1.6 \text{ k}\Omega$$

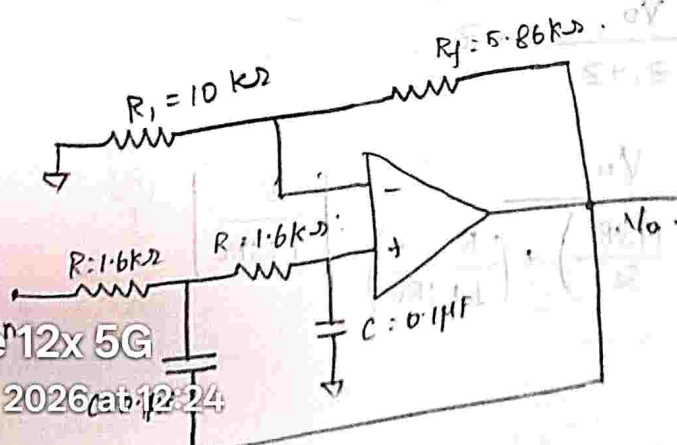

order factors of polynomials.

1. $s+1$
2. $s^2 + \sqrt{5}s + 1$
3. $(s+1)(s^2+s+1)$
4. $(s^2+0.765s+1)(s^2+1.848s+1)$
5. $(s+1)(s^2+0.618s+1)(s^2+1.618s+1)$

Wien- Bridge oscillator:

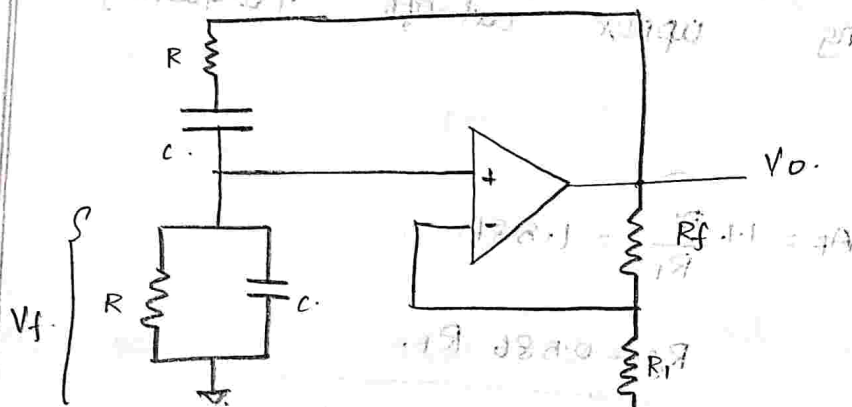


Let $Z_1 = R + \frac{1}{sC} = \frac{1+sRC}{sC}$

$Z_2 = R \parallel \frac{1}{sC} = \frac{R \times 1/sC}{R + 1/sC} = \frac{R}{sRC + 1}$

here, V_f = Voltage across ' Z_2 '

$V_f = \frac{V_o}{Z_1 + Z_2} \cdot Z_2$

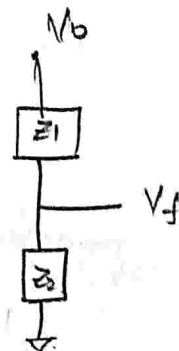$= \frac{V_o}{\left(\frac{1+sRC}{sC} \right) + \left(\frac{R}{1+sRC} \right)} \cdot \left[\frac{R}{1+sRC} \right]$



realme 12x 5G

20 April 2026 at 12:24

$$= \frac{V_o (1+sRC)(sC)}{[C(1+sRC)^2 + sCR]} \cdot \frac{R}{(1+sRC)}$$

$$V_f = \frac{V_o (sRC)}{1 + (sRC)^2 + 2sRC + sCR}$$

$$\text{total } V_f = \frac{V_o (sRC)}{1 + 3sRC + (sRC)^2}$$

$$\therefore \beta = \frac{V_f}{V_o} = \frac{sRC}{1 + 3sRC + (sRC)^2}$$

$$= \frac{sRC}{sRC \left[3 + sRC + \frac{1}{sRC} \right]}$$

$$= \frac{1}{3 + j\omega RC + \frac{1}{j\omega RC}}$$

$$\beta = \frac{1}{3 + j \left[\omega RC - \frac{1}{\omega RC} \right]}$$

to have sustained oscillations ' β ' must be a Real.

$$\beta = \frac{V_f}{V_o} = \frac{1}{3}$$

equating Imaginary part to '0'.

$$\omega RC - \frac{1}{\omega RC} = 0$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega^2 = \frac{1}{R^2 C^2} \Rightarrow \omega = \frac{1}{RC}$$

$$\boxed{f_0 = \frac{1}{2\pi RC}}$$



realme 12x 5G

20 April 2026 at 12:24

To satisfy the magnitude condition,

$$A_v \beta = 1.$$

$$A_v \left(\frac{1}{3} \right) = 1.$$

$$A_v = 3.$$

(13). Design a Wien bridge oscillator for $f_0 = 1 \text{ kHz}$.

Sol: Given, $f_0 = 1 \text{ kHz} = 1000 \text{ Hz}$.

$$\text{W.K.T } f_0 = \frac{1}{2\pi RC} = 1000$$

$$\text{Let } C = 0.1 \mu\text{F}.$$

$$R = \frac{1}{2\pi \times 1000 \times 0.1 \times 10^{-6}}$$

$$R = 1.59 \text{ k}\Omega.$$

$$R \approx 1.6 \text{ k}\Omega.$$

for Wien-bridge


$$A_v = 3.$$

$$\left[1 + \frac{R_f}{R_i} \right] = 3.$$

$$R_f = 2R_i.$$

$$\text{Let } R_i = 10 \text{ k}\Omega.$$

$$\therefore R_f = 20 \text{ k}\Omega.$$

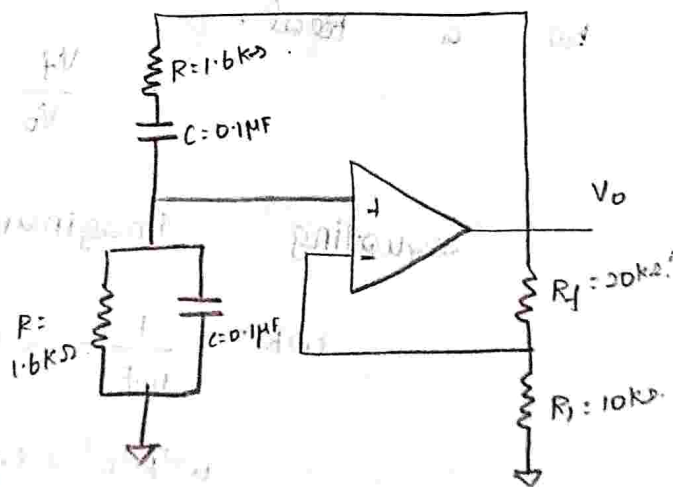


realme 12x 5G

20 April 2026 at 12:24

condition,

for for

Narrow Band Pass Filter (NBPF).

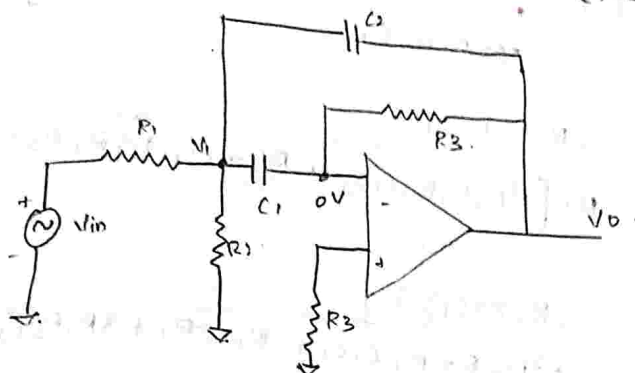

let, $z_1 = 1/sC_1$, $z_2 = 1/sC_2$

write Nodal equation w.r.t Node 'V1'

$$\frac{V_1 - V_{in}}{R_1} + \frac{V_1}{R_2} + (V_1 - V_o) sC_2 + V_1 (sC_1) = 0$$

$$V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} + sC_2 + sC_1 \right] - \frac{V_{in}}{R_1} - V_o (sC_2) = 0 \rightarrow \textcircled{1}$$

write Nodal eqn w.r.t Node 'o'

$$(0 - V_1) sC_1 + \frac{(0 - V_o)}{R_3} = 0$$

$$\frac{V_o}{R_3} = -V_1 sC_1$$


$$V_1 = \frac{-V_o}{sR_3C_1} \rightarrow \textcircled{2}$$

apply equation $\textcircled{2}$ into equation $\textcircled{1}$

$$\left[\frac{-V_o}{sR_3C_1} \right] \left[\frac{1}{R_1} + \frac{1}{R_2} + sC_2 + sC_1 \right] - \frac{V_{in}}{R_1} - V_o (sC_2) = 0$$

$$V_o (sC_2) + \frac{V_o}{sR_3C_1} \left[\frac{1}{R_1} + \frac{1}{R_2} + sC_2 + sC_1 \right] = -\frac{V_{in}}{R_1}$$
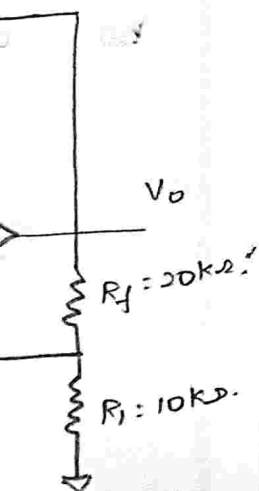
$$V_o \left[sC_2 + \frac{1}{sR_3C_1} \left(\frac{R_2 + R_1 + sR_1R_2C_2 + sR_1R_2C_1}{R_1R_2} \right) \right] = -\frac{V_{in}}{R_1}$$



realme 12x 5G

20 April 2026 at 12:24

$$V_o \left[\frac{s^2 R_1 R_2 R_3 C_1 C_2 + R_2 + R_1 + s R_2 R_1 C_2 + s R_2 R_3 C_1}{s R_1 R_2 R_3 C_1} \right] = \frac{V_{in}}{R_1}$$

$$\frac{V_o}{V_{in}} = \frac{-s R_1 R_2 R_3 C_1}{R_1 [s^2 R_1 R_2 R_3 C_1 C_2 + R_2 + R_1 + s R_2 R_1 C_2 + s R_2 R_3 C_1]}$$

$$\frac{V_o}{V_{in}} = \frac{-(R_2 R_3 C_1) s}{s^2 R_2 R_3 R_1 C_1 C_2 + R_2 + R_1 + s R_2 R_1 C_2 + s R_2 R_3 C_1}$$


$$\frac{V_o}{V_{in}} = \frac{-(R_2 R_3 C_1) s}{R_1 R_2 R_3 C_1 C_2 \left[s^2 + \frac{1}{R_1 R_3 C_1 C_2} + \frac{1}{R_2 R_3 C_1 C_2} + \frac{s}{R_2 R_1 C_2} + \frac{s}{R_2 R_3 C_1} \right]}$$

Let, $C_1 = C_2 = C$

$$\frac{V_o}{V_{in}} = \frac{-(s/R_1 C)}{s^2 + \frac{1}{R_1 R_3 C^2} + \frac{1}{R_2 R_3 C^2} + \frac{2s}{R_3 C}}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{(-s/R_1 C)}{s^2 + \frac{2s}{R_3 C} + \frac{1}{R_3 C^2} \left[\frac{1}{R_2} + \frac{1}{R_1} \right]} \rightarrow \textcircled{3}$$

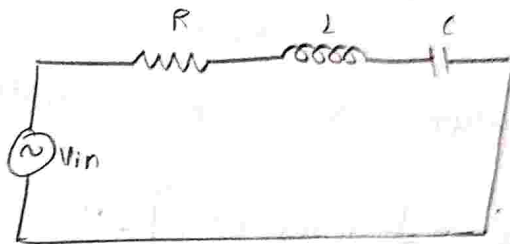Transfer fn of RLC series resonance circuit.



Overall impedance.

$$Z = R + sL + \frac{1}{sC} = \frac{sRC + s^2 LC + 1}{sC}$$

$$V_o = \frac{V_{in} \cdot A_F}{\left[\frac{sRC + s^2 LC + 1}{sC} \right]}$$

realme 12x 5G

20 April 2026 at 12:24 Max Gain of resistance.

Note: P 1

$$C_1] = -\frac{V_{in}}{R_1}$$

$$R_2 C_2 + s R_1 R_2 C_1]$$

$$R_2 C_2 + s R_1 R_2 C_1$$

$$\frac{1}{R_1 C_1} + \frac{s}{R_3 C_1} + \frac{s}{R_3 C_2}]$$

→ (3)

circuit.

$$= \frac{V_{in} (s R_2) \cdot A_F}{L C \left[s^2 + \frac{R}{L} s + \frac{1}{L C} \right]}$$

$$V_o = \frac{V_{in} (R/L) s \cdot A_F}{L C \left[s^2 + (R/L) s + 1/L C \right]}$$

$$\therefore \frac{V_o}{V_{in}} = \frac{-s (R/L) \cdot A_F}{s^2 + \left(\frac{R}{L}\right) s + \frac{1}{L C}}$$

Note:

⇒ at resonance Max
o/p occurs
across the resistor
'R'.

$$\therefore V_o = V_R$$

→ (4)

here, quality factor, $Q = \frac{\omega_0 L}{R}$

$$\therefore \frac{R}{L} = \frac{\omega_0}{Q} \rightarrow (5)$$

$$\text{Also } \omega_0^2 = \frac{1}{L C}$$

$$\omega_0 = \frac{1}{\sqrt{L C}} \rightarrow (6)$$

apply equ (5), (6) into equ (4).

$$\therefore \frac{V_o}{V_{in}} = \frac{-s (\omega_0 / Q) \cdot A_F}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2} \rightarrow (7)$$

The above equation (7) represents the
transfer fn of RLC series resonant circuit.

compare equ (7) with equ (3).

$$A_F \cdot \frac{\omega_0}{Q} = \frac{1}{R_1 C}$$

$$\therefore R_1 = \frac{Q}{\omega_0 C \cdot A_F} = \frac{Q}{2 \pi f_0 C \cdot A_F} \rightarrow (8)$$



realme 12x 5G

20 April 2026 at 12:24

111.11

$$\frac{\omega_0}{Q} = \frac{2}{R_3 C}$$

$$R_3 = \frac{2Q}{\omega_0 C} = \frac{2Q}{2\pi f_0 C} = \frac{Q}{\pi f_0 C}$$

$$R_3 = \frac{Q}{\pi f_0 C} \rightarrow (9)$$

also,

$$\omega_0^2 = \frac{1}{R_3 C^2} \left[\frac{1}{R_2} + \frac{1}{R_1} \right]$$

$$\omega_0^2 [R_3 C^2] = \frac{1}{R_2} + \frac{1}{R_1}$$

$$\frac{1}{R_2} = \omega_0^2 [R_3 C^2] - \frac{1}{R_1}$$

$$\frac{1}{R_2} = \omega_0^2 [R_3 C^2] - \frac{1}{(Q/2\pi f_0 C A F)}$$

$$= \omega_0^2 R_3 C^2 - \frac{2\pi f_0 C A F}{Q}$$

$$\frac{1}{R_2} = \frac{Q \omega_0^2 [R_3 C^2] - 2\pi f_0 C A F}{Q}$$

$$\therefore R_2 = \frac{Q}{Q \omega_0^2 (R_3 C^2) - 2\pi f_0 C A F}$$

$$= \frac{Q}{Q \omega_0^2 \left[\frac{Q}{\pi f_0 C} \right] C^2 - 2\pi f_0 C A F}$$

$$= \frac{Q}{Q \omega_0^2 \left[\frac{2Q C^2}{2\pi f_0 C} \right] - 2\pi f_0 C A F}$$

realme 12x 5G

20 April 2026 at 12:24

Q

$2Q^2 \omega_0 C - 2\pi f_0 C A F$

$\therefore \omega_0 = 2\pi f_0$

from

111.11

equ

to



$$= \frac{Q}{\omega_0 C [2Q^2 - A_F]} .$$

$$\therefore R_2 = \frac{Q}{2\pi f_0 C [2Q^2 - A_F]} \rightarrow (10)$$

from equ (9).

$$f_0 = \frac{Q}{\pi R_3 C} \rightarrow (11)$$

likewise from equ (8).

$$f_0 = \frac{Q}{2\pi R_1 C \cdot A_F} \rightarrow (12)$$

equating (11) & (12).

$$\frac{Q}{\pi R_3 C} = \frac{Q}{2\pi R_1 C A_F} .$$

$$\therefore A_F = \frac{R_3}{2R_1} \rightarrow (13)$$

to change centre frequency from $f_0 \rightarrow f_0'$

$$(14) \quad R_2' = R_2 \left[\frac{f_0}{f_0'} \right]^2 .$$



realme 12x 5G

20 April 2026 at 12:24

All resistors used in this IC is 5kΩ
 that's why is called 555 timer.



$$V_1 = \frac{V_{cc}}{R+2R} (2R)$$

$$= \frac{V_{cc}}{3R} (3R)$$

$$V_1 = \frac{2}{3} V_{cc}$$



$$V_1 = \frac{V_{cc}}{3R} (R)$$

$$= \frac{V_{cc}}{3}$$

⇒ If you want to alter the voltage at inverting terminal of IC we connect pin 5.
 ⇒ Capacitor can discharge via Q_1 to create low resistance path.

connect capacitor across the collector terminal of transistor



⇒ Reset - negative edge triggered pulse.

⇒ If Q_2 - ON make $Q'_1 = 1$ o/p is 0. allow reset.

⇒ If I want to disable Reset signal.

Simply Q_2 make OFF

If Q_2 - OFF not allowing Reset

If we connect V_{cc} to Reset, Q_2 become

of Reset signal is disabled.



realme 12x 5G

20 April 2026 at 12:25


MULTIVIBRATOR

USING IC 555


TIMER:



mon

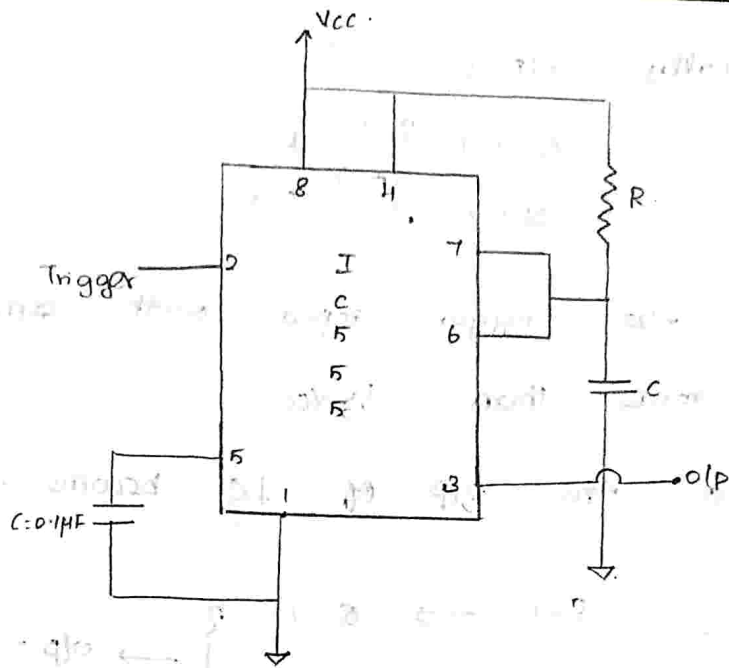

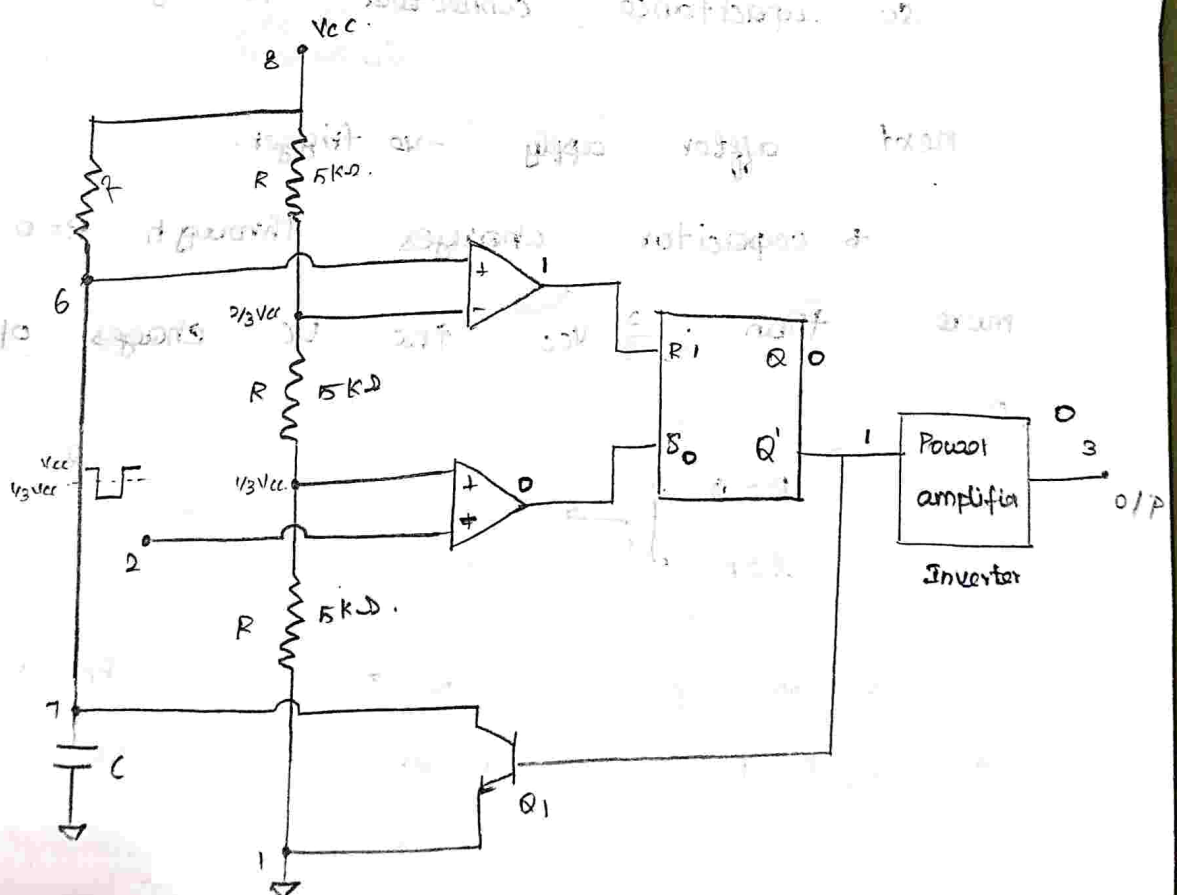This performs monostable operation (or) one-shot multivibrator.



realme 12x 5G modified circuit to perform monostable operation.



Initially, $o/p = 0$.

$$\left. \begin{array}{l} Q' = 1 \\ Q = 0 \end{array} \right\} \rightarrow \begin{array}{l} R = 1 \\ S = 0 \end{array}$$

Apply -ve trigger input with amplitude more than $\frac{1}{3} V_{cc}$.

so the o/p of IC become $= 1$.

after short duration S become 0.

$$\left. \begin{array}{l} S = 1 \\ R = 1 \end{array} \right\} \rightarrow \begin{array}{l} Q = 1 \\ Q' = 0 \end{array} \rightarrow o/p = 1$$

initially, $Q_1 \rightarrow ON$ creates low resistance path so capacitance connected to ground. (discharged).

next after apply -ve trigger.

* capacitor charges through $R=0$ more than $\frac{2}{3} V_{cc}$ the VC charges o/p 0.

$$\left. \begin{array}{l} R = 0 \\ S = 1 \end{array} \right\} \rightarrow \begin{array}{l} Q = 0 \\ Q' = 1 \end{array} \rightarrow o/p = 0$$

$\Rightarrow$ discharge sudden decrease becoz Q_1 of C directly connect to ground without R.


both $R=S=1$, so we need to apply short duration pulse with amplitude more than $\frac{1}{3} V_{cc}$, so $S=1$ long time it changes to $S=0$.

$$\left. \begin{array}{l} S = 0 \\ R = 1 \end{array} \right\} \rightarrow \begin{array}{l} Q = 0 \\ Q' = 1 \end{array} \rightarrow o/p = 0$$



realme 12x 5G

20 April 2026 at 12:25

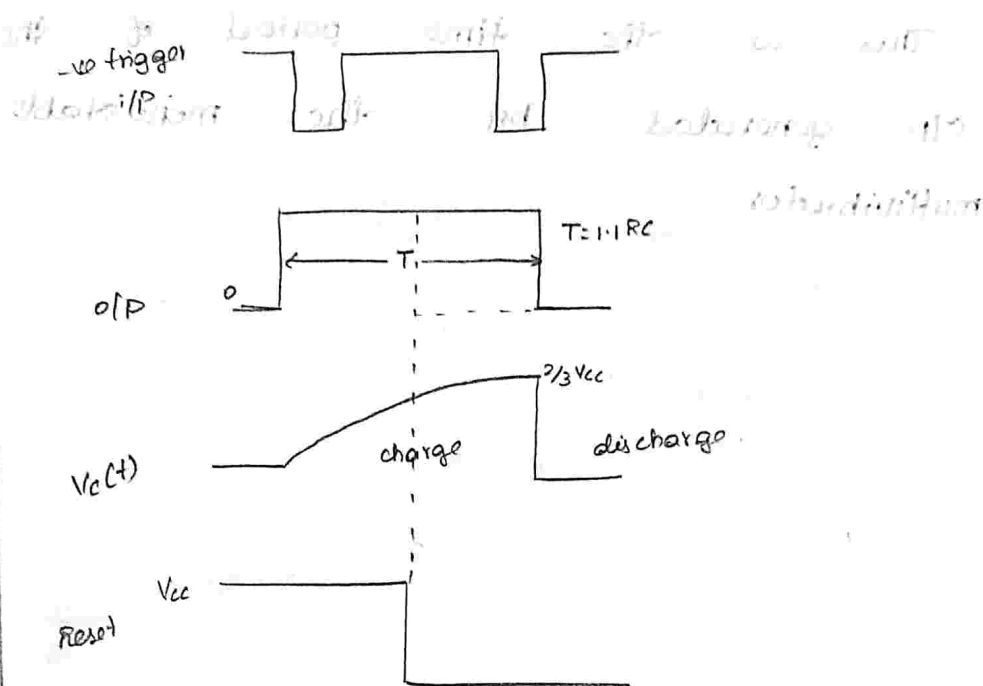

Voltage across capacitance is expressed as.

$$\begin{aligned}
 V_c(t) &= V_f - (V_f - V_i) e^{-t/RC} \\
 &= V_{cc} - (V_{cc} - 0) e^{-t/RC} \quad [\because \text{during charging.}] \\
 &= V_{cc} - V_{cc} e^{-t/RC} \quad \begin{matrix} V_f = V_{cc} \\ V_i = 0 \end{matrix}
 \end{aligned}$$

$$V_c(t) = V_{cc} (1 - e^{-t/RC})$$

at $t = T$, $V_c(t) = \frac{2}{3} V_{cc}$.

$$\frac{2}{3} V_{cc} = V_{cc} [1 - e^{-T/RC}]$$

$$e^{-T/RC} = 1 - \frac{2}{3} = \frac{1}{3}$$

take ln on b/s,

$$-\frac{T}{RC} = \ln \left(\frac{1}{3} \right)$$

$$+\frac{T}{RC} = 1.098$$

$$T = 1.1 RC$$



realme 12x 5G


20 April 2026 at 12:25

This is the time period of the
O/P generated by the monostable
multivibrator.

excitation table:

	Reset. R	Set S	Present state Q	Next state Q _{n+1}
	0	0	0	0
don't care (X)	0	1	0	1
	1	0 (X)	1	0
	0	0	1	1
	1	1	X	X. → Invalid.

Monostable operation using IC 555 timer.

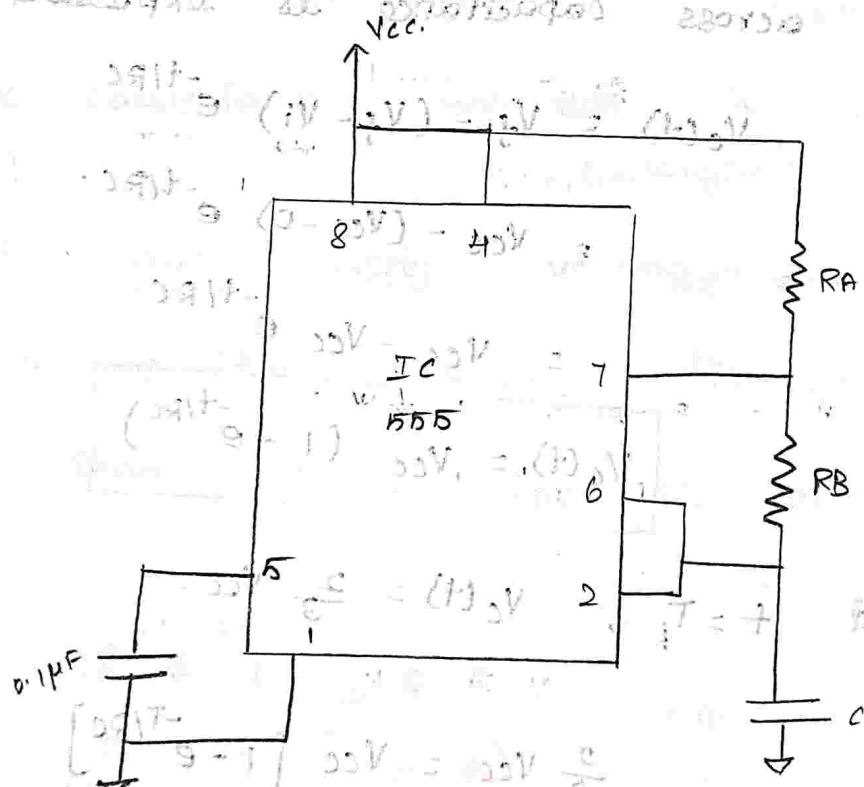


*. Capacitor is charged through two resistor RA & RB.



realme 12x 5G

20 April 2026 at 12:25

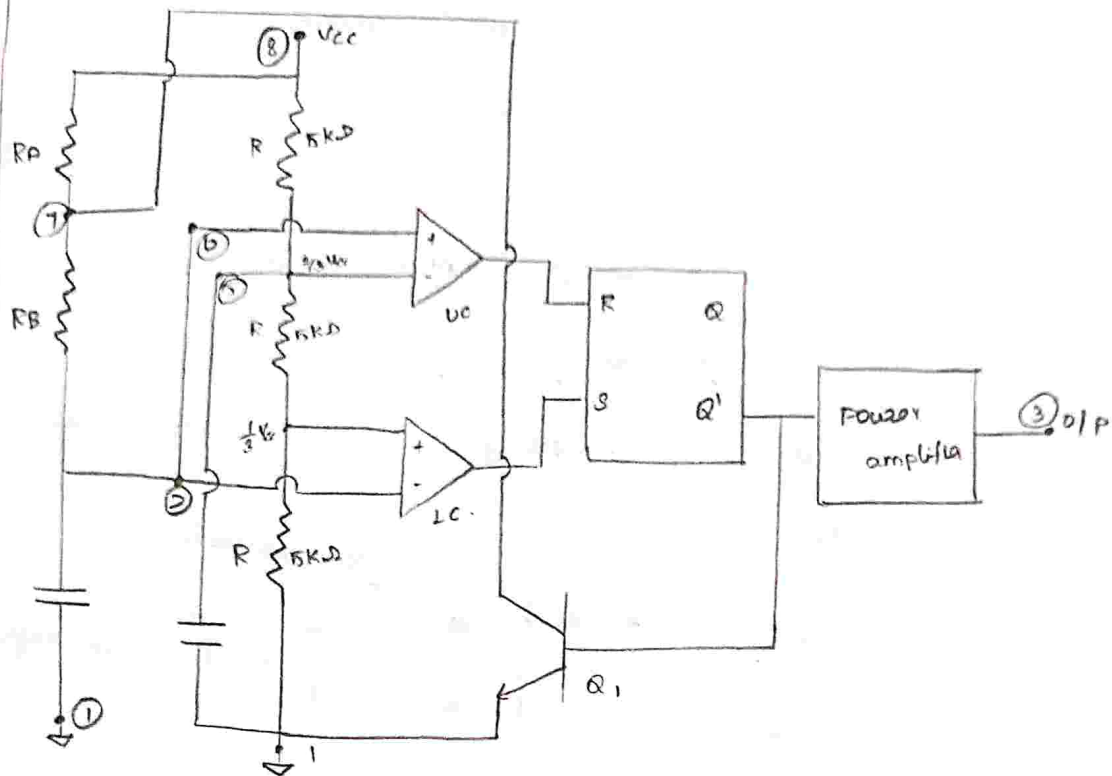

If we don't want the pin 5 (control voltage) so we connect with ground through capacitor.

First: $UC \rightarrow \frac{0}{8} V_{cc}$ in $-ve$ terminal. so o/p of UC $\rightarrow 0$.
No voltage in $+ve$

$LC \rightarrow \frac{1}{3} V_{cc}$ in $+ve$ so o/p of LC $\rightarrow 1$
No volt in $-ve$

$UC \rightarrow 0$ $R = 0$ $\left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow Q = 1$ $\left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow \text{o/p '1'}$
 $LC \rightarrow 1$ $S = 1$ $\left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow \bar{Q} = 0$ $\left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow \text{o/p '1'}$
(there no connection b/w C & ground)

If $\bar{Q} = 0 \rightarrow$ transistor (Q) is OFF, so

capacitor is connected to V_{cc} through R_A & R_B .

capacitor to get charge through

so the voltage at capacitor $\uparrow$ so upto V_{cc} but, after charge beyond $\frac{2}{3}$ (or) $\frac{1}{3} V_{cc}$
 + whenever it is crossing $\frac{1}{3} V_{cc}$,
 $LC \Rightarrow$ -ve terminal more than +ve.

so o/p of $LC \Rightarrow 0$.

But VC unchange becoz $\frac{1}{3} V_{cc} \rightarrow \frac{2}{3} V_{cc}$
 it takes some time.

Now, $R=0$ } $Q=1$ } previous state.
 $LC \Rightarrow 0$ } $S=0$ } $Q'=0$ } $\rightarrow$ o/p = 1 (unchanged)

* When crossing $\frac{2}{3} V_{cc}$,

VC $\Rightarrow$ +ve terminal more than -ve.

so o/p of VC $\Rightarrow 1$

$R=1$ } $Q=0$ }
 $S=0$ } $Q=1$ } $\rightarrow$ o/p = 0

$\bar{Q}=1 \rightarrow$ transistor is ON so capacitor

start discharging through RB.

* Now, whenever $\downarrow$ so below $\frac{2}{3} V_{cc}$.


VC $\Rightarrow$ become +ve < -ve voltage so o/p = 0.

whenever $\downarrow$ so below $\frac{1}{3} V_{cc}$.



$$\left. \begin{matrix} R=0 \\ S=1 \end{matrix} \right\} \rightarrow \left. \begin{matrix} Q=1 \\ Q'=0 \end{matrix} \right\} \rightarrow O/P=1$$

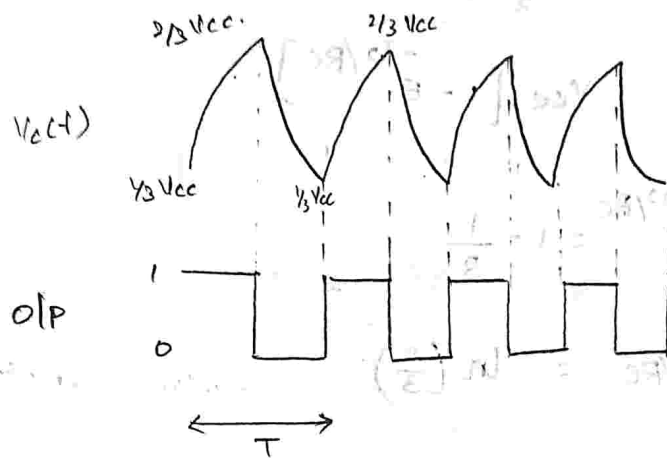$\Rightarrow \bar{Q}=0$, (Q) transistor OFF, charging process occurs.



General equation.

$$V_c(t) = V_f = (V_f - V_i) e^{-t/RC}$$

$$[\because T = t_{\text{high}} + t_{\text{low}}]$$

$t_1 \rightarrow$ capacitor : $0V \rightarrow \frac{2}{3} V_{cc}$.

$t_2 \rightarrow$ capacitor : $0V \rightarrow \frac{1}{3} V_{cc}$.

$$t_{\text{high}} = t_1 - t_2 = \frac{1}{3} \rightarrow \frac{2}{3} V_{cc} \text{ [charging time]}$$

$$V_c(t) = V_{cc} - (V_{cc} - 0) e^{-t/RC}$$

$$V_c(t) = V_{cc} [1 - e^{-t/RC}]$$

at $t = T_1$ $0 \rightarrow \frac{2}{3} V_{cc}$ $t_1 \quad \frac{2}{3} V_{cc} \rightarrow 0$

$$\frac{2}{3} V_{cc} = V_{cc} [1 - e^{-T/RC}]$$

$$e^{-T/RC} = 1 - \frac{2}{3}$$

$$e^{-T/RC} = \frac{1}{3}$$



realme 12x 5G

20 April 2026 at 12:26

$$-T_1/RC = -1.098.$$

$$+T_1 = 1.1 RC.$$

$$\text{at } t \rightarrow T_2. \quad 0 \rightarrow \frac{1}{3} V_{CC}.$$

$$\frac{1}{3} V_{CC} = V_{CC} [1 - e^{-T_2/RC}]$$

$$e^{-T_2/RC} = 1 - \frac{1}{3}.$$

take ln,

$$-T_2/RC = \ln\left(\frac{2}{3}\right)$$

$$\frac{-T_2}{RC} = -0.405$$

$$T_2 = 0.41 RC$$

$$t_{\text{high}} = T_1 - T_2.$$

$$= (1.1 - 0.41) RC.$$

$$t_{\text{high}} = 0.69 RC. \Rightarrow T_{ON} = 0.69 (R_A + R_B) C.$$

$$\therefore t_{\text{low}} \rightarrow \text{discharging} \quad t_2 - t_1. \quad \left(\frac{2}{3} V_{CC} \rightarrow \frac{1}{3} V_{CC}\right)$$

$$V_C(t) = V_f - (V_f - V_i) e^{-t/RC}.$$

$$[V_{CC} \rightarrow 0V]$$

$$= 0 - (0 - V_{CC}) e^{-t/RC}.$$

$$V_C(t) = V_{CC} e^{-t/RC}$$



realme 12x 5G

20 April 2026 at 12:26

$\therefore t_{\text{low}} \rightarrow \text{discharging time } (T_d)$

$$V_c(t) = V_f - (V_f - V_i) e^{-t/RC}$$

$$\frac{2}{3}V_{cc} \rightarrow \frac{1}{3}V_{cc}$$

$$= 0 - (0 - \frac{2}{3}V_{cc}) e^{-t/RC}$$

$$V_c(t) = \frac{2}{3}V_{cc} \cdot e^{-t/RC}$$

at $t = t_d$

$$\frac{1}{3}V_{cc} = \frac{2}{3}V_{cc} e^{-t_d/RC}$$

$$\frac{1}{2} = e^{-t_d/RC}$$

$$\ln(0.5) = -t_d/RC$$

$$-0.693 = -\frac{t_d}{RC}$$

$$\therefore T_d = 0.69 RC$$

$$t_{\text{low}} = t_d = 0.69 R_B C$$

$$T = T_{\text{high}} + T_{\text{low}}$$

$$= T_c + T_d$$

$$T = 0.69 [R_A + 2R_B] C$$

$$f = \frac{1}{T} \approx \frac{1.44}{(R_A + 2R_B)C}$$



realme 12x 5G

20 April 2026 at 12:26

To find Duty cycle: (D)


It is the ratio b/w ON time and total time period.

$$D = \frac{T_{ON}}{T} = \frac{0.69 (R_A + R_B) C}{0.69 (R_A + 2R_B) C}$$

$$D = \frac{R_A + R_B}{R_A + 2R_B}$$

This is suitable for duty cycle is greater than 50%.

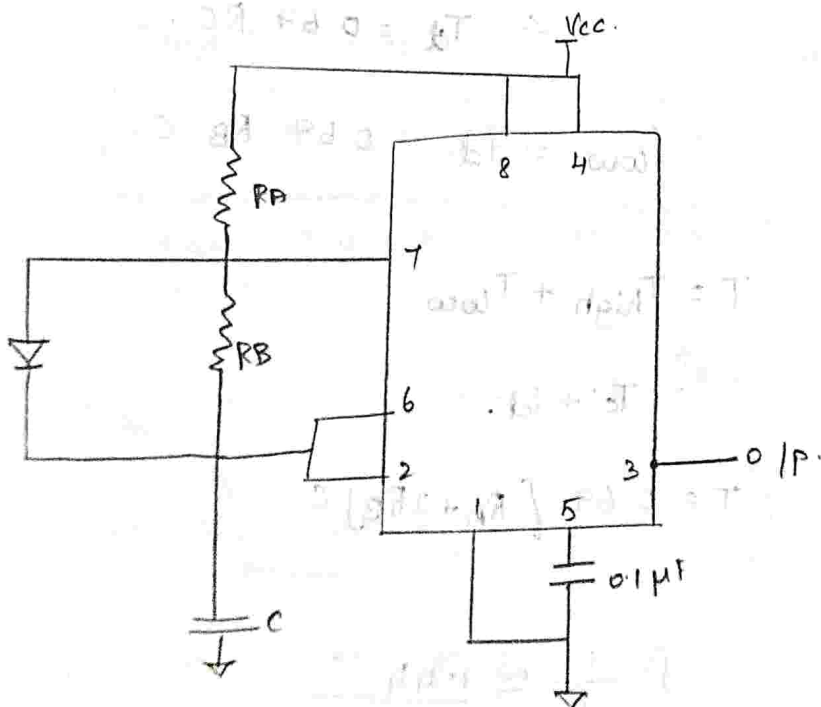To generate < 50%, = 50% we modify the circuit.



The capacitor charge through R_A &



realme 12x 5GB

20 April 2026 at 12:26

$$T_{ON} = 0.69 (R_A) C \quad (\text{charging})$$

design
timer
duty cycle

Note:

$$T_{ON} = C$$

$$T_{OFF} =$$

Sol:-

design an astable multivibrator using IC 555 timer for o/p of frequency 1 kHz and duty cycle of 75%.

Note:

design a astable using

IC-555.

Duty cycle.
> 50%.

Duty cycle
< 50%.

$$T_{ON} = 0.69 (R_A + R_B) C.$$

$$T_{ON} = 0.69 R_A C.$$

$$T_{OFF} = 0.69 R_B C.$$

$$T_{OFF} = 0.69 R_B C.$$

if $D = 50\%$, then $R_A, R_B = R.$

Sol:-

Given, $f = 1 \text{ kHz} = 10^3 \text{ Hz} \Rightarrow T = 1 \text{ ms}.$

$$D = 75\% = \frac{75}{100} = 0.75.$$

$$D = \frac{T_{ON}}{T} \Rightarrow T_{ON} = T \times D = \frac{D}{f}.$$

$$= \frac{0.75}{10^3}$$

$$T_{ON} = 0.75 \times 10^{-3} \text{ s}.$$

$$T = T_{ON} + T_{OFF}.$$

$$T_{OFF} = 1 \text{ ms} - 0.75 \text{ ms}.$$



realme 12x 5G

20 April 2026 at 12:26

$$T_{OFF} = 0.25 \text{ ms.}$$

$$D = \frac{(R_A + R_B)C}{(R_A + 2R_B)C} = 0.75$$

$$R_A + R_B = 0.75 R_A + 1.5 R_B.$$

$$0.25 R_A = 0.5 R_B.$$

$$R_A = 2 R_B.$$

to find R_A & R_B :

$$T_{ON} = 0.69 (R_A + R_B) C = 0.75 \times 10^{-3} \text{ s.}$$

$$(\because R_A = 2 R_B)$$

$$(2 R_B + R_B) C = 1.0869 \times 10^{-3}$$

$$3 R_B C = 1.0869.$$

$$\text{Let } C = 0.1 \times 10^{-6} \text{ F.}$$

$$R_B = \frac{1.0869 \times 10^{-3}}{0.3 \times 10^{-6}}$$

$$R_B = 3.623 \times 10^3 \Omega.$$

$$\therefore R_A = 2 \times R_B.$$

$$R_A = 7.246 \times 10^3 \Omega.$$

$$\therefore R_A = 7.24 \text{ k}\Omega, \quad R_B = 3.623 \text{ k}\Omega.$$

Design

to pr


duty

sol:



realme 12x 5G

20 April 2026 at 12:26

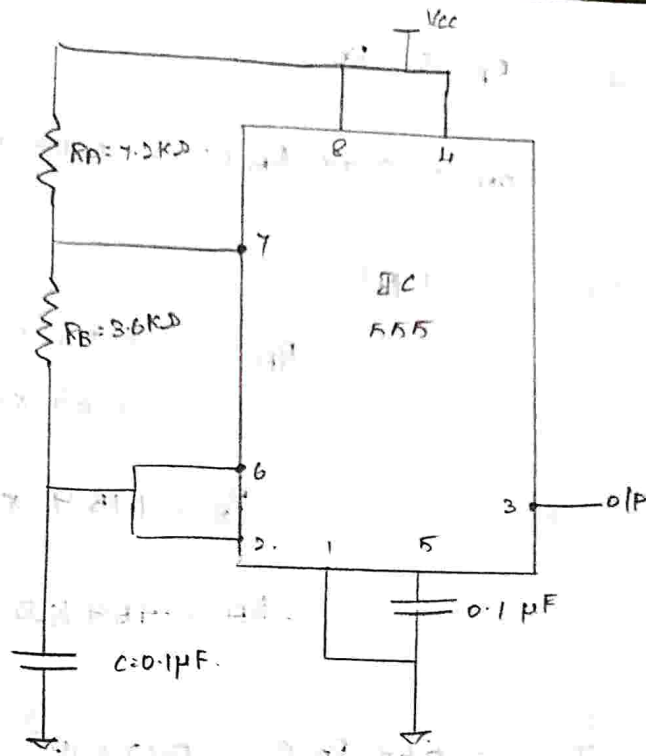

Design an astable multivibrator using IC 555 to produce 5 kHz o/p waveform with duty cycle of 40%.

sol:

Given,

$$f = 5 \text{ kHz} \Rightarrow T = 0.2 \text{ ms.}$$

$$D = 40\% = \frac{40}{100} = 0.4$$

$$D = \frac{T_{ON}}{T} \Rightarrow T_{ON} = T \cdot D = 0.4 \times 0.2 \times 10^{-3}$$

$$T_{ON} = 0.08 \text{ ms.}$$

$$T = T_{ON} + T_{OFF}$$

$$T_{OFF} = (0.2 - 0.08) \times 10^{-3}$$

$$T_{OFF} = 0.12 \text{ ms.}$$



realme 12x 5G

20 April 2026 at 12:26

to find R_A & R_B .

$$T_{ON} = 0.69 R_A C = 0.08 \times 10^{-3}.$$

let $C = 0.1 \mu F$.

$$R_A = \frac{0.08 \times 10^{-3}}{0.69 \times 10^{-7} - 4}$$

$$R_A = 1.159 \times 10^3 \Omega.$$


$$R_A = 1.159 K\Omega.$$

$$T_{OFF} = 0.69 R_B C = 0.12 \times 10^{-3}.$$

let $C = 0.1 \mu F$.

$$R_B = \frac{0.12 \times 10^{-3}}{0.69 \times 10^{-7} - 3}$$

$$R_B = 1.739 K\Omega.$$

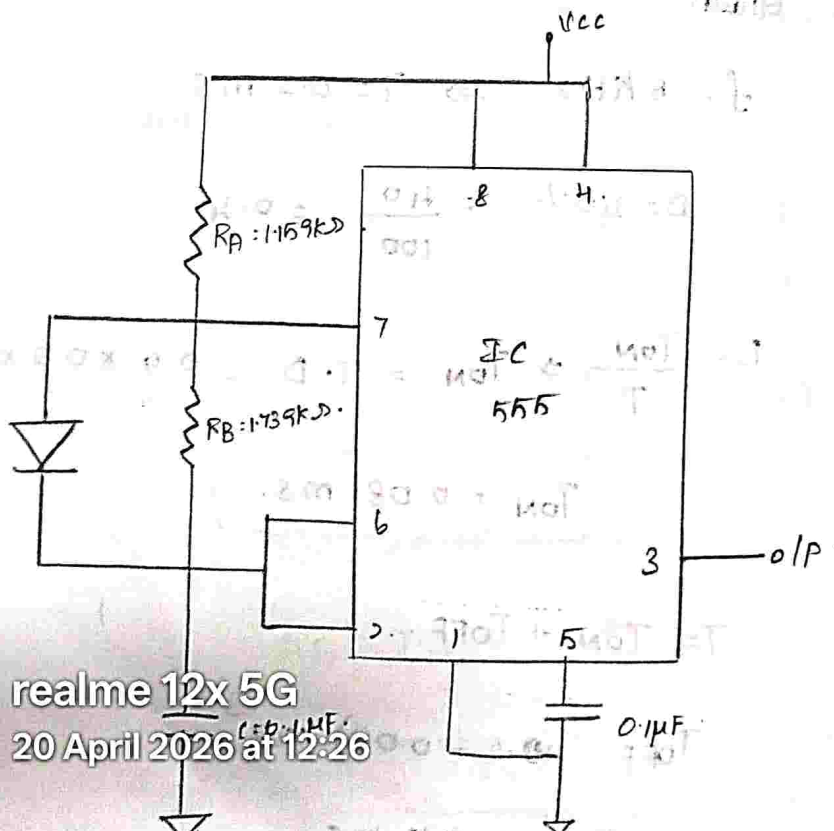

Design

IC 555

5KHz.

Sol:

To f



realme 12x 5G
20 April 2026 at 12:26

Design a astable multivibrator using IC 555 to generate a o/p of 5 kHz. with duty cycle of 50%.

Sol:

Given,

$$f = 5 \text{ kHz} \Rightarrow T = 0.5 \text{ ms}$$

$$D = 50\% = \frac{50}{100} = 0.5$$

$$D = \frac{T_{ON}}{T} \Rightarrow T_{ON} = D \cdot T = 0.5 \times 0.5 \times 10^{-3}$$

$$T_{ON} = 0.25 \text{ ms}$$

$$T = T_{ON} + T_{OFF}$$

$$T_{OFF} = (0.5 - 0.25) \times 10^{-3}$$

$$T_{OFF} = 0.25 \text{ ms}$$

To find R_A & R_B .

$$T_{ON} = 0.69 R_A C = 0.25 \times 10^{-3}$$

$$\text{Let } C = 0.1 \mu\text{F}$$

$$R_A = \frac{0.25 \times 10^{-3}}{0.069 \times 10^{-6}}$$

$$R_A = 3.623 \text{ k}\Omega$$


Thus,

$$R_A = R_B = 3.623 \text{ k}\Omega$$



realme 12x 5G

20 April 2026 at 12:26

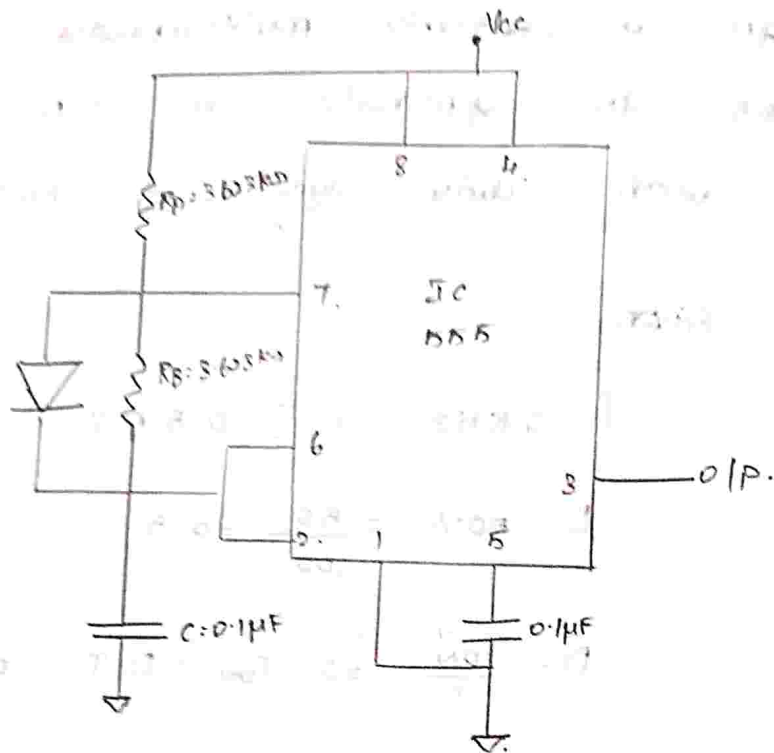

Applications of IC 555 timer in astable mode.

FSK generator circuit: [Frequency shift keying].

free running lamp generator and its derivation

refer PDF (11-03-26)
in ECE family.

Voltage controlled oscillator (VCO).

⊗ * e/p frequency is strongly depends on i/p voltage.

* The frequency of o/p of VCO is

controlled by voltage applied

realme 12x 5G
20 April 2026 at 12:26

manufacturer Name
IC Number

4. 24

EN

N

3 →

3 →


4 →

R_T →

C_T →

buffer → high

Internal

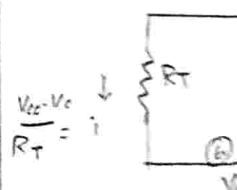

5 → Vc

*. It is 8-pin package.



3 → used to get square wave o/p.

4 → " " " triangle " "


R_T → Timing resistor

NC → No connection

C_T → Timing capacitor

buffer → high i/p impedance logic. (same i/p get at o/p).

Internal circuit:

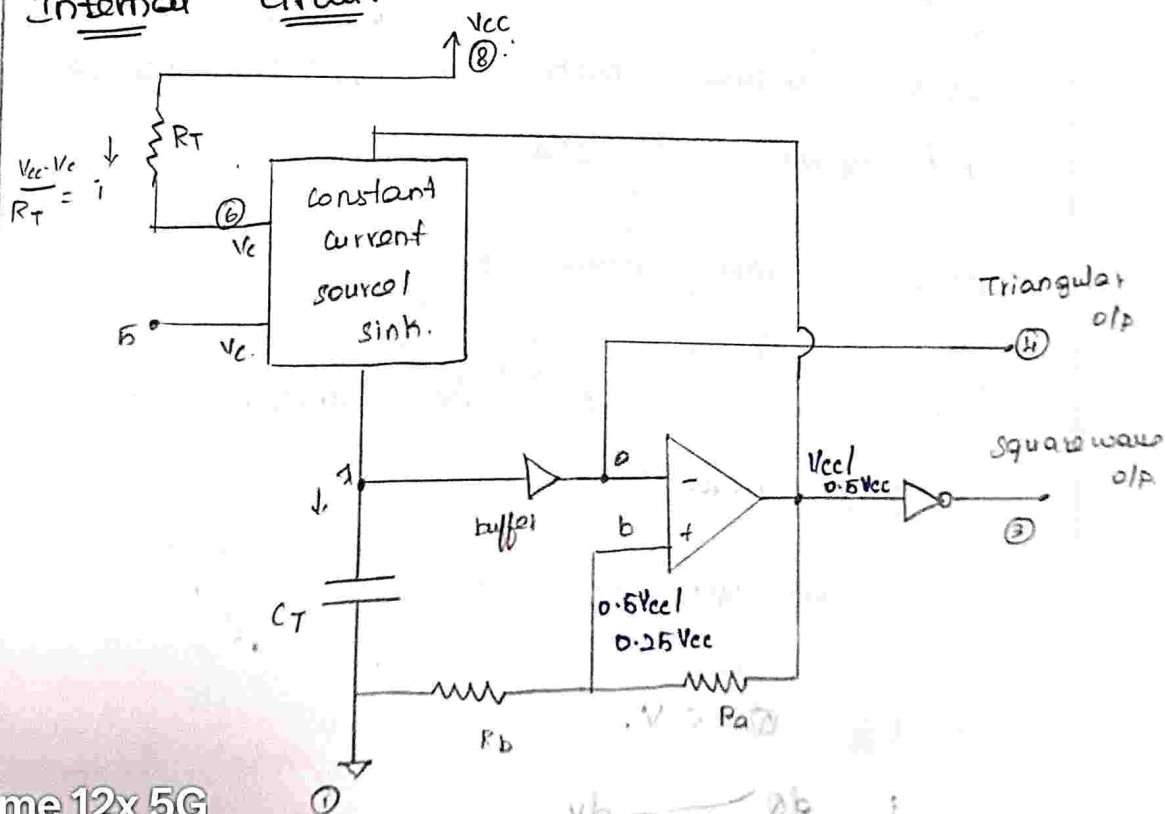

Schmitt trigger



realme 12x 5G

20 April 2026 at 12:26

conditions:

1. Output of Schmitt trigger vary
 V_{cc} to $0.5 V_{cc}$.

$$2. V_T = \frac{V_{cc} R_b}{R_a + R_b} = 0.5 V_{cc} \quad [\because R_a = R_b]$$

How o/p of ST = V_{cc} ↑

$$V_T = \frac{0.5 V_{cc} R_b}{R_a + R_b} = 0.25 V_{cc}$$

o/p of ST = $0.5 V_{cc}$ ↑

* when o/p of ST is V_{cc} , capacitor charges
 when beyond $0.5 V_{cc}$ charges ↑, the
 o/p goes $0.5 V_{cc}$.

* The capacitor discharges when it
 goes below $0.25 V_{cc}$, o/p changes V_{cc}
 and again it charges.

without constant current source,

o/p will be.



by using constant current source.

we get linear o/p



$$Q = C V.$$

realme 12x 5G
 20 April 2026 at 12:26




vary

$$i = c \frac{\Delta V}{\Delta t}$$

This relates the current & voltage difference of capacitor.

$$i = \frac{V_{cc} - V_c}{R_T}$$

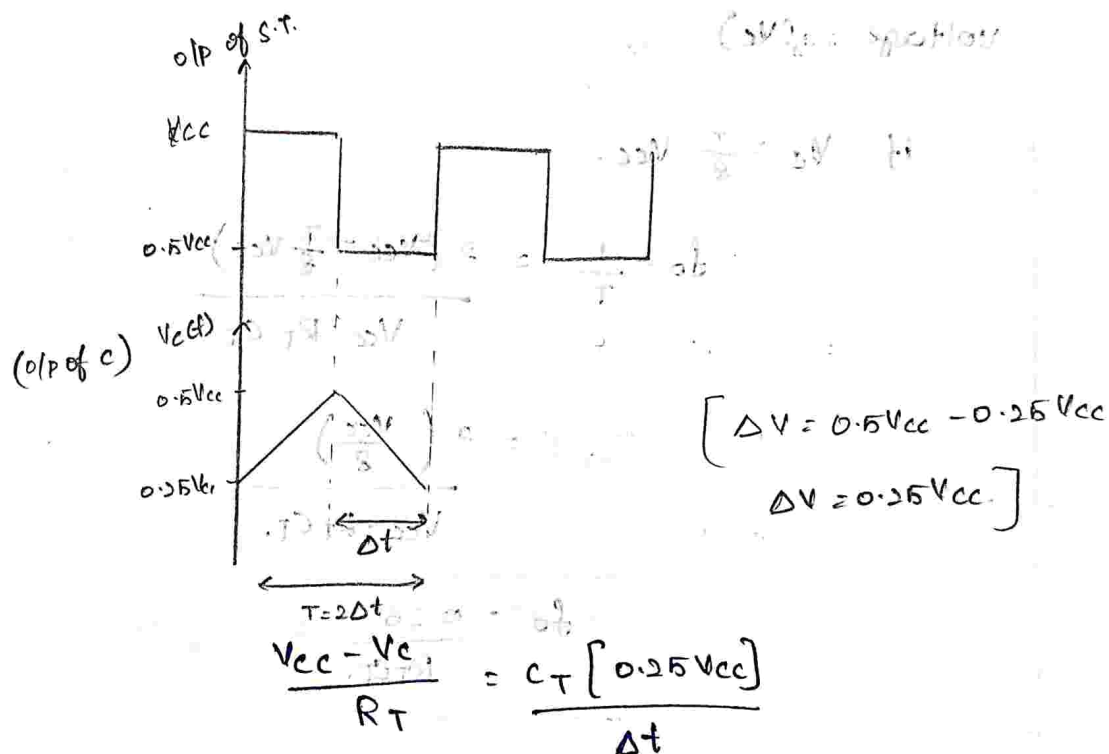$\Delta V \rightarrow$ voltage difference of capacitor.



$$\Delta t = \frac{0.25V_{cc} \cdot C_T \cdot R_T}{(V_{cc} - V_c)}$$

$$T = \Delta t + \Delta t = 2\Delta t = \frac{0.5V_{cc} C_T R_T}{(V_{cc} - V_c)}$$

$\Rightarrow$ it takes Δt for charging & Δt for discharging



realme 12x 5G

20 April 2026 at 12:26

$$f_o = \frac{1}{T} = \frac{2(V_{cc} - V_c)}{V_{cc} \cdot R_T \cdot C_T} \quad \text{--- (1)}$$

General expression of V_{cc}

Here, all are constant (V_{cc} , R_T , C_T) except V_c - control voltage.

The O/P frequency is controlled by voltage (V_c)

$$\text{if } V_c = \frac{T}{8} V_{cc}$$

$$f_o = \frac{1}{T} = \frac{2(V_{cc} - \frac{T}{8} V_{cc})}{V_{cc} \cdot R_T \cdot C_T}$$

$$= \frac{2 \left(\frac{V_{cc}}{8} \right)}{V_{cc} \cdot R_T \cdot C_T}$$

$$f_o = \frac{0.25}{R_T \cdot C_T} \quad \text{--- (2)}$$

Voltage-frequency conversion ratio (K_V):

To change the frequency we should change the V_c .

$$f_o = \frac{2(V_{cc} - V_c + \Delta V_c)}{R_T \cdot C_T \cdot V_{cc}}$$

realme 12x 5G

20 April 2026 at 12:26



$$\underline{W.K.T} \quad f_0 = \frac{2(V_{CC} - V_C)}{R_T \cdot C_T \cdot V_{CC}}$$

$$f_1 - f_0 = \Delta f = \frac{2V_{CC} - 2V_C + 2\Delta V_C}{V_{CC} \cdot R_T C_T} - \frac{2V_{CC} - 2V_C}{V_{CC} R_T C_T}$$

$$\Delta f = \frac{2\Delta V_C}{V_{CC} R_T C_T}$$

$$\frac{\Delta f}{\Delta V_C} = \frac{2}{R_T C_T V_{CC}} \rightarrow \textcircled{3}$$

Sub ② in ③.

$$\frac{\Delta f}{\Delta V_C} = \frac{2}{\frac{0.25}{f_0} V_{CC}}$$

$$\therefore \frac{\Delta f}{\Delta V_C} = \frac{8f_0}{V_{CC}} \Rightarrow K_V$$

Phase - Locked Loop: (PLL) ^{refer pdf (16/3/16)}

It can able to extract the i/p signal.

(or) - It is used to fetch transmitter frequency when i/p is applied.

⇒ when difference btw f_0 & f_s is 90°


then the phase detector will be 0

error voltage

* Main blocks of PLL. (NE/SE 565)

- 1) Phase detector.
- 2) Error amplifier.
- 3) Low pass filter.
- 4) VCO.

Block diagram:

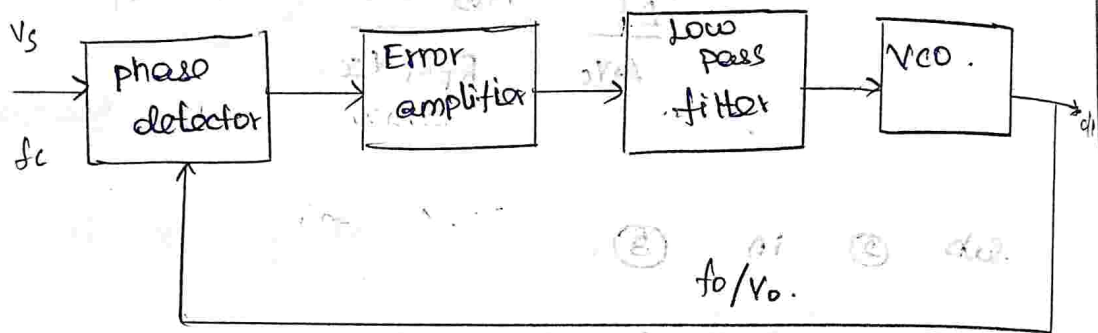

* PLL can be operated in 3 Modes:

1. Free Running Mode. (I/P is not given)
2. Capture Mode. - capture Range
3. Lock Mode. Lock-in Range

Pull - in Time

* In Free Running Mode the PLL act as VCO.

* Remaining 2 modes are used to find when the o/p freq of VCO is equal to

realme 12x 5G

20 April 2026 at 12:26

$$f_o = f_s$$



error amplifier - It depends upon o/p of phase detector (strengthens i/p signal)

phase detector - Generally a multiplier circuit.

o/p is $(f_s + f_o)$ sum of f_s & f_o
diff. of two freq $(f_s - f_o)$

Capture mode $\rightarrow$ PLL starts to track applied i/p.

Lock mode $\rightarrow$ PLL can exactly maintain the same relationship $f_o = f_s$ (i/p freq.)

capture range - over a period of time when it is tracking the i/p signal.

Lock-in range $>$ Capture Range, $\Delta f_L > \Delta f_C$

For better performance
pull-in time: Time taken by the PLL to reach (attain) the lock mode.